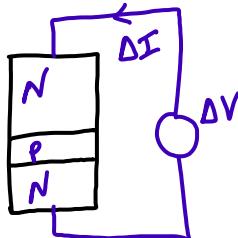


* Output resistance:

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_T}\right) \quad \text{--- (1)}$$




$$\gamma_0 = \frac{\partial V_{CE}}{\partial I_C}$$

$$\frac{\partial I_C}{\partial V_{CE}} = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} = \frac{I'_C}{V_A}$$


$$\gamma_0 = \left(\frac{\partial I_C}{\partial V_{CE}} \right)^{-1} \underset{\substack{\text{fixed} \\ \sqrt{V_{BE}}}}{= \frac{V_A}{I'_C}}$$

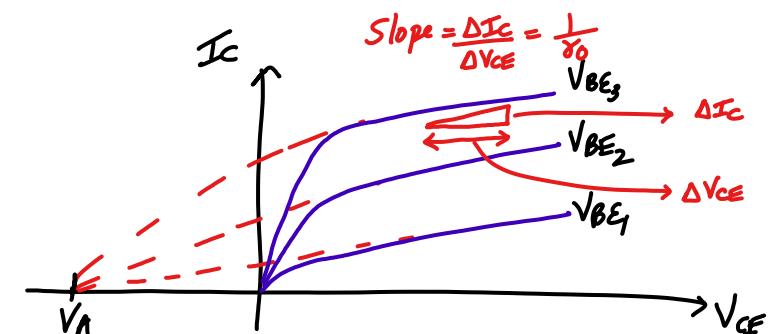
$$\boxed{\gamma_0 = \frac{V_A}{I_C}} \quad \text{--- O/P resistance of NPN BJT}$$



Large signal model (NPN BJT)

NPN BJT
Flw Active
region

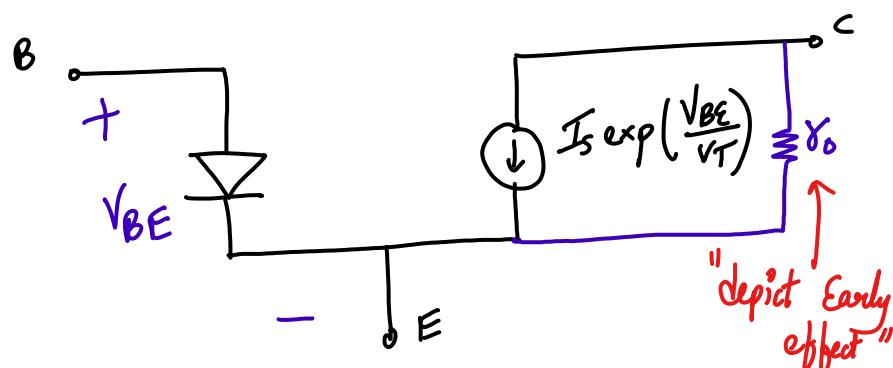

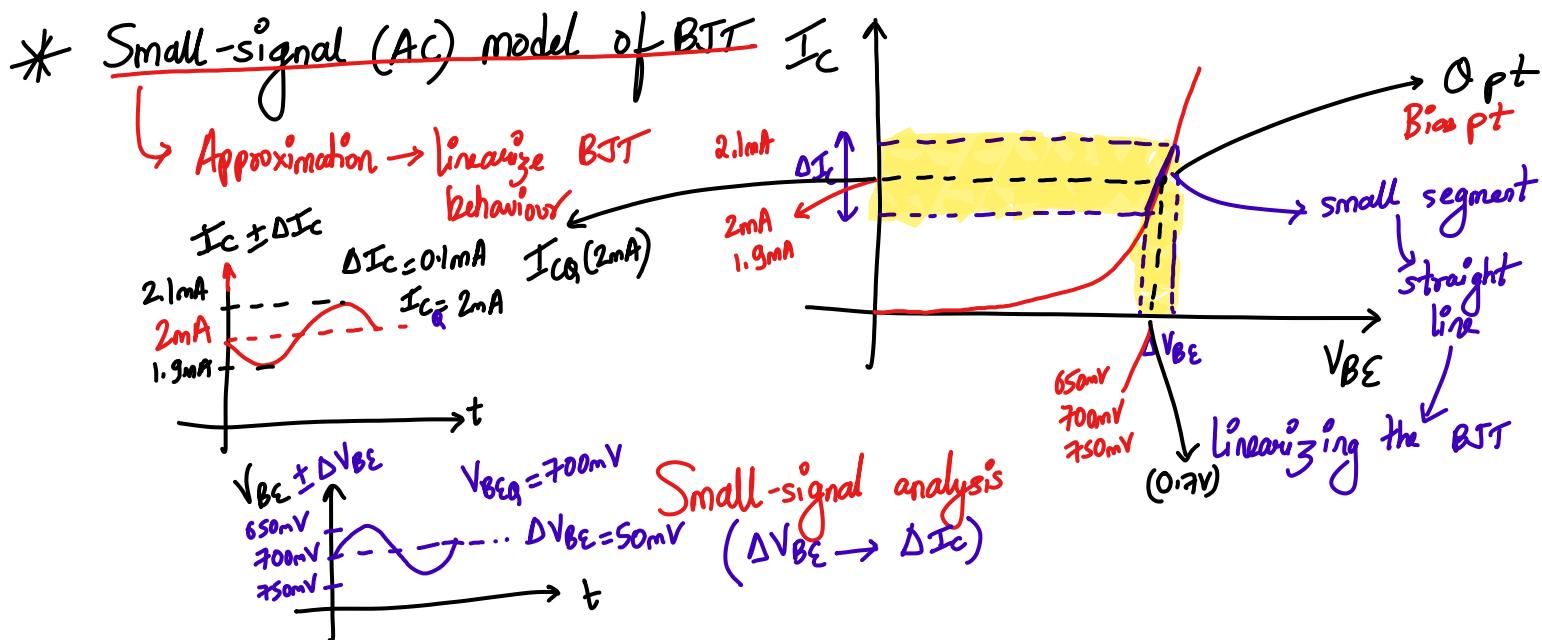

1. $I_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$

2. $I_c + \Delta I_c = I_s \exp\left(\frac{V_{BE} + \Delta V_{BE}}{V_T}\right)$

3. $I_c + \Delta I_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \exp\left(\frac{\Delta V_{BE}}{V_T}\right)$

$\rightarrow I_c + \Delta I_c = I_c \exp\left(\frac{\Delta V_{BE}}{V_T}\right)$

$\rightarrow I_c + \Delta I_c = I_c \left(1 + \frac{\Delta V_{BE}}{V_T}\right)$

$\rightarrow \Delta I_c \equiv \frac{\Delta V_{BE}}{V_T} I_c$

$V_T = 26 \text{ mV}$ at R.T

Transconductance (g_m):

$$\frac{\Delta I_c}{\Delta V_{BE}} = g_m \quad ; \quad g_m = \frac{I_c}{V_T}$$

Unit: $\frac{\text{mA}}{\text{V}}$

$V_T = 26 \text{ mV}$ at R.T

$$\Delta I_c = g_m \Delta V_{BE}$$

$$\Delta V_{BE} \rightarrow \Delta I_B \quad ; \quad I_c = \beta I_B \quad \Delta I_c = \beta \Delta I_B$$



Input resistance (R_{in}) of BJT

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_B} = \frac{\Delta I_c / g_m}{\Delta I_c / \beta} = \frac{\beta}{g_m}$$

$R_{in} = \frac{\beta}{g_m}$ \rightarrow Input resistance of BJT

Small-signal model of NPN BJT:
(Approximate model) "hybrid-pi model"

$$\Delta I_C = g_m \Delta V_{BE}$$

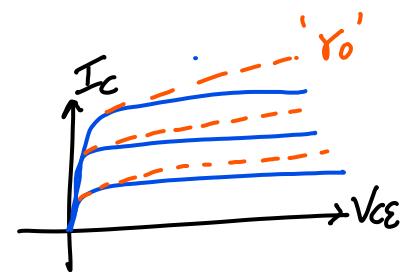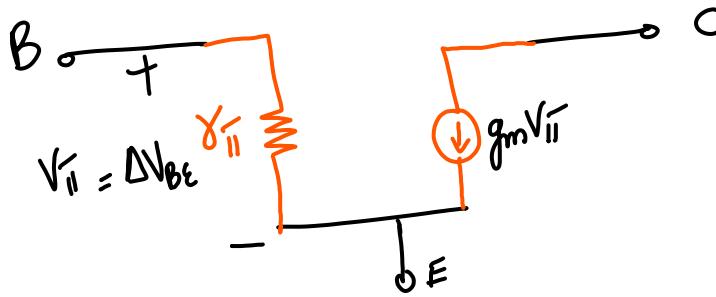

→ Inclusion of Early effect:

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$


$$\frac{dI_C}{dV_{CE}} = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{I_C} \frac{1}{V_A} \equiv \frac{I_C}{V_A}$$

$$r_0 = \left(\frac{\Delta I_C}{\Delta V_{CE}} \right)^{-1} = \frac{V_A}{I_C}$$

$$V_{ii} = \Delta V_{BE}$$

Small signal hybrid-pi model of NPN BJT


β , V_A : given

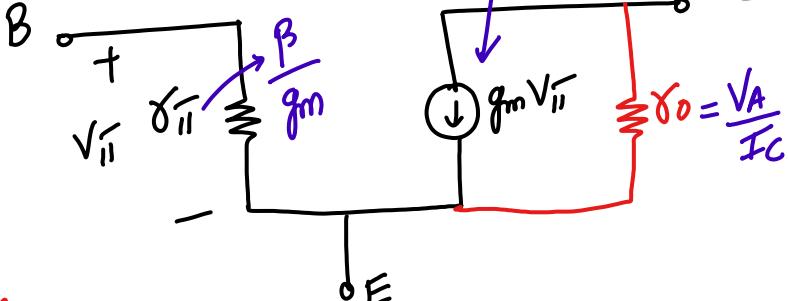

Approximate mode:

- ① F/w active mode
- ② I_C
- ③ $\beta \rightarrow r_{ii}$
- ④ $r_0 \rightarrow V_A$

"AC analysis"

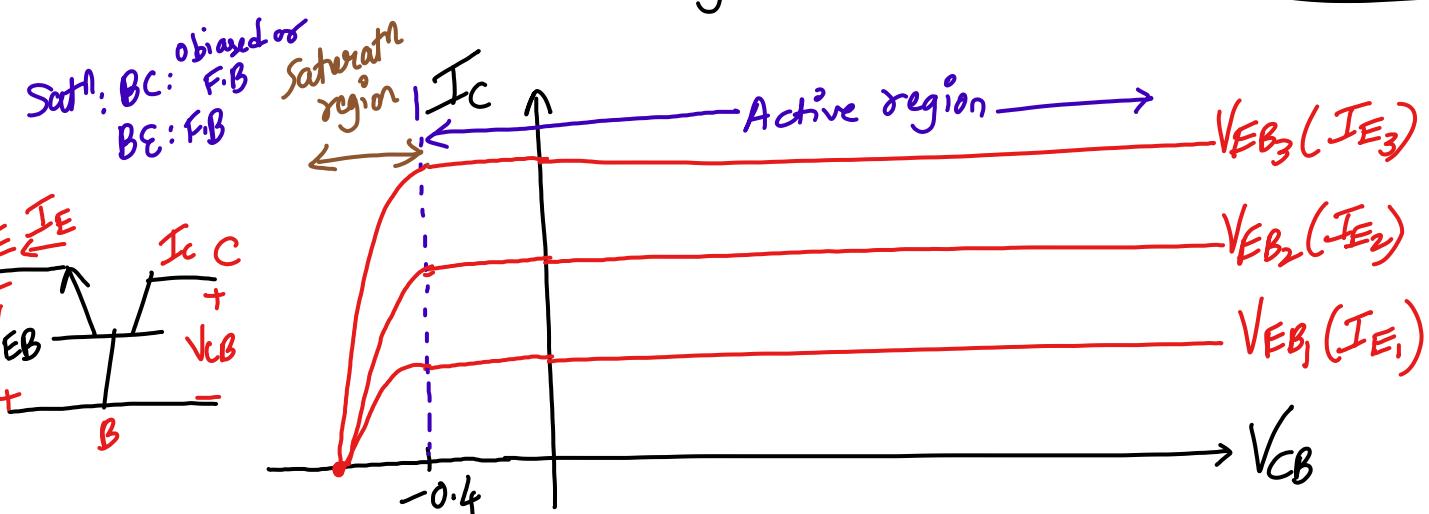

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$


$$I_C = f^n (V_{BE}, V_{CE})$$

$$BEJ^{\eta}: FB$$


$$BCJ^{\eta}: RB$$

$$V_{CB} = V_{CE} - V_{BE}$$

- 0.4V 0.3V 0.7V

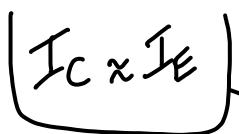$I_C \times I_E$  $V_{CE(sat)} \approx 0.3V$
Active region

Next time: BJT configurations

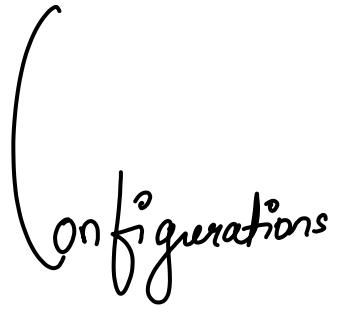- 1) Common Base (CB)
 - 2) Common Emitter (CE)
 - 3) Common Collector (CC)
-  Configurations



