
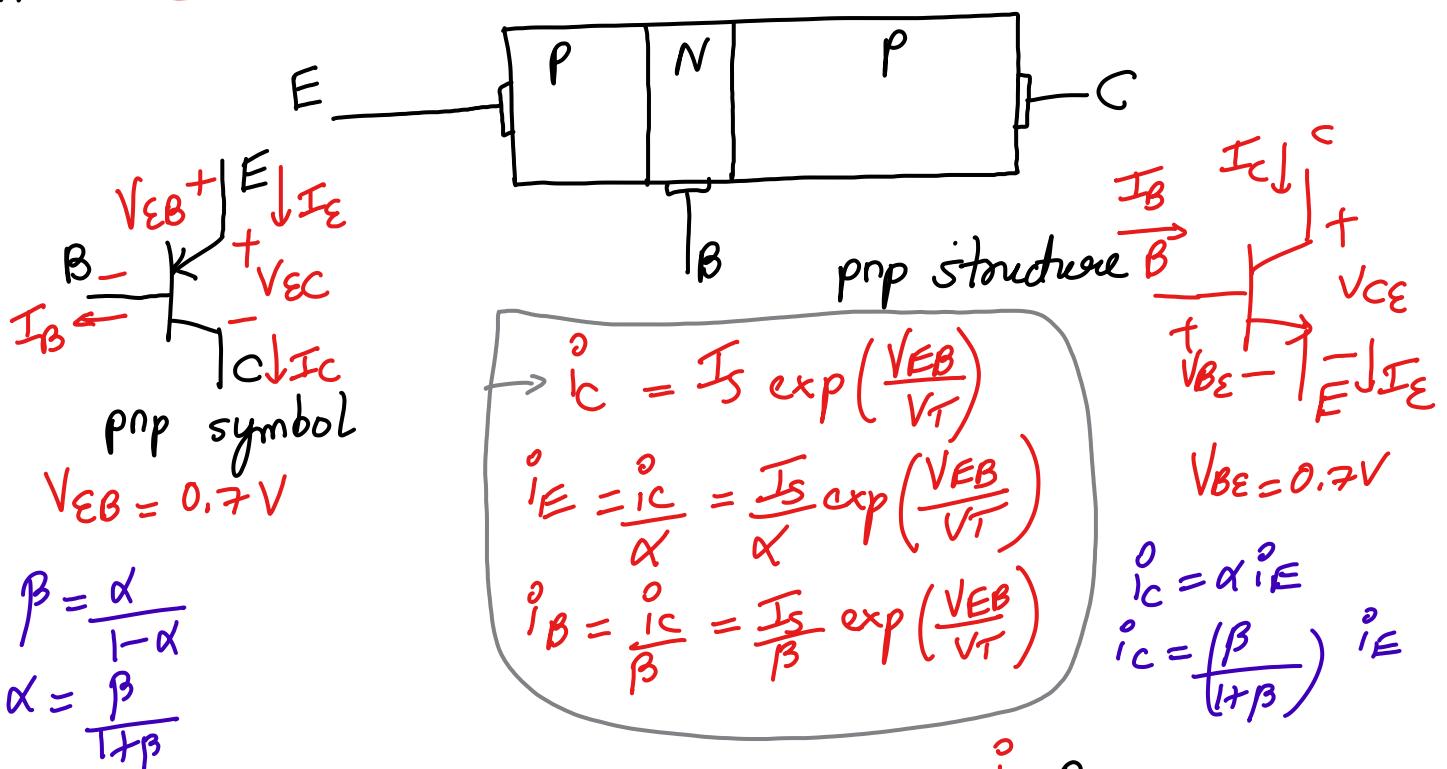



# PNP transistor:

Common-Emitter ckt (pn):

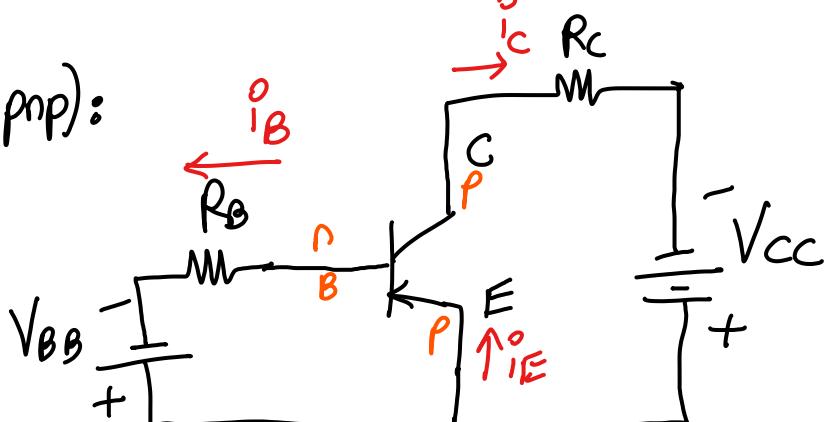

"5m"

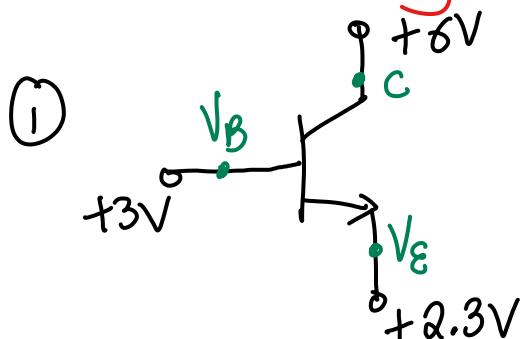Min Numerical 1:- Identify region of operation of given device



→ Since B-E is F.B  
& B-C is R.B

Given npn obj is in forward-Active mode

$$V_C = 6V, V_B = 3V, V_E = 2.3V$$


$$V_{BE} = V_B - V_E = 0.7V$$

↪ B-E is F.B

$$V_{BC} = V_B - V_C = 3 - 6V$$

$$V_{BC} = -3V$$

↪ B-C is R.B

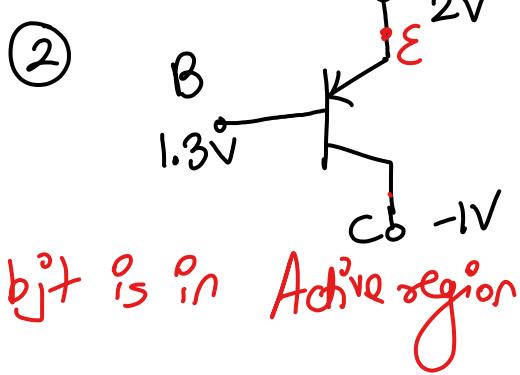

$$V_C = -1V, V_B = 1.3V, V_E = 2V$$

$$V_{EB} = V_E - V_B = 2 - 1.3 = 0.7V$$

$V_{EB} = 0.7V \rightarrow BEJ^n$  is F.B



$$\rightarrow V_{CB} = V_C - V_B = -1 - 1.3 = -2.3V$$

$\downarrow CBJ^n$  is R.B

Numerical 10: Find  $I_{CQ}$  &  $V_{ECQ}$  for ckt shown below

Sol:

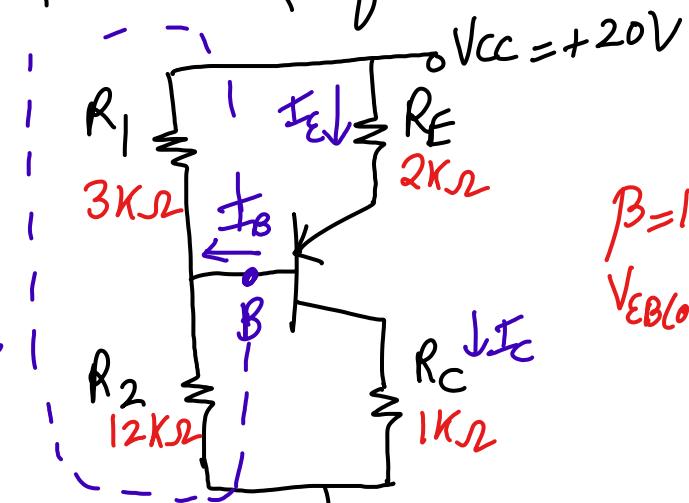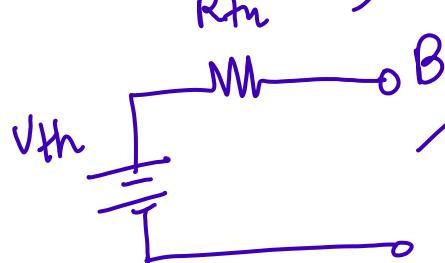i) Apply Thvenin's thm  
at B,  
 $R_{Th}$



$$\beta = 100V$$

$$V_{EB(on)} = 0.7V$$

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{cc} ; R_{Th} = R_1 // R_2$$

$$V_{Th} = \left( \frac{12}{12+3} \right) \times 20 = 16V$$

$$R_{Th} = 3k // 12k = 2.4k\Omega$$

KVL to I/P (B-E) loop,

$$V_{Th} + I_B R_{Th} + V_{EB} + I_E R_E - V_{cc} = 0$$

$$V_{Th} + I_B R_{Th} + V_{EB} + (1+\beta) I_B R_E - V_{cc} = 0$$

$$I_{BQ} = \frac{V_{cc} - V_{Th} - V_{EB}}{R_{Th} + (1+\beta) R_E}$$


$$\therefore I_{BQ} = \frac{20 - 16 - 0.7}{2.4 \times 10^3 + 101 \times 2 \times 10^3}$$

$$I_{BQ} = \frac{16.14}{10124} \mu A$$

$$I_E = I_C + I_B$$

$$I_E = \beta I_B + I_B$$

$$I_E = I_B (1 + \beta)$$

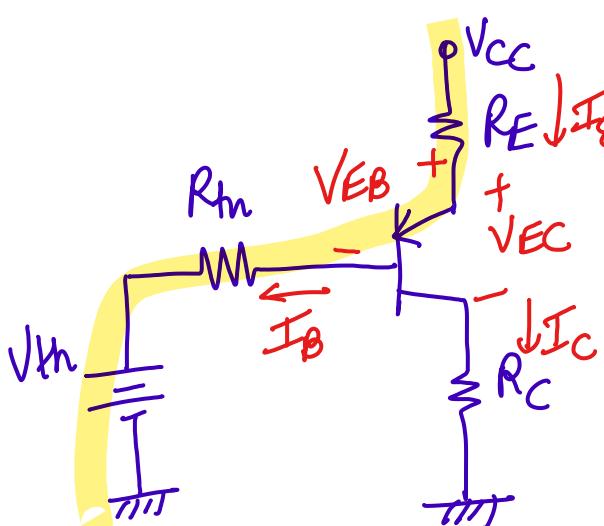

$$I_{CQ} = \beta I_{BQ} = 100 \times 16.14 \mu A = \underline{1.614 mA}$$


KVL to d/p (CE) loop,

$$V_{CC} - I_E R_E - V_{EC} - I_C R_C = 0$$

$$V_{ECQ} = V_{CC} - I_C R_C - I_E R_E$$

$$V_{ECQ} = 20 - 1.614mA \times 2k\Omega - 1.63mA \times 1k\Omega$$
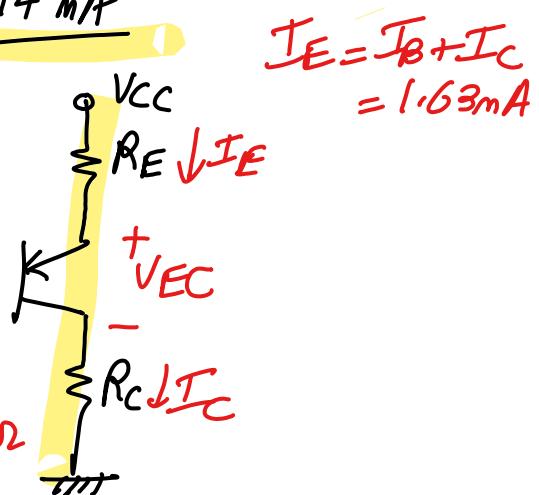
$$\underline{\underline{V_{ECQ} = 15.1V}}$$





## Min<sup>o</sup> Numerical 2<sup>o</sup>

① Identify region of operation

"Cut-off region"

$$V_B = 0$$

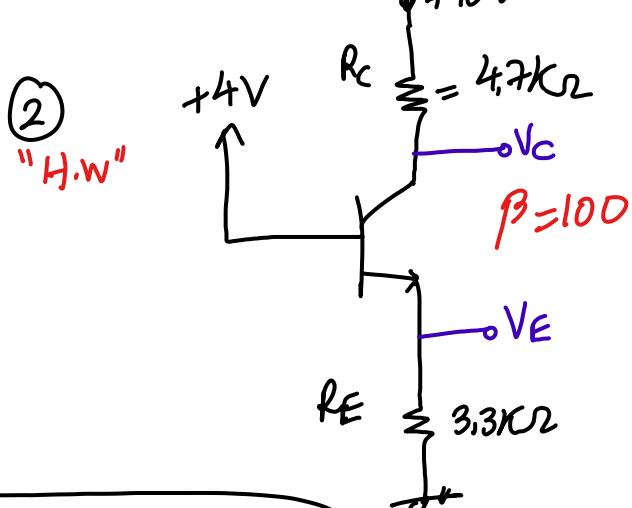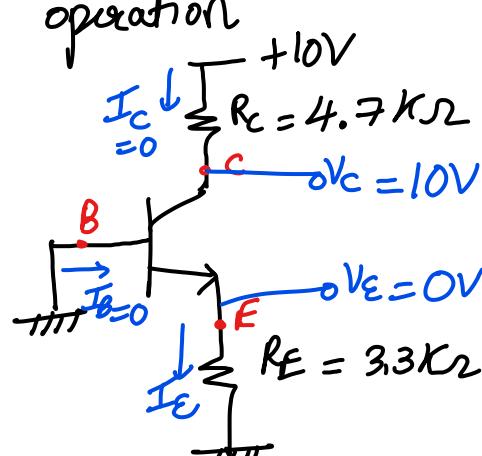

$I_B$   
 $I_C$   
 $V_{BE}$   
 $V_{BC}$

95, 93, 101, 40, 44,  
97, 80, 100, 85, 7,  
8, 26, 64, 6, 70, 58

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{101} = 0.99$$

Solution:

$$\text{a)} V_{BE} = V_B - V_E ; V_B = 4V$$

$$V_E = V_B - V_{BE} = 4 - 0.7$$

$$\underline{\underline{V_E = 3.3V}}$$

$$\text{b)} V_E = I_E R_E$$

$$I_E = \frac{V_E}{R_E} = \frac{3.3}{3.3k\Omega} = \underline{1mA}$$

$$\text{c)} I_C = \alpha I_E = 0.99 \times 1mA = \underline{0.99mA}$$

$$\text{d)} V_C = V_{CC} - I_C R_C = 100 - 0.99 \times 4.7$$

$$\underline{\underline{V_C = 5.3V}}$$

$$e) I_C = \beta I_B \rightarrow I_B = \frac{I_C}{\beta} = \frac{0.99mA}{100} = \underline{\underline{9.9\mu A}}$$

$$f) V_{BC} = V_B - V_C = 4 - 5.3 = -1.3V$$

↳ BC junction is reverse-biased

$$g) V_{BE} = 0.7$$

↳ BE junction is forward-biased

h) BJT is in Active mode of operation

       ×















