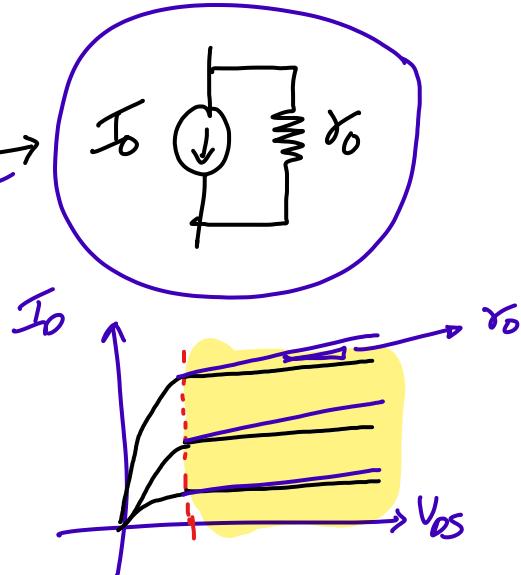
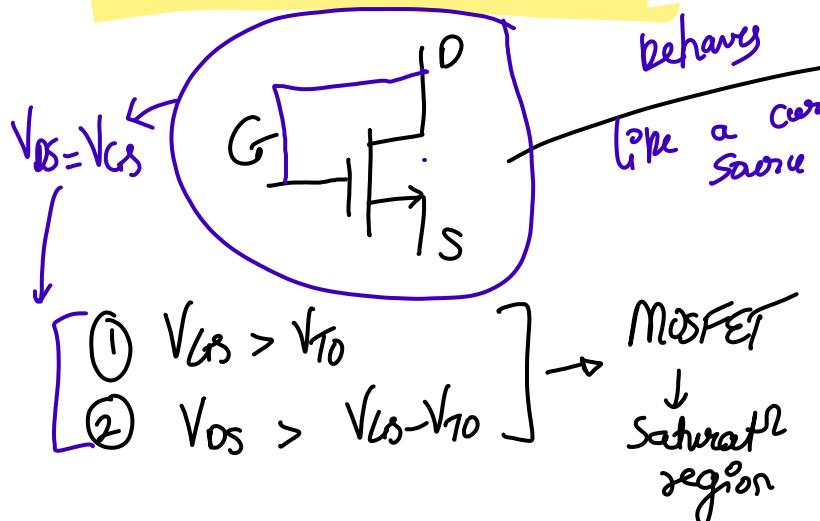



MOSFET current source:

Voltage compliance range:


It is the voltage range over which the circuit can maintain a constant current.

Types of Current mirrors:

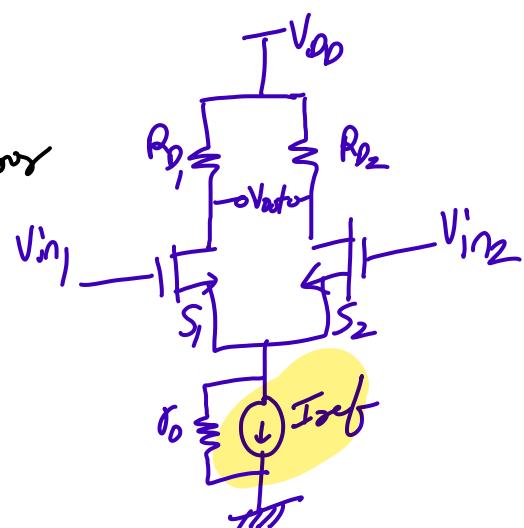- ① Basic two transistor current mirror
- ② Three transistor current mirror
- ③ Cascode current mirror
- ④ Wilson current mirror



Basic two-transistor current mirror:

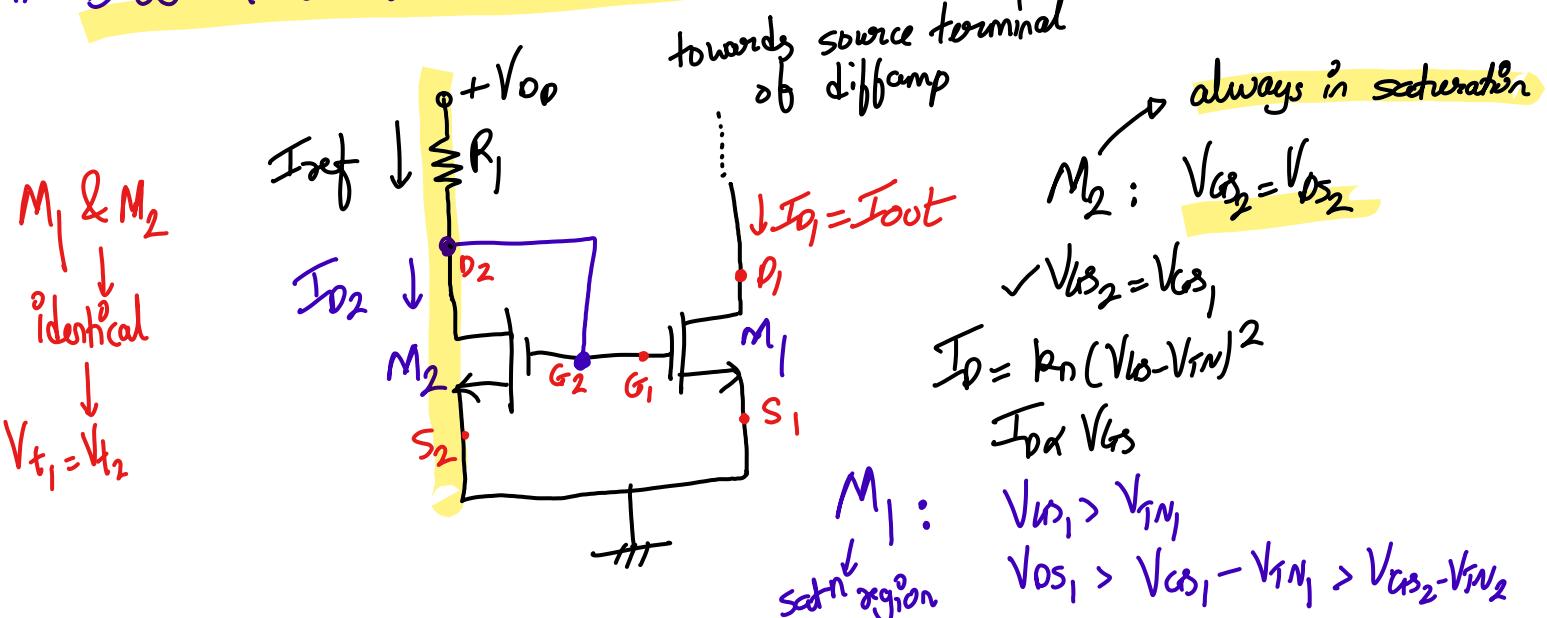

Current relationship,

$$I_{D_{\text{sat}}} = k_n (V_{DS} - V_{TN})^2 (1 + 2V_{DS}) \quad \text{--- (1)}$$

$$k_n = \frac{\mu_n (\text{ox})}{2} \frac{W}{L}$$

γ -channel length modulation parameter

$$\rightarrow I_{\text{out}} = I_{D_1} = k_{n1} (V_{DS_1} - V_{TN_1})^2 (1 + 2V_{DS_1}) \quad \text{--- (2)}$$

$$\rightarrow I_{D_2} = I_{\text{ref}} = k_{n2} (V_{DS_2} - V_{TN_2})^2 (1 + 2V_{DS_2}) \quad \text{--- (3)}$$

M_1 & M_2 are matched \rightarrow same physical parameters (V_{TN} , μ_n , ox & γ)
 in same IC

$$\therefore \frac{I_{\text{out}}}{I_{\text{ref}}} = \frac{I_{D_1}}{I_{D_2}} = \frac{k_{n1} (V_{DS_1} - V_{TN_1})^2 (1 + 2V_{DS_1})}{k_{n2} (V_{DS_2} - V_{TN_2})^2 (1 + 2V_{DS_2})}$$

$$\therefore \frac{I_{\text{out}}}{I_{\text{ref}}} = \frac{\frac{\mu_n (\text{ox})}{2} \left(\frac{W}{L} \right)_1 (V_{DS_1} - V_{TN_1})^2 (1 + 2V_{DS_1})}{\frac{\mu_n (\text{ox})}{2} \left(\frac{W}{L} \right)_2 (V_{DS_2} - V_{TN_2})^2 (1 + 2V_{DS_2})}$$

$$V_{DS_1} = V_{DS_2}, V_{TN_1} = V_{TN_2}$$

$$\boxed{\frac{I_{\text{out}}}{I_{\text{ref}}} = \frac{(W/L)_1}{(W/L)_2} \times \frac{(1 + 2V_{DS_1})}{(1 + 2V_{DS_2})}} \quad \text{--- (4)}$$

$2V_{DS} \ll 1 \rightarrow \text{approximation}$

$$\boxed{\frac{I_{\text{out}}}{I_{\text{ref}}} = \frac{(W/L)_1}{(W/L)_2}}$$

$$I_{\text{out}} = \frac{(W/L)_1}{(W/L)_2} I_{\text{ref}}$$

$$I_{\text{ref}} = 1 \mu A ; I_{\text{out}} = 10 I_{\text{ref}}$$

basis of current mirror

$$\rightarrow V_{DS_2} = V_{DD} - I_{\text{ref}} R_L ; V_{DS_2} = V_{DS_2}$$

$$I_{\text{ref}} = I_{D_2} = k_{n2} (V_{DS_2} - V_{TN_2})^2 (1 + 2V_{DS_2})$$



$$2V_{DS_2} \ll 1$$

$$I_{\text{ref}} = I_{D_2} = R_{D_2} (V_{DD} - I_{\text{ref}} R_1 - V_{TN_2})^2$$

$$R_1, V_{00}, V_{IN_2}, R_{N_2} \rightarrow I_{Zef} \rightarrow$$


O/p resistance of 2-transistor current mirror:-

$$y_0 = ?$$

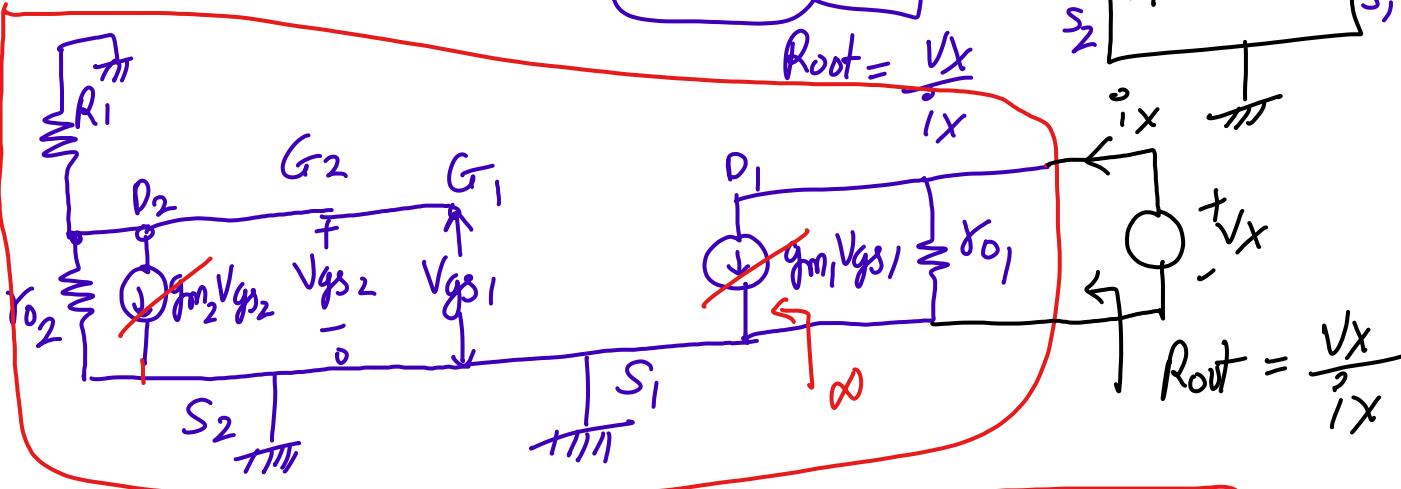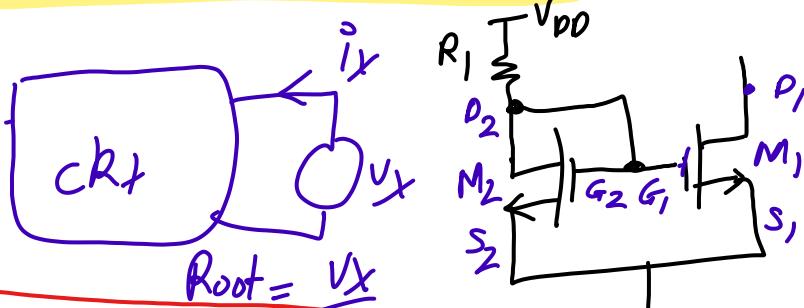

$$R_{\text{out}} = \sigma_0,$$

$$Y_{D_1} = \frac{1}{2\sqrt{D_1}}$$

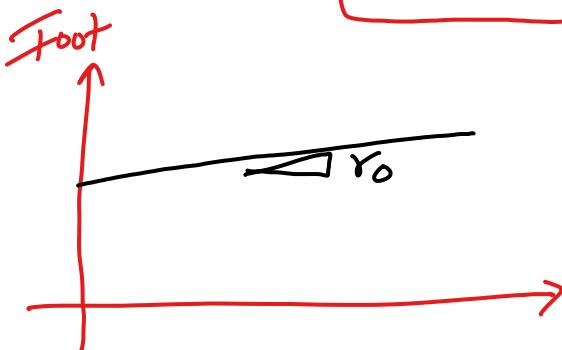

Limitation:- here $R_1 \rightarrow$ (occupy more space in IC)

3 transistor MOSFET current mirror:-

