

DC


Q1.

We get

$$I_x = I_1$$

$$I_y = I_2 - I_3 \\ = I_2 + 1$$

$$I_3 = 1 \text{ A}$$

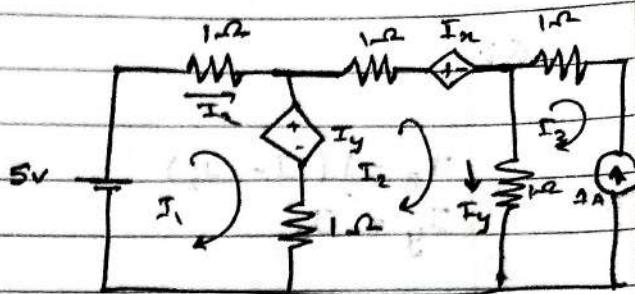

KVL at loop 1

~~$$5 - 1 \cdot I_1 - I_y - 1(I_1 - I_2) = 0$$~~

~~$$5 - 2I_1 - I_2 - I_3 + I_2 = 0$$~~

~~$$2I_1 + I_3 =$$~~

$$2I_1 = 4$$

$$I_1 = 2 \text{ A}$$


KVL at loop 2

~~$$-1(I_2 - I_1) - I_y - 1(I_2) - I_3 - 1(I_2 - I_3) = 0$$~~

~~$$-I_2 + I_1 - I_2 - 1 - I_2 - I_1 - I_2 + 1 = 0$$~~

~~$$-4I_2 - 4 = 0$$~~

~~$$I_2 = -\frac{1}{4} \text{ A}$$~~

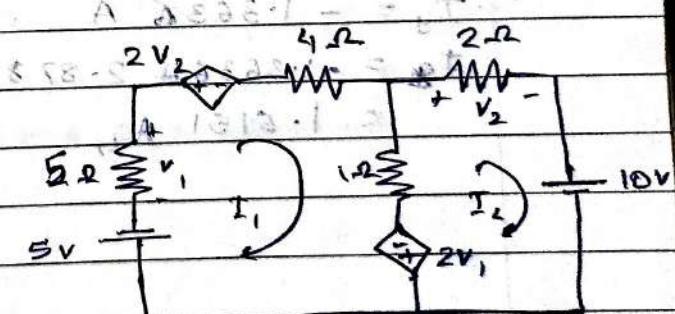

Q2 We get

$$I_x V_1 = -5I_1$$

$$V_2 = 2I_2$$

~~$$\text{KVL at } ① \quad -5 - 5(I_1) - 2V_2 - 4I_1 - 1(I_1 - I_2) + 2V_1 = 0$$~~

~~$$-5 - 5I_1 - 2(-5I_1) - 4I_1 - I_1 + I_2 + 2V_1 = 0 \quad 2(2I_2)$$~~


~~$$-5 - 5I_1 + 10I_1 - 4I_1 - I_1 + I_2 + 4I_2 = 0$$~~

~~$$-5 + 5I_2 = 0$$~~

$$I_2 = 1 \text{ A}$$

~~$$\therefore V_1 = -5(V_2) \quad V_2 = 2(V_1)$$~~

~~$$= -5V_1 \quad = 2V_1$$~~

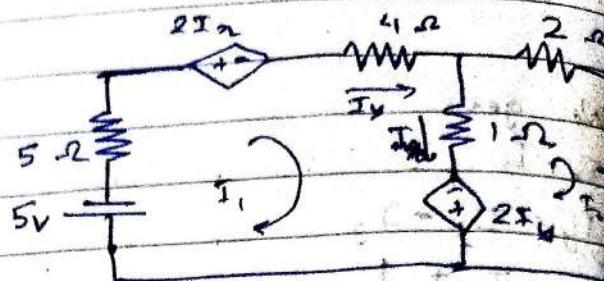

$$I_x = 1(I_1 - I_2)$$

$$I_y = I_1$$

KVL at loop 1

$$-5 - 5I_1 - 2I_x - 4I_1 - 1(I_1 - I_2) + 2I_y = 0$$

$$-5I_1 - 2(I_1 - I_2) - 4I_1 - I_1 + I_2 + 2(I_1) \quad \text{Eq 1}$$

$$-5I_1 - 2I_2 - 4I_1 - I_1 + 2I_1 + 2I_2 + 2I_2 = 5 \quad \text{Eq 2}$$

$$-10I_1 + 3I_2 = 5 \quad \text{Eq 3}$$

KVL at loop 2

$$-2I_y - 1(I_2 - I_1) - 2I_2 - 10 = 0$$

$$-2I_1 - I_2 + I_1 - 2I_2 = 10$$

$$-I_1 - 3I_2 = 10$$

$$I_1 = -1.3636 \text{ A}$$

$$I_2 = -2.8787 \text{ A}$$


$$I_y = -1.3636 \text{ A}$$

$$I_x = -1.3636 + 2.8787$$

$$= 1.5151 \text{ A}$$

Q2.

KVL loop 2

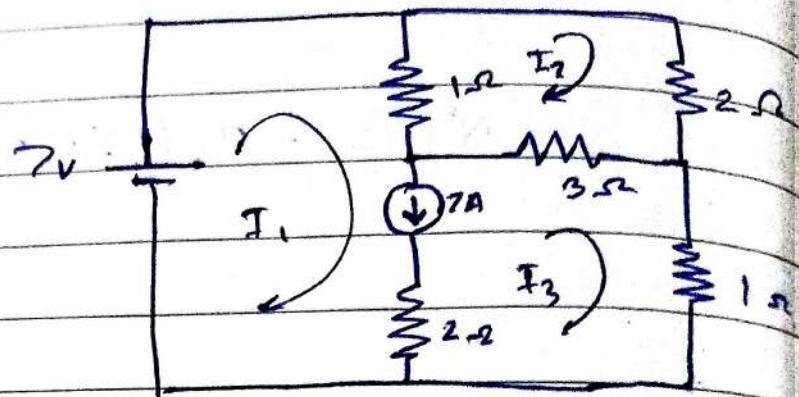

$$7 = 1(I_2 - I_1)$$

$$-3(I_2 - I_1) - 1(I_2 - I_1) - 2I_2 = 0$$

$$-3I_2 + 3I_3 - I_2 + I_1 - 2I_2 = 0$$

$$I_1 - 6I_2 + 3I_3 = 0 \quad 2I_1 = 0$$

$$7 = I_1 - I_3$$

Supermesh 1 & 3

~~$$7 - 1(I_2 - I_1) - 3(I_3 - I_2) - I_3 = 0$$~~

~~$$7 - I_2 + I_1 - 3I_3 + 3I_2 - I_3 = 0$$~~

~~$$7 + I_1 + 2I_2 - 2I_3 = 0$$~~

~~$$I_1 + 2I_2 - 2I_3 = -7$$~~

$$7 - 1(I_1 - I_2) - 3(I_3 - I_2) - I_3 = 0$$

$$7 - I_1 + I_2 - 3I_3 + 3I_2 - I_3 = 0$$

$$7 - I_1 + 4I_2 - 4I_3 = 0$$

$$I_1 - 4I_2 + 4I_3 = 7$$

$$I_1 = 9 \quad I_2 = 2.5 \quad I_3 = 2$$

$$\boxed{I_4 = 40 \text{ A}}$$


Supermesh

$$N_L = +\frac{1}{5} (I_2 - I_1)$$

$$N_L = -2 (I_2 - I_1)$$

S1.

HVL in loop 1

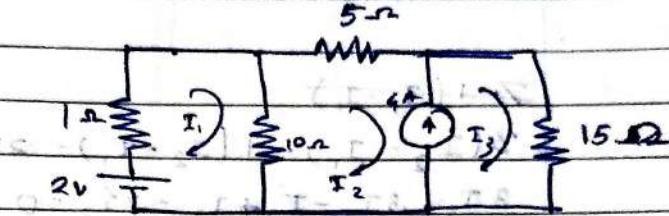

$$2 - 1(I_1) - 10(I_1 - I_2) = 0$$

$$-2 = I_1 - 10I_1 + 10I_2$$

$$-2 = -9I_1 + 10I_2 \quad \text{--- (1)}$$

$$4I_2 - 4 = I_3 - I_2 \quad \text{--- (2)}$$

Supermesh $I_2 \& I_3$

$$-10(I_2 - I_1) - 5I_2 - 15I_3 = 0$$

$$-10I_2 + 10I_1 - 5I_2 - 15I_3 = 0$$

$$10I_1 - 15I_2 - 15I_3 = 0 \quad \text{--- (3)}$$


$$I_1 = -2.3478 \text{ A} \quad I_2 = -2.7826 \text{ A} \quad I_3 = 1.2173 \text{ A}$$

$$I_1 = -2.8695 \text{ A} \quad I_2 = -2.9565 \text{ A} \quad I_3 = 1.0434 \text{ A}$$

Nodal

Date: _____

$$I_{100} = ?$$

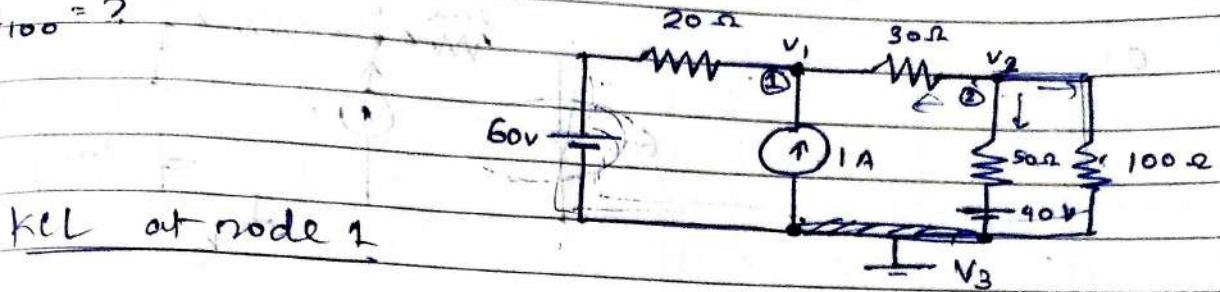

KCL at node 1:

$$I = \frac{V_1 - V_3 - 60}{20} + \frac{V_1 - V_2}{30}$$

$$I = \frac{V_1}{20} - \frac{60}{20} + \frac{V_1}{30} - \frac{V_2}{30}$$

$$I = V_1 \left(\frac{1}{20} + \frac{1}{30} \right) - \frac{V_2}{30} - \frac{60}{20}$$

KCL at node 2:

$$0 = \frac{V_2 - V_1}{30} + \frac{V_2 - V_3}{100} + \frac{V_2 - V_3 - 40}{50}$$


$$0.8 = -\frac{1}{30}V_1 + V_2 \left(\frac{1}{30} + \frac{1}{100} + \frac{1}{50} \right) - \cancel{\frac{V_2 - V_3 - 40}{50}}$$

$$I_{30\Omega} = \frac{V_1 - V_2}{30} + (-)$$

$$I_{100\Omega} = \frac{V_2 - V_3}{100}$$

$$V_{30\Omega} = V_1 - V_2$$

$$N_{100\Omega} = V_2 - V_3$$

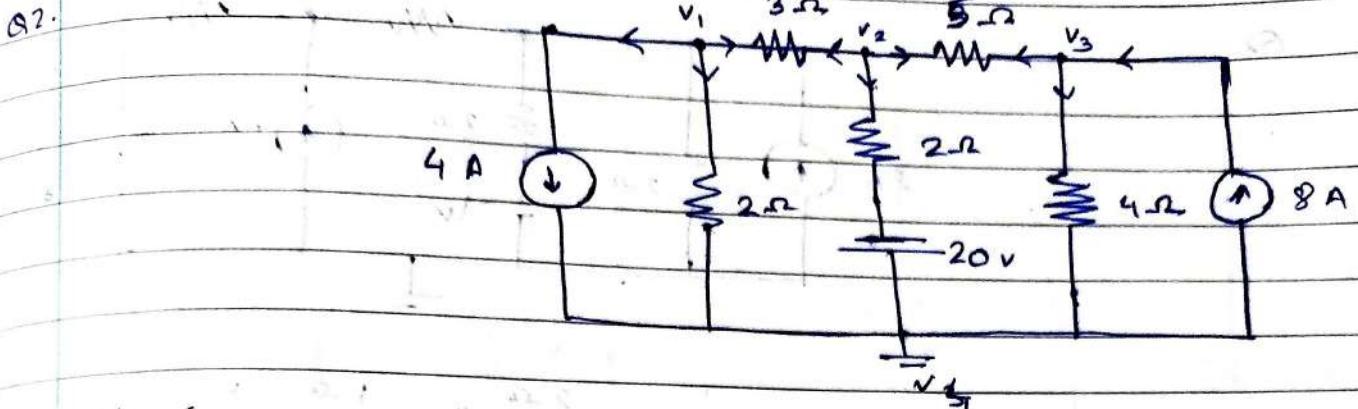

node 1

$$-4 = \frac{v_1 - v_4}{2} + \frac{v_1 - v_2}{3}$$

$$v_4 = 0$$

$$-24 = 3v_1 - 3v_4 + 2v_1 - 2v_2$$

$$-24 = 5v_1 - 2v_2 - 3v_4 \quad \text{--- (1)}$$

node 2

$$0 = \frac{v_2 - v_1}{3} + \frac{v_2 + 20}{2} + \frac{v_2 - v_3}{4}$$

$$0 = 10v_2 - 10v_1 + 15v_2 + 300 + 6v_2 - 6v_3$$

$$10v_1 - 16v_2 + 6v_3 = 300$$

$$10v_1 - 16v_2 + 6v_3 = 300$$

$$-5v_1 - 8v_2 + 150 = 300 \quad \text{--- (2)}$$

node 3

$$8 = \frac{v_3}{4} + \frac{v_3 - v_2}{5}$$

$$160 = 2v_3 - v_2 \quad \text{--- (3)}$$

$$v_1 = 16V \quad v_2 = 52V \quad v_3 = 106V$$

$$v_1 = 16V \quad v_2 = 52V \quad v_3 = 106V$$


$$v_1 = 16V \quad v_2 = 52V \quad v_3 = 106V$$

Nodal

Date:

Q. ∇_{SS}

8.

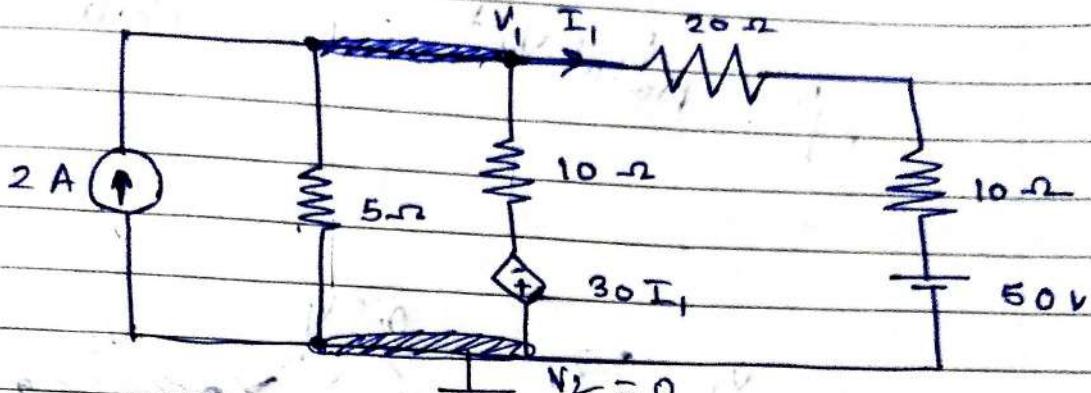

$$I_1 = \frac{V_1 - V_2 - 50}{30}$$

KCL at V_1

$$2 = \frac{V_1 - V_2}{5} + \frac{V_1 - V_2}{10} + 30I_1 + \frac{V_1 - V_2 - 50}{30}$$

$$2 = \frac{V_1}{5} + \frac{V_1}{10} + \cancel{\beta(V_1 - V_2 - 50)} + \frac{V_1 - 50}{30}$$

$$2 = \frac{V_1}{5} + \frac{V_1}{10} + \frac{V_1}{10} - 5 + \frac{V_1}{30} - \frac{50}{3}$$

$$\frac{2+5+5}{3} = V_1 \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{10} + \frac{1}{30} \right)$$

$$V_1 =$$


$$V_{SS} = V_1 - V_2$$

Nodal
eqⁿ: Nodal Volt

Mesh

Date :

loop current
(our)

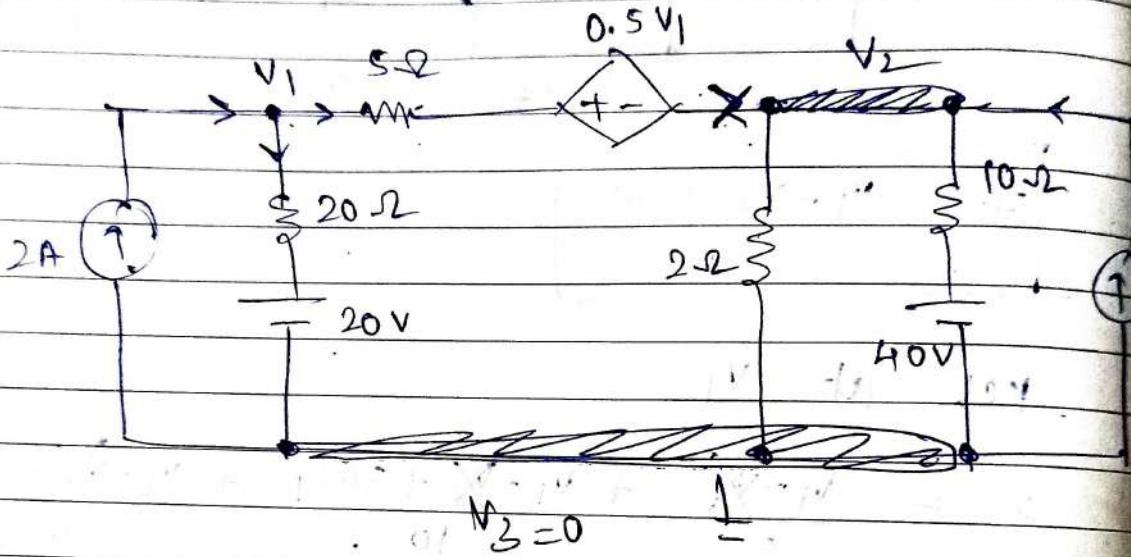

KCL at node V_1 ,

$$2 = \frac{V_1 - V_3 - 20}{20} + \frac{V_1 - 0.5V_1}{5}$$

$$40 = V_1 - V_3 - 20 + 4V_1 - 2V_1$$

$$60 = -2V_1 = 3V_1 \rightarrow V_1 = 20 \text{ V}$$

At V_2

$$4 = \frac{V_2 - V_1 + 0.5V_1}{5} + \frac{V_2}{2} + \frac{V_2 - 40}{10}$$

$$40 = 2V_2 - 2V_1 + V_1 + 5V_2 + V_2 - 40$$

$$80 = -V_1 + 8V_2$$

$$V_1 = 8V_2 = 80$$

$$\Rightarrow 20 - 8V_2 = -80$$

$$8V_2 = -100$$

$$V_2 = -12.5 \text{ V}$$


Whenever only single voltage source is present between two nodes then its a supernode.
no R is series

Date :

Supernode

Type 1

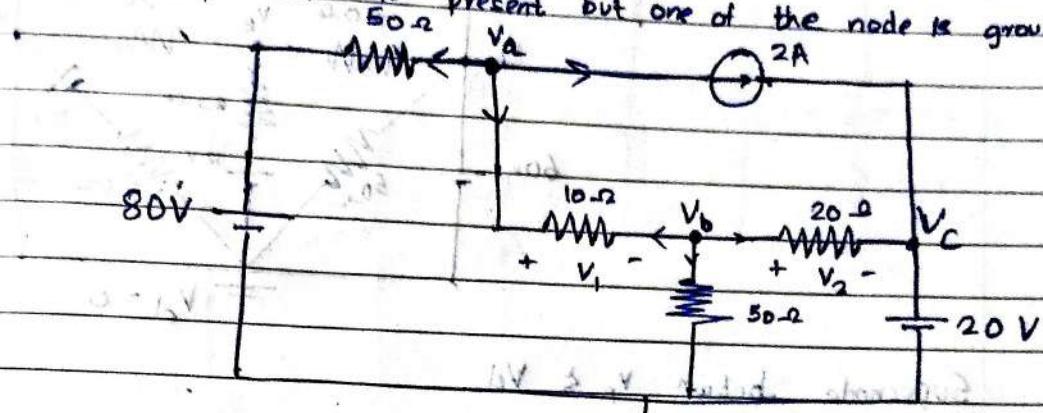In this type Supernode is present but one of the node is ground.



Supernode is present between V_c and V_d since V_d is ground \therefore type 1

volt. source eqn

$$20 = V_c - \cancel{V_d}$$

$$\therefore V_c = 20$$

KCL at node V_a

$$-2 = \frac{V_a - V_d}{50} + \frac{V_a - V_b}{10}$$

$$-100 = V_a - V_d - 80 + 5V_a - 5V_b$$

$$-20 = 6V_a - 5V_b$$

KCL at node V_b

$$0 = \frac{V_b - V_a}{10} + \frac{V_b}{50} + \frac{V_b - V_c}{20}$$

$$0 = 10V_b - 10V_a + 2V_b + 5V_b - 5V_c$$

$$0 = -10V_a + 17V_b$$


$$0 = -10V_a + 17V_b - 5(20)$$

$$100 = -10V_a + 17V_b$$

$$V_a = 3.07 \text{ V}$$

$$V_b = 7.69 \text{ V}$$

Type 2

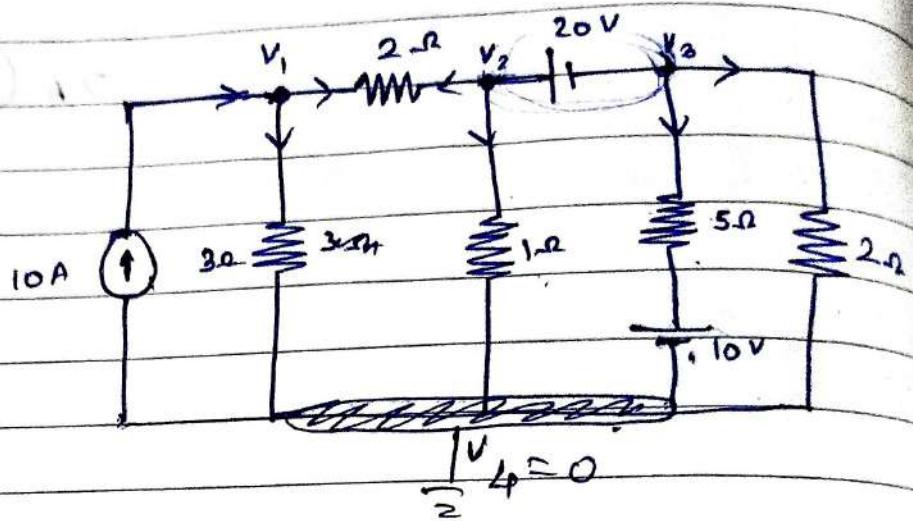

Supernode 2 & 3

Type 2

① KCL to node 1

② volt source eq'

③ KCL to Supernode

$$0 = \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{1} +$$

- KCL at node ΔV_1

$$10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_4}{3} \quad (1)$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_4$$

$$60 = 5V_1 - 3V_2 - 3V_4 \quad (1)$$

$$- 20 = V_2 - V_3 \quad (ii)$$

- Considering V_2 and V_3 as supernode

$$0 = \frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3 - 10}{5} + \frac{V_3}{2} \quad (iii)$$

$$0 = 5V_2 - 5V_1 + 10V_2 + 2V_3 - 20 + 5V_3$$

$$20 = -5V_1 + 15V_2 + 7V_3 \quad (iii)$$

$$V_1 = 18.94 \text{ V}, V_2 = 11.57 \text{ V}, V_3 = -8.42 \text{ V}$$

$$\frac{V_1}{3} + \frac{V_2}{2} + \frac{V_3}{5} + \frac{V_4}{2} = 3 + 8 =$$

$$V_1 = 18.94, V_2 = 11.57, V_3 = -8.42, V_4 = 20$$

$$V_1 = 18.94, V_2 = 11.57, V_3 = -8.42, V_4 = 20$$

Thevenin's , Norton & Max power

Step 1 : To find N_{TH}

- (i) Redraw circuit with disconnecting the common branch through which output is required

 - i] Mark terminal A & B
 - ii] Apply mesh or nodal
 - iii] choose a path from B to A tree from Current Source and apply KVL and hence find V_{AB}


$$V_{AB} = V_{th}$$

Step 2: To find I_N

- i] Redraw the circuit by S.C. branch through which output is req.
 - ii] If S.C branch is horizontal then pass I direction rightwards
If S.C branch is Vertical " " " " downward,
 - iii] Apply mesh or nodal and find I through S.C branches and hence we get I_n .


Step 3: Equivalent Circuit

To find : $R_M = R_N$

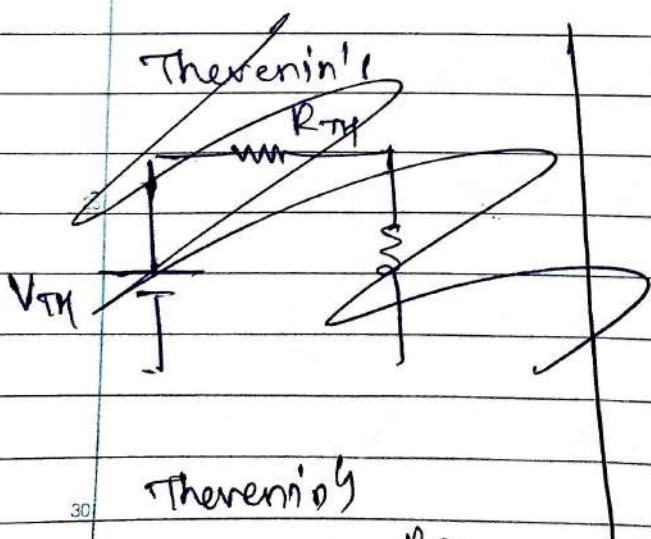


$$R_{TH} = R_N = \frac{N_{TH}}{IN}$$

Steps: eq. ckt

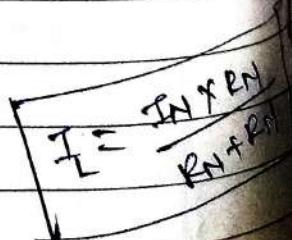

Norton's

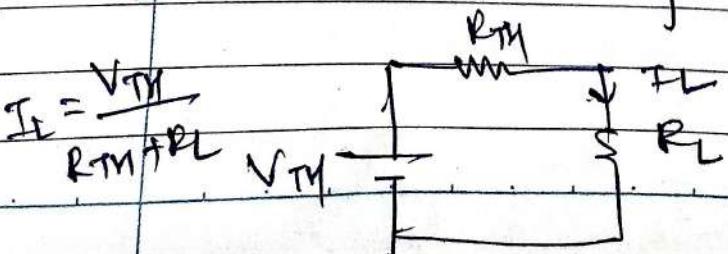


Max power:

$$P_{\max} = \frac{V_m^2}{4R_m}$$


Note if dependent source depends upon Nodal volt then only Nodal Analysis

To find V_{AB}

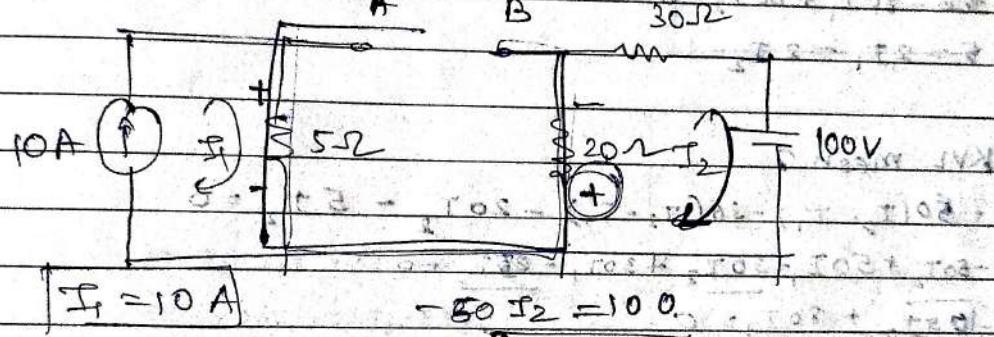

$$V_{AB} = 20I_2 + 5I_1 = +40 + 50 = 10 \text{ V}$$

To find I_1

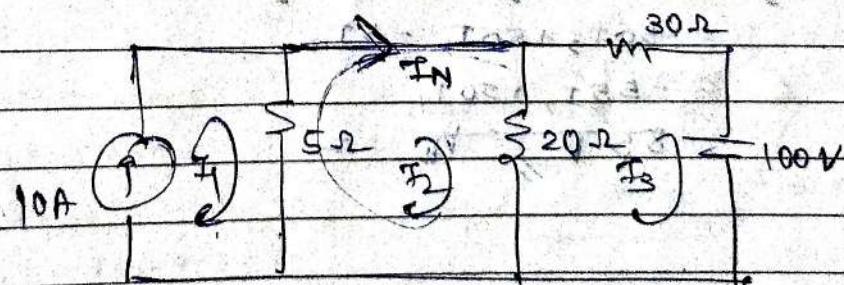

$$I_2 = 0.5882 \text{ A}$$

$$I_3 = -1.7647 \text{ A}$$

$$I_2 = 0.5$$

$$I_2 = 0, I_3 = -2 \text{ A}$$

$$I_1 = 10$$

$$5I_1 - 25I_2 + 20I_3 = 0$$

$$20I_2 - 50I_3 = 100$$

$$I_N = I_2 \approx 6.5882 \text{ A}$$

$$R_{TH} = R_N = \frac{N_{TH}}{I_N} = \frac{10}{0.5882} = 17.00102$$

$\rightarrow V_{th}:$

KVL mesh 1

220

$$220 - 30(I_1 - I_2) - 50(I_1 - I_2) = 0$$

220

$$220 - 30I_1 + 30I_2 - 50I_1 + 50I_2 = 0$$

220

$$220 - 80I_1 + 80I_2 = 0$$

$$5 = 2I_1 - 2I_2$$

KVL mesh 2

$$-50(I_2 - I_1) - 30(I_2 - I_1) - 20I_2 - 5I_2 = 0$$

$$-50I_2 + 50I_1 - 30I_2 + 30I_1 - 20I_2 = 0$$

$$-105I_2 + 80I_1 = 0$$

$$8I_1 = 105A \quad I_2 = 8A \quad 8 \cdot 8 = 64 \\ = 11.65A$$


$$V_{AB} = -50(I_2 - I_1) - 5I_2$$

$$= -50I_2 + 50I_1 - 5I_2$$

$$= -55I_2 + 50I_1$$

$$= 85V$$

$$V_{th} = 85V$$

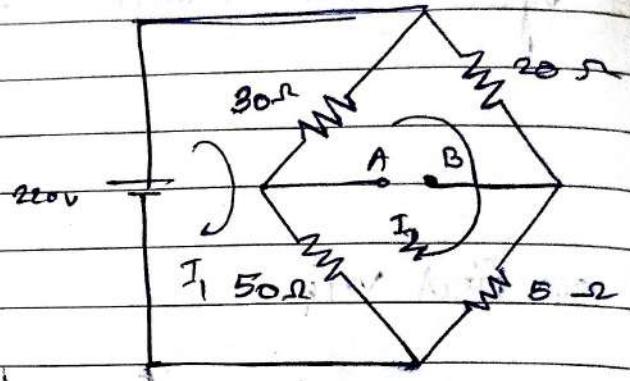


a

$$I_2 = I_1$$

$$I_3 = -2I_2$$

$$3I_2 = 9$$

$$I_2 = 3 \text{ A}$$

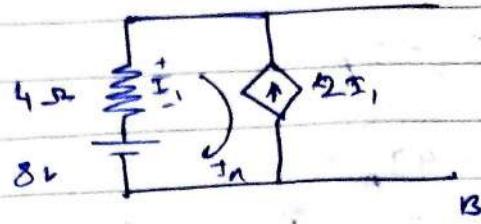


$$\therefore V_{AB} = 8 - 4I_2$$

$$= 8 \text{ V}$$

$$8 - 4I_2 = 0$$

$$8 = 4I_2$$

$$\therefore I_2 = 2 \text{ A}$$

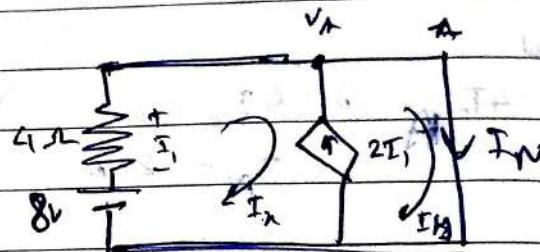


$$4 = I_2 - I_1$$

$$4 = I_2 - 2$$

$$I_2 = 6 \text{ A}$$


$$\therefore I_N = 6 \text{ A}$$

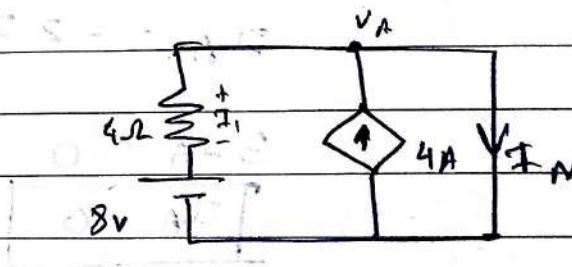

$$R_{th} = \frac{8}{6}$$

$$= 1.3334 \sqrt{2}$$

~~V_B~~ ~~I₁~~ ~~8~~
~~T₃₄~~

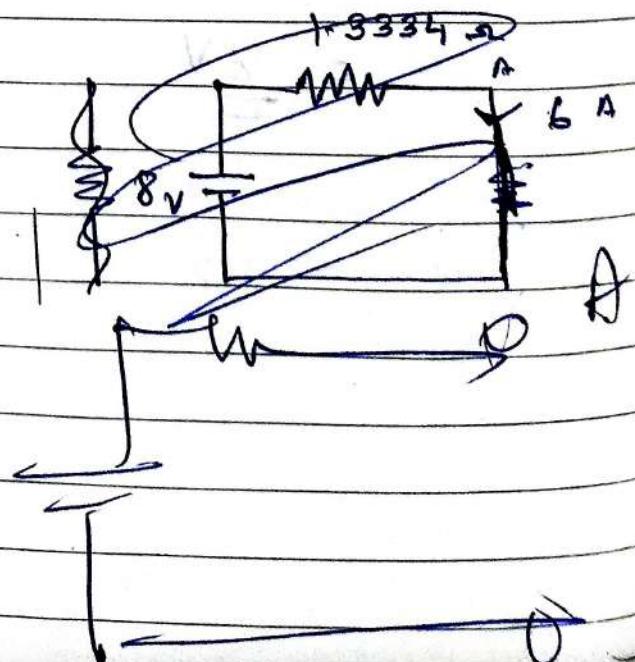

25

30

8.

$$I = I_1$$

$$10I - 20I_1 - 40I_1 - 50 = 0$$



$$50I_1 = 50$$

$$I_1 = 1 \text{ A}$$

$$\therefore I = I_1 = 1 \text{ A}$$

$$V_{AB} = 10 - 20I_1 \\ = -10 \text{ V}$$

$$I_N = I_1 - I_2 \rightarrow$$

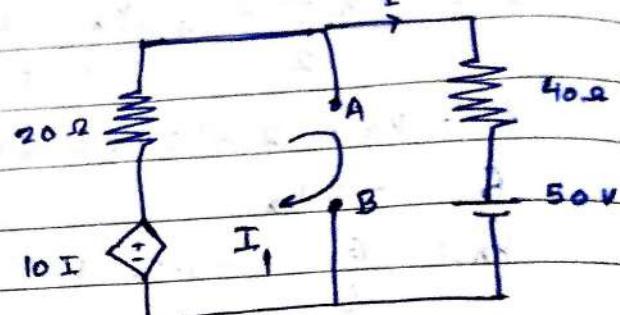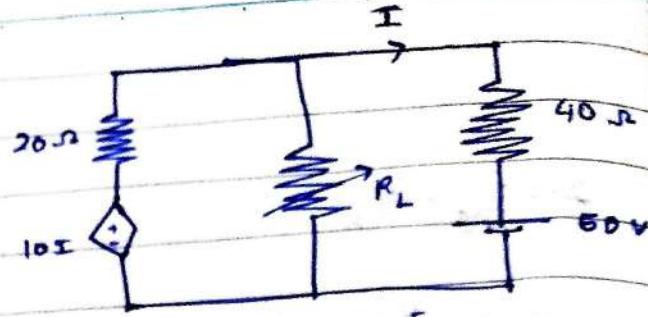


$$10I - 20I_1 = 0$$

$$I_1 = 0 \text{ A} \quad -20I_1 + 10I_2 = 0 \quad \text{if } 20\Omega$$

$$-40I_2 - 50 = 0$$

$$40I_2 = -50$$

$$I_2 = 1.25 \text{ A}$$

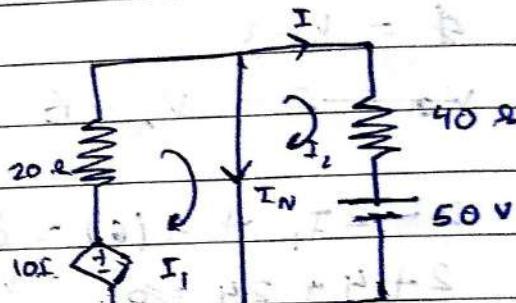

$$20I_1 = 10(1.25)$$

$$I_1 = 0.625 \text{ A}$$

$$I_N = -0.625 \text{ A}$$


$$R_{th} = \frac{V_{th}}{I_N} = \frac{10}{-0.625} = 16 \Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{10^2}{4(16)} = 1.5625 \text{ W}$$

Given

$$I_x = I_2$$

$$I_1 = 10 \text{ A}$$

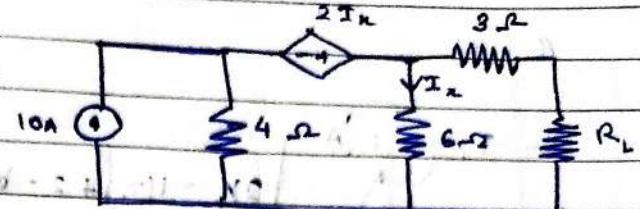

$$-4(I_2 - I_1) + 2I_x - 6I_2 = 0$$

$$-4I_2 + 4I_1 + 2I_x - 6I_2 = 0$$

$$4I_1 - 8I_2 = 0$$



$$40 = 8I_2$$

$$I_2 = 5 \text{ A}$$

$$V_{AB} = 6I_2 - 3I_2$$

$$= 6(5) - 3(5)$$

$$= 30 - 15 \text{ V}$$

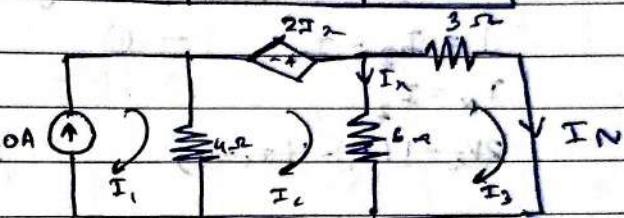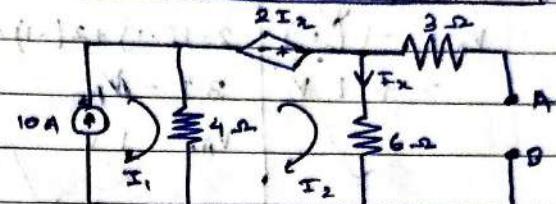

$$= 15 \text{ V}$$

$$I_3 = I_N$$

$$-4(I_2 + I_1) + 2I_x - 6(I_2 - I_3) = 0$$

$$-4I_2 + 4I_1 + 2I_2 - 6I_2 + 6I_3 = 0$$

$$4I_1 - 8I_2 + 6I_3 = 0$$

$$+ 8I_2 - 6I_3 = 40 \text{ A}$$

$$I_x = I_2 - I_3$$

$$-4I_2 + 4I_1 + 2I_2 - 2I_3 - 6I_2 + 6I_3 = 0$$

$$40 = 8I_2 - 4I_3 - i$$

$$-6(I_3 - I_2) - 3I_3 = 0$$

$$-6I_3 + 6I_2 - 3I_3 = 0$$

$$6I_2 - 9I_3 = 0$$

$$I_2 = 7.5 \text{ A}$$

$$I_3 = 5 \text{ A} = I_N$$

$$I_{\text{out}} =$$

$$R_{\text{in}} = \frac{30}{5} = 6 \text{ ohm}$$

$$P_{\text{max}} = \frac{V_{\text{th}}^2}{4R_{\text{in}}} = \frac{15^2}{4 \times 6} = 18.75 \text{ W}$$


$$= \frac{(30)^2}{4(16)}$$

$$= 37.5 \text{ W}$$

Graph theory


Current Source \Rightarrow open circuit

Voltage Source \Rightarrow straight line

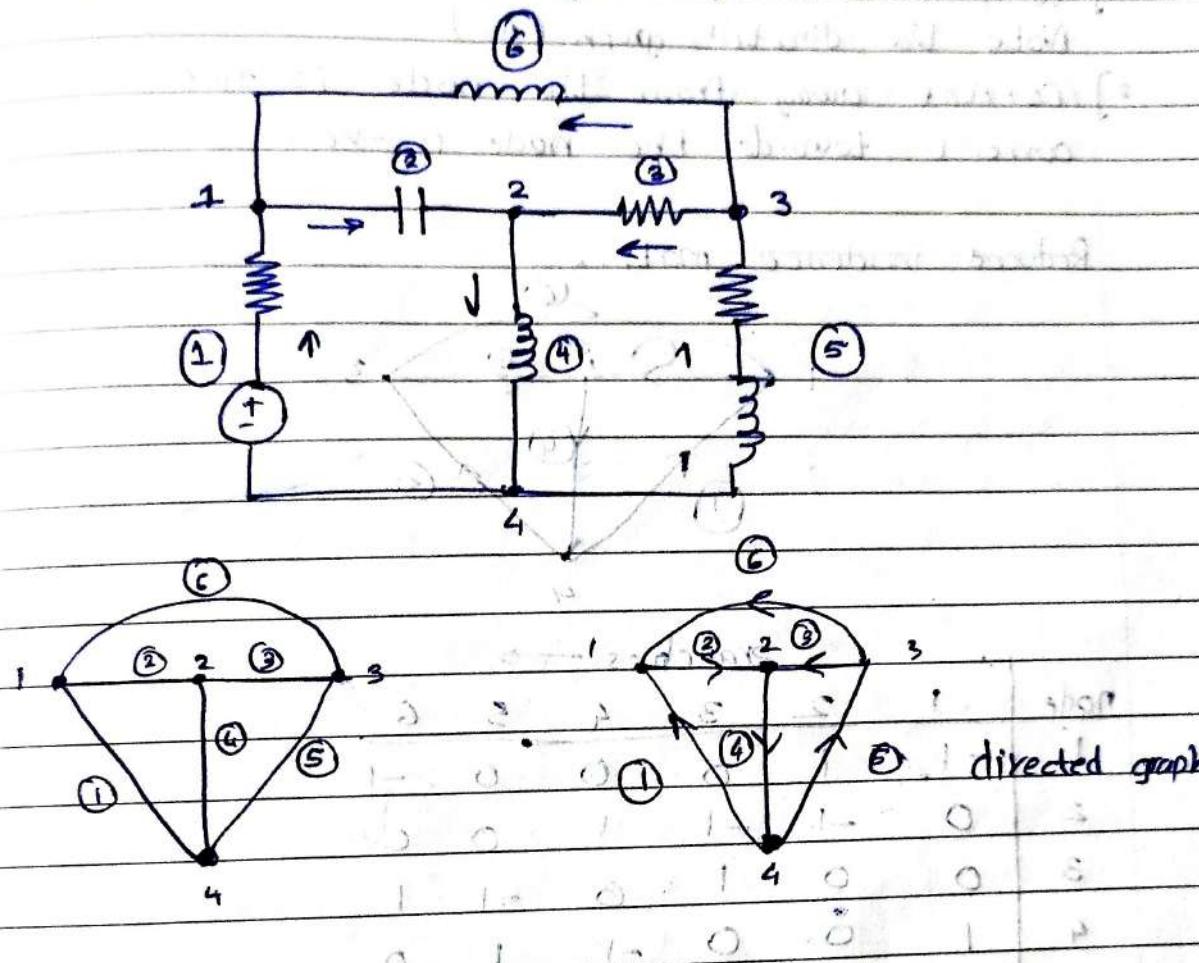

Tree: Max no. of branches should be present but they should not form a loop

Tree example:

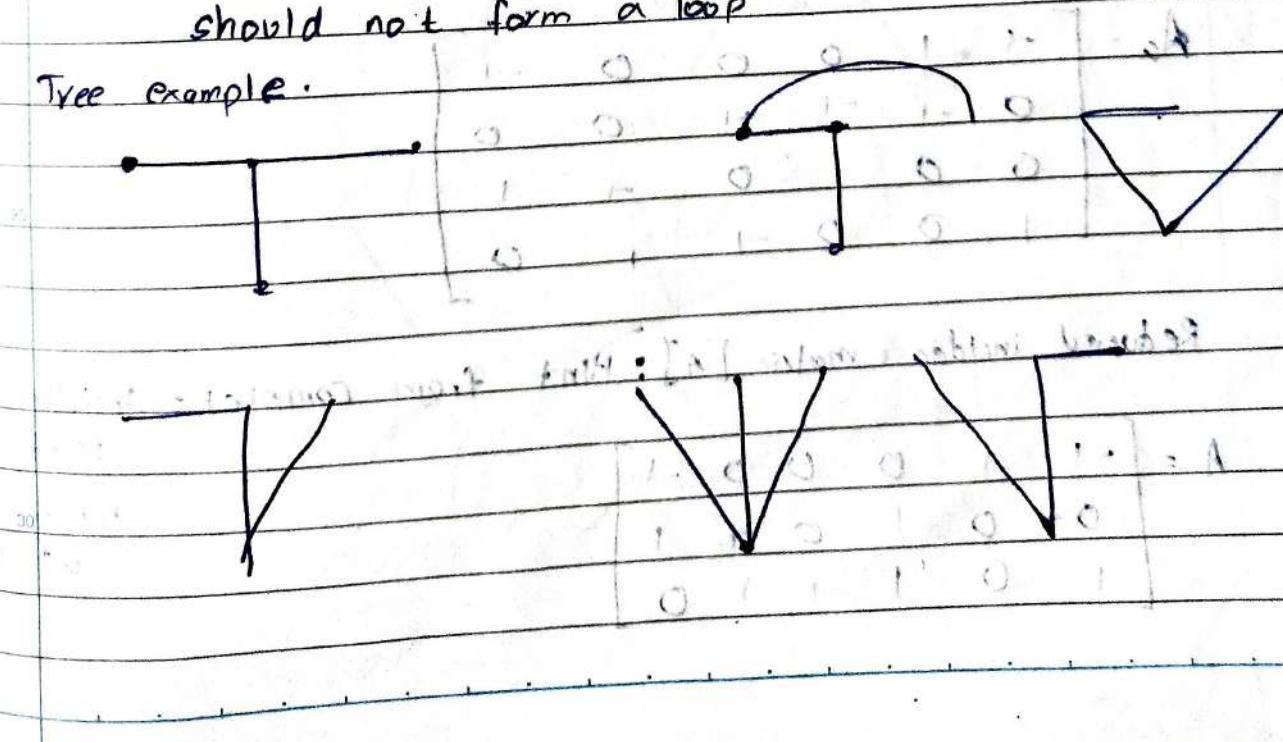


Incidence matrix

i] Complete incidence matrix

Note: Use directed graph (A_a)

ii] Current away from the node is +ve
current towards the node is -ve.

Reduced incidence matrix

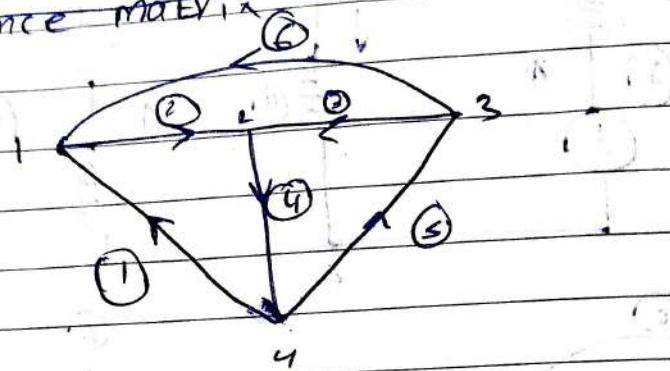

branches →

node	1	2	3	4	5	6
1	-1	1	0	0	0	-1
2	0	-1	-1	1	0	0
3	0	0	1	0	-1	1
4	1	0	0	-1	1	0

$$A_a = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 \\ 1 & 0 & 0 & -1 & 1 & 0 \end{bmatrix}$$

Reduced incidence matrix, $[A]$: Hint from complete incidence mat

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & -1 & 1 \\ 1 & 0 & 1 & -1 & 1 & 0 \end{bmatrix}$$

remove any
of them

No of possible trees $\Rightarrow |A \cdot A^T|$, if vertices are



$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 & -1 & 1 \\ 1 & 0 & 1 & -1 & 1 & 0 \end{bmatrix}$$

$$A^T = \begin{bmatrix} -1 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & -1 \\ 0 & -1 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

3×6

$$A \cdot A^T = \begin{bmatrix} 1+1+1 & -1+1+1+1 & 0 & 3 & 3 & 1+1+1 \\ -1 & 1+1+1+0 & 0+1+0 & 1+5 & 2+1+3 & -1 \\ -1 & -1 & 0+1+1+1 & 1+1 & 0+1 & 3 \end{bmatrix}$$

$$|A \cdot A^T| = 16 //$$

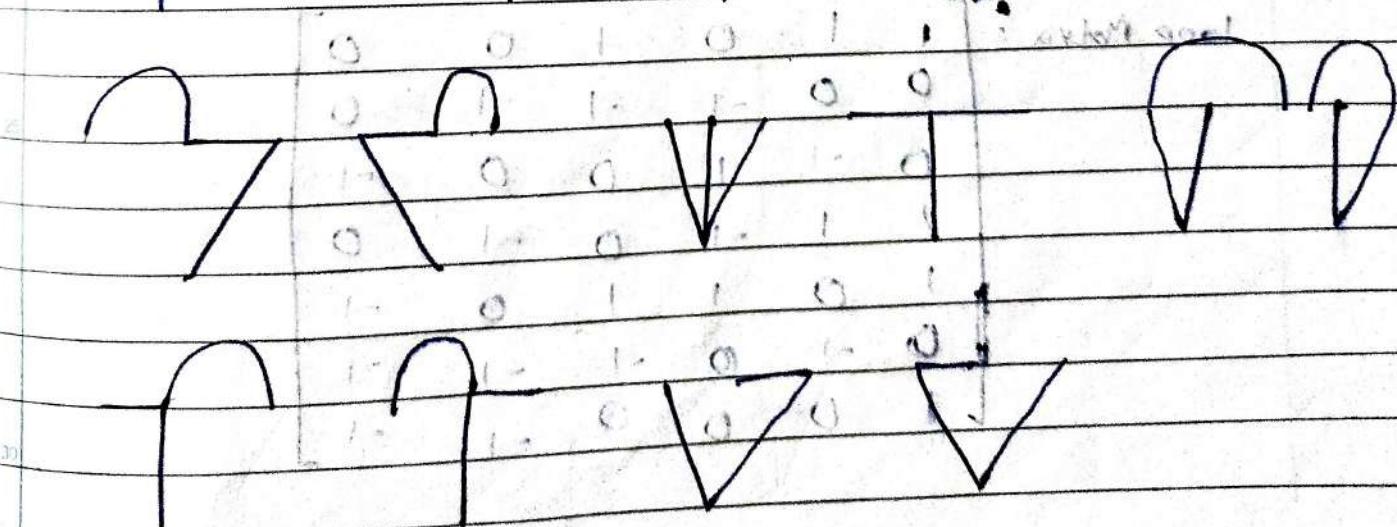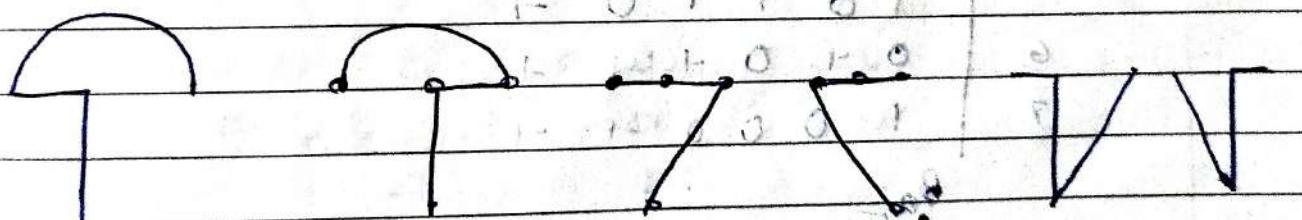

Circuit matrix
or
loop matrix (B_a) Use components / branches

Note: Use directed graph

Clockwise current = 1
Anticlockwise current = -1

loop 1: {1, 2, 4, 3}

loop 2: {3, 4, 5, 3}


loop 3: {2, 3, 6, 3}

loop 4: {1, 3, 4, 6} \rightarrow {1, 2, 3, 5}

loop 5: {2, 1, 5, 6, 3}

loop 6: {2, 4, 5, 6, 3}

loop 7: {1, 5, 6, 3}

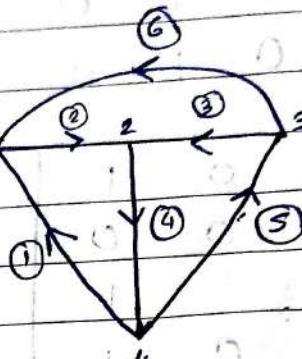

loops	1	2	3	4	5	6	7	\sum	$\sum \sum$
1	-1	1	0	1	0	0	1	-1	0
2	0	0	-1	-1	0	0	1	1	1
3	0	-1	1	0	0	0	-1		
4	+1	1	-1	0	-1	0		+1	+1
5	1	0	1	1	0	-1			
6	0	-1	0	-1	-1	-1			
7	1	0	0	0	-1	-1			

$$\text{Loop Matrix } B_a = \begin{bmatrix} 1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 & 0 \\ 0 & -1 & 1 & 0 & 0 & -1 \\ 1 & 1 & -1 & 0 & -1 & 0 \\ 1 & 0 & 1 & 1 & 0 & -1 \\ 0 & -1 & 0 & -1 & -1 & 1 \end{bmatrix}$$


Tieset Matrix (B)

Consider a tree and join rest of the branches with dotted line.

Hint: Same direction as that of the dotted is + diff direction " "


Tieset 1:

$$\{1, 2, 4\}$$

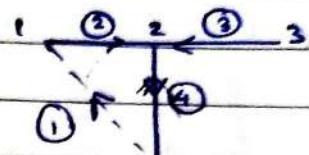


Tieset 2:

$$\{5, 3, 4\}$$

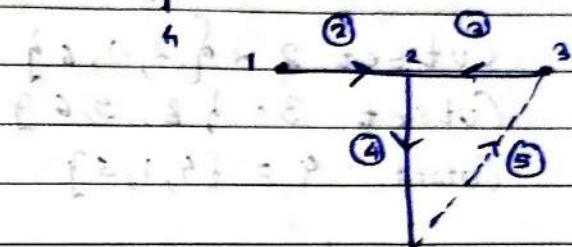

Tieset 3:

$$\{6, 2, 3\}$$

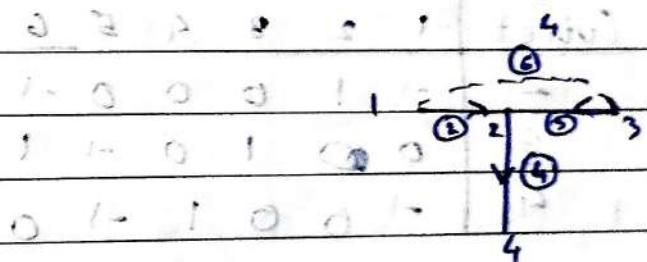

— branches →


Tieset	1	2	3	4	5	6	0	1	2	3	4
1	1	1	0	1	0	0	1	0	0	0	0
2	0	0	1	1	1	0	0	0	0	0	0
3	0	1	-1	0	0	1	0	1	0	0	0

$$B = \begin{bmatrix} 1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \end{bmatrix}$$

Cutset matrix (Q_A)

Note: Use directed graph

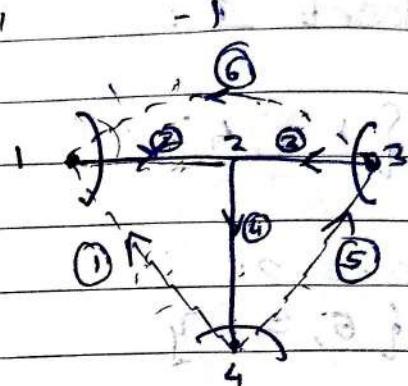- While cutting we must only cut one dark line then no restriction of cutting dotted line
- Always give a cut near the node
- Same direction as that of dark line = 1
Opposite " -1"



$$\text{Cutset } 2 = \{2, 1, 6\}$$


$$\text{Cutset } 3 = \{3, 5, 6\}$$

$$\text{Cutset } 4 = \{4, 1, 5\}$$



Cutset	1	2	3	4	5	6
2	-1	1	0	0	0	-1
3	0	0	1	0	-1	1
4	-1	0	0	1	-1	0

$$Q_A = \left[\begin{array}{cccccc|ccc}
-1 & 1 & 0 & 0 & 0 & -1 & 1 & 1 & 1 \\
0 & 0 & 1 & 0 & -1 & 1 & 0 & 1 & 1 \\
-1 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 1 \\
1 & 0 & 0 & -1 & -1 & 0 & 1 & 0 & 1
\end{array} \right]$$

$$\left[\begin{array}{cccccc|ccc}
1 & 0 & 1 & 0 & 1 & 1 & 1 & 1 & 1 \\
0 & 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 \\
1 & 0 & 0 & -1 & -1 & 0 & 1 & 0 & 1
\end{array} \right]$$

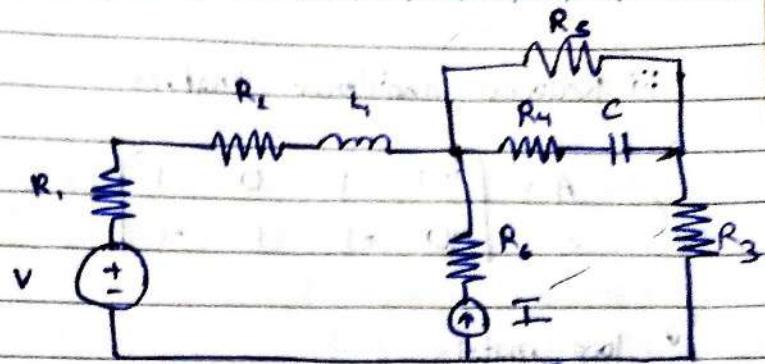

3) Incidence

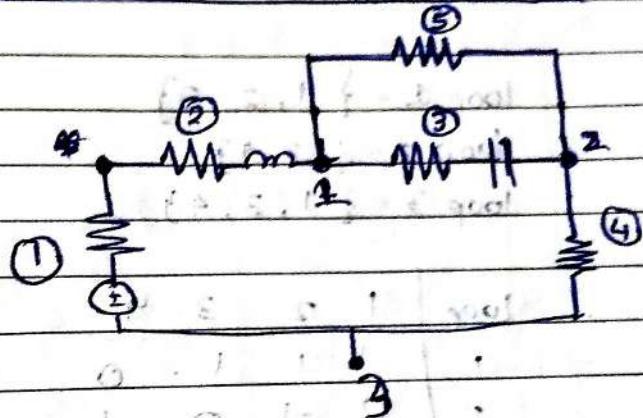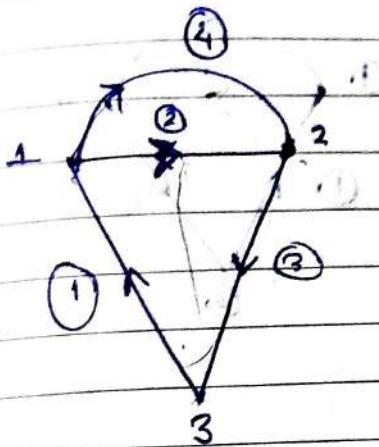

branches

node	1	2	3	4
1	-1	+1	0	+1
2	0	-1	+1	-1
3	+1	0	-1	0


$$A_a = \begin{bmatrix} -1 & 1 & 0 & 1 \\ 0 & -1 & 1 & -1 \\ +1 & 0 & -1 & 0 \end{bmatrix}$$

ii) F-cutset

$$\text{f-cutset } 2 = \{2, 1, 4\}$$


$$\text{cutset } 3 = \{3, 1\}$$

Cutset	1	2	3	4
2	-1	1	0	1
3	-1	0	1	0

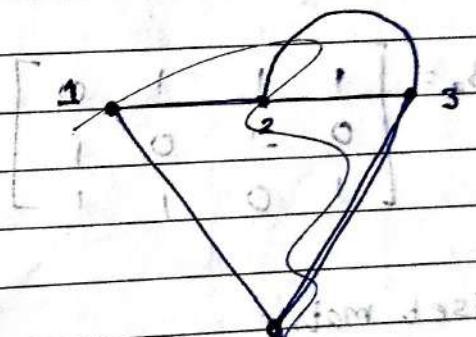

f-cutset 2 = {1, 2, 4}

cutset 3 = {1, 3}

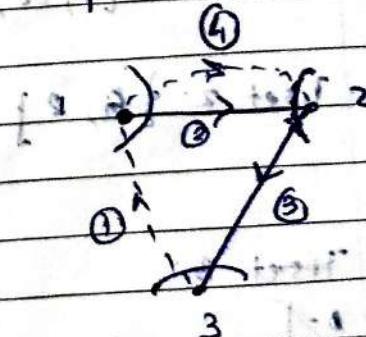

iii Reduced incidence matrix


$$A = \begin{bmatrix} -1 & 1 & 0 & 1 \\ 0 & -1 & 1 & -1 \end{bmatrix}$$

iv loop matrix

$$\text{loop 1} = \{1, 2, 3\}$$

$$\text{loop 2} = \{2, 1, 3\}$$

$$\text{loop 3} = \{1, 3, 4\}$$

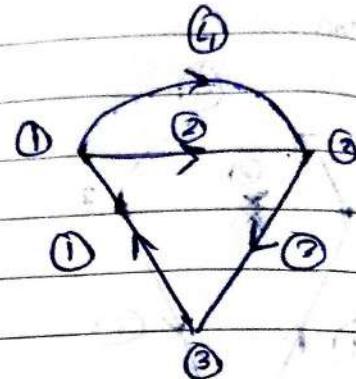

loop	1	2	3	4
1	1	1	1	0
2	0	-1	0	1
3	1	0	1	1

$$B_L = \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & -1 & 0 & 1 \\ 1 & 0 & 1 & 1 \end{bmatrix}$$


v Tiset matrix

$$\text{Tiset 1} = \{1, 2, 3\}$$

$$\text{Tiset 2} = \{1, 2\}$$

Tiset 3:

df

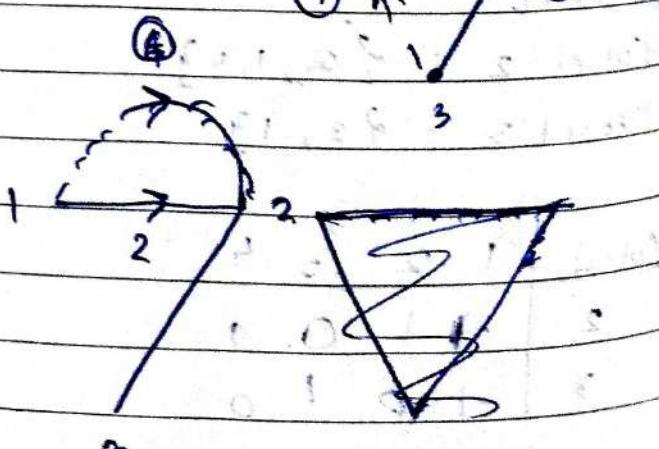

Duality \rightarrow Conversion

current
Resistance
Inductance
Branch Current
Mesh
SC

Volt
Conductance
~~Conductance~~ Capacitor
Branch voltage
Node
O.C

