

BJT amplifier (AC analysis)


- CE amplif^r
- CB amplif^r
- CC amplif^r

Cond's for an amplifier:

- ① I_{IP} slg should be small (\sim mV)
- ② BJT should be biased in "Forward-Active Mode"
- ③ Consider small slg hybrid-II model
- ④ Consider small time-varying quantities ($v_{in}(t)$, $V_{out}(t)$)

Hybrid-II model:

} *npn BJT*

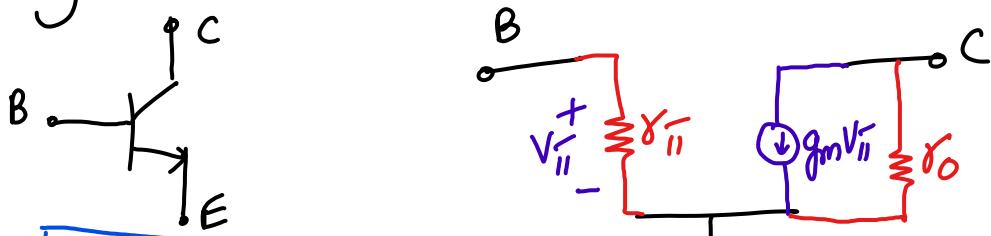


$$V_T = 26 \text{ mV}$$

at R.T
(27°C)

$$\gamma_{II} = \frac{\beta}{g_m} \quad ; \quad g_m = \frac{I_{CQ}}{V_T} \quad ; \quad \gamma_0 = \frac{V_A}{I_{CQ}}$$


VA: Early voltage

Given: β, V_A

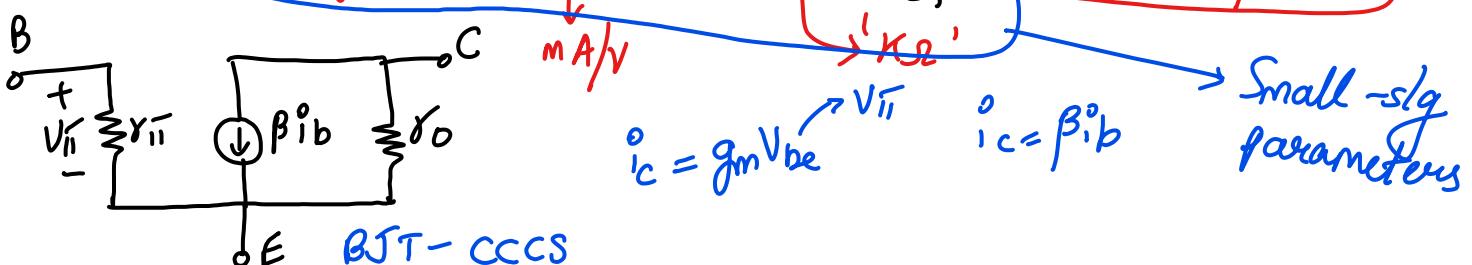


$$i_c = g_m v_{be}$$

$$i_c = \beta i_b$$

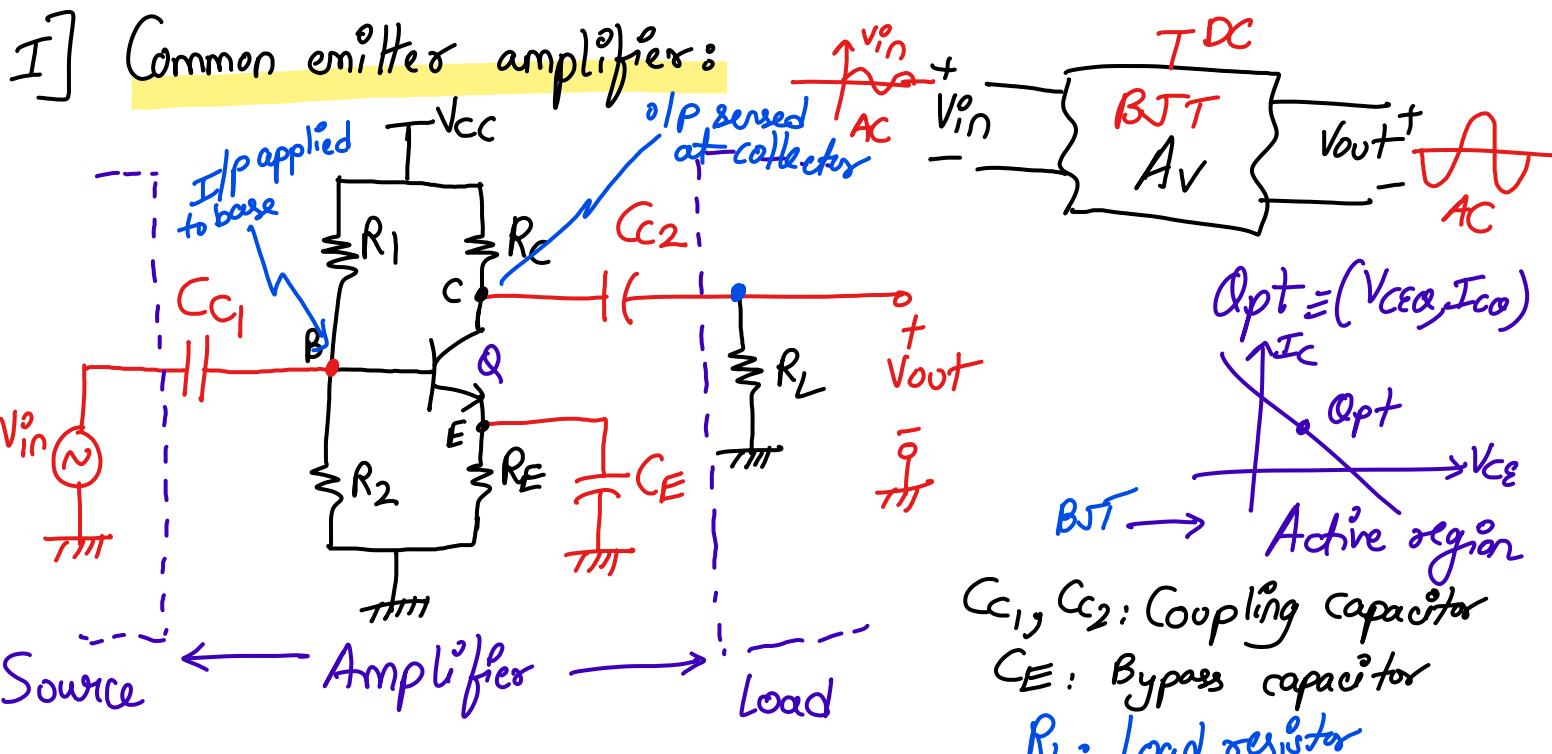


DC analysis:

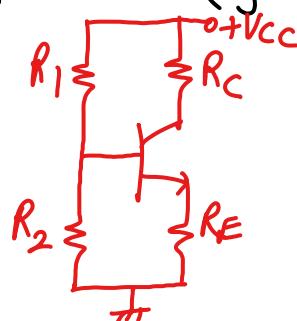→ consider all connected capacitors as open ckt ($f=0 \rightarrow X_C = \frac{1}{2\pi f C} = \infty$)




AC analysis (DC supply \rightarrow s.c.)

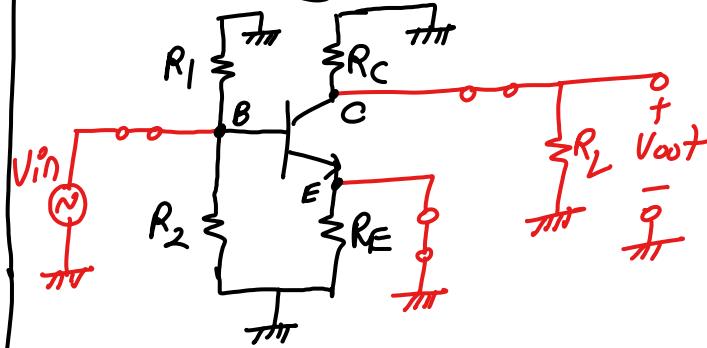→ All connected capacitors are replaced by short ckt ($f \neq 0$)



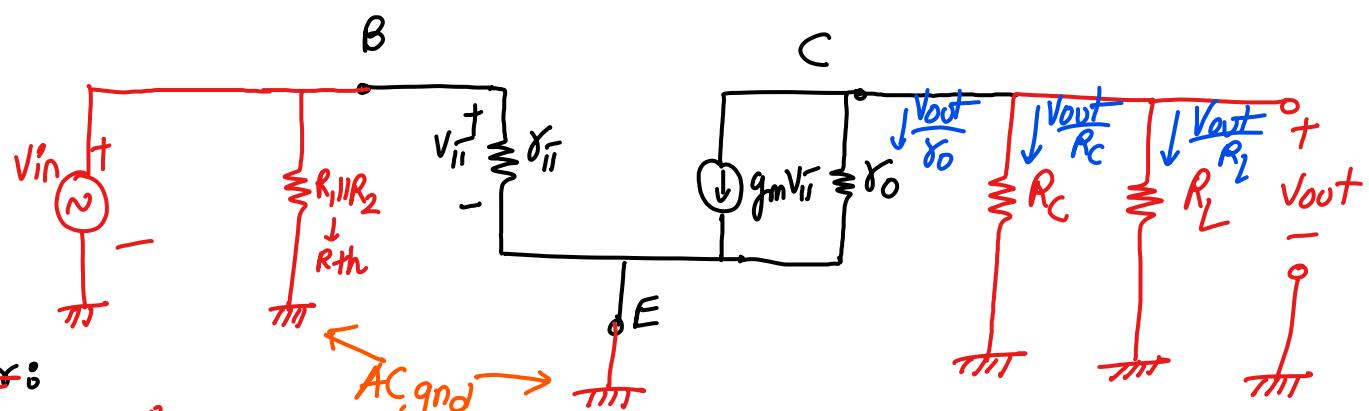→ Replace BJT by its small-sig hybrid-II model



Amplifier:

- 1) $A_v \rightarrow$ Voltage gain
- 2) R_{in}/Z_{in}
- 3) R_{out}/Z_{out}

Small-sig equivalent circuit

$$V_{ii} = V_{in}$$

BJT
gain: β
 $R_{in}: \gamma_{II}$; $R_{out} = \gamma_O$

$$\textcircled{1} \quad \text{Av: Voltage gain} ; \quad \text{Av} = \frac{V_{\text{out}}}{V_{\text{in}}}$$



Apply KCL at 'c' terminal,

$$g_m V_{\text{in}} + \frac{V_{\text{out}}}{R_0} + \frac{V_{\text{out}}}{R_C} + \frac{V_{\text{out}}}{R_L} = 0$$

$$\rightarrow g_m V_{\text{in}} = -V_{\text{out}} \left(\frac{1}{R_0} + \frac{1}{R_C} + \frac{1}{R_L} \right)$$

$$\rightarrow \boxed{\text{Av} = \frac{V_{\text{out}}}{V_{\text{in}}} = -g_m (R_0 || R_C || R_L)}$$


Voltage gain

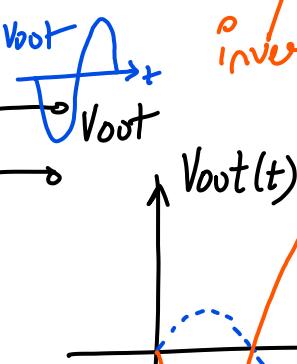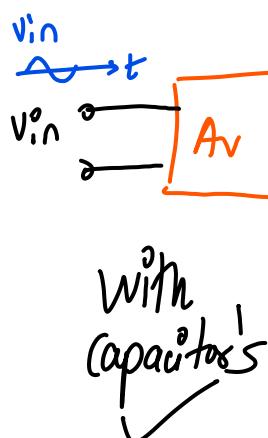




-ve sign indicates that I/P & O/P are out of phase by 180°

$\cdots \cdots V_{\text{in}}(t)$
— — — $V_{\text{out}}(t)$

w/o capacitors X

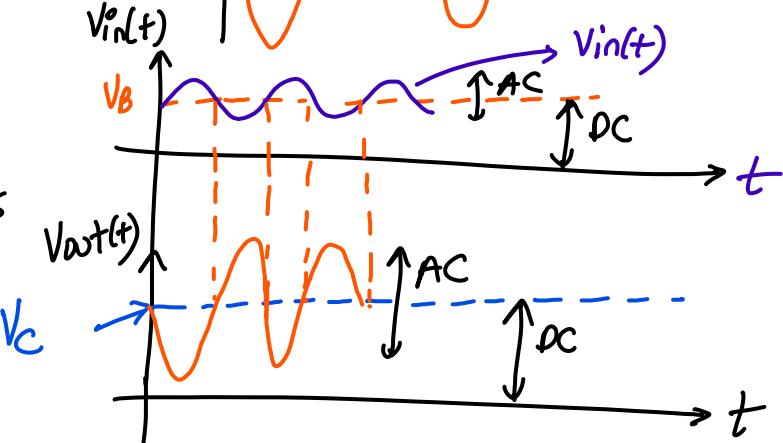

b) Input impedance:

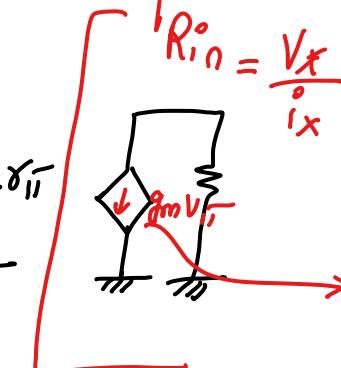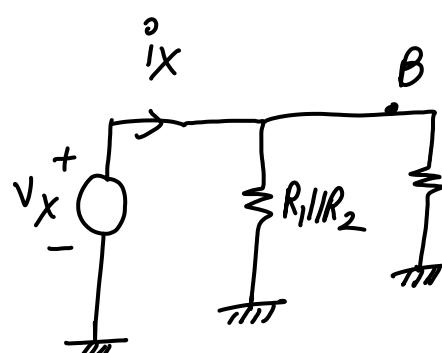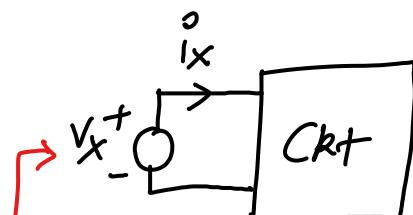

impedance offered
by $\downarrow i_x$ is ∞
current source

$$R_{\text{in}} = \frac{V_x}{i_x}$$


$$\frac{V_x}{i_x} = R_1 || R_2 || \gamma_{II}$$

$$R_{in}^o = \gamma_{II}$$

BJT

$$R_{in}^o = R_1 || R_2 || \gamma_{II} \rightarrow I/p \text{ impedance of amplifier}$$

c) O/P resistance (R_{out}):

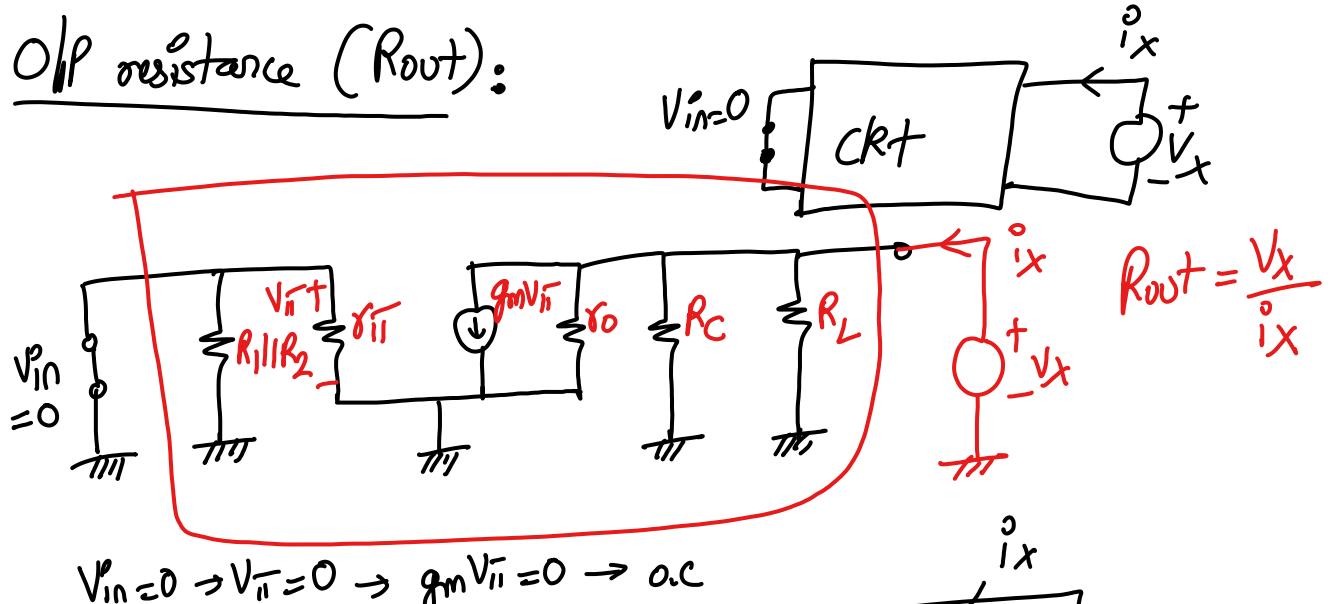

$$V_{in}=0 \rightarrow V_{II}=0 \rightarrow g_m V_{II}=0 \rightarrow o.c$$


$$\frac{V_x}{i_x} = \gamma_O || R_C || R_L$$

$$R_{out} = \gamma_O || R_C || R_L$$

O/P resistance of amplifier

BJT

$$R_{out} = \gamma_O$$

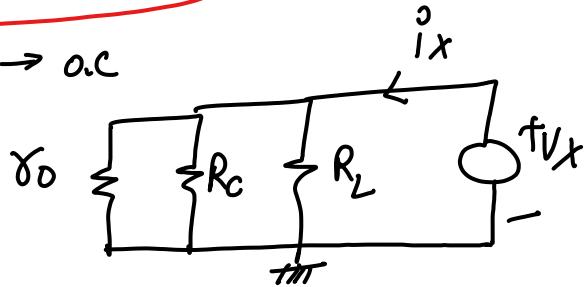

97, 80, 78, 85, 67,
44, 101, 8, 64, 2

Attendance, AEC b/c 10 (7/8/29)

