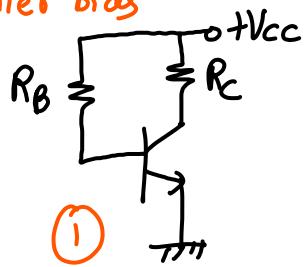



BJT Biasing ckt's:

① Fixed bias

② Emitter bias



Forward-Active mode



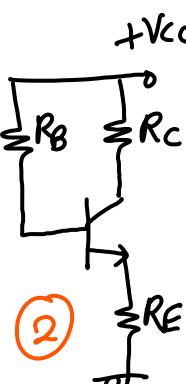
B-E J^o: F.BB-C J^o: R.B

$$\rightarrow Q_{pt} = (V_{CE0}, I_{C0})$$

DC Analysis

③ Collector to base bias

④ C to B bias with R_E

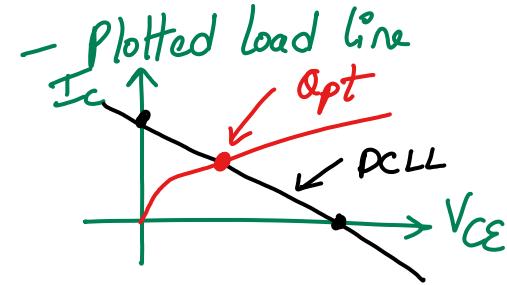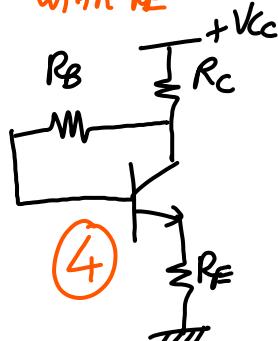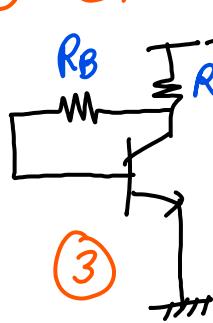


⑤ Voltage-divider biasing:



 $R_1 - R_2$ form of voltage-divider

$$V_2 = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_2 = 4.5V$$

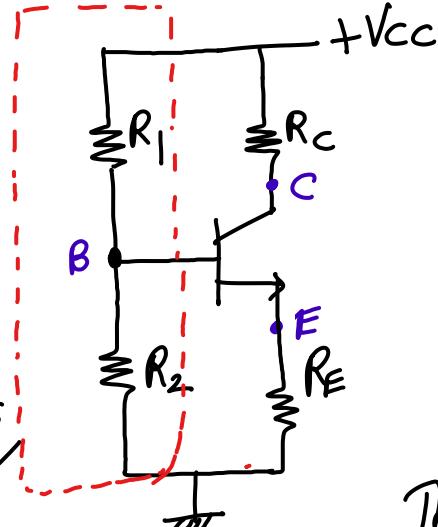

R_1 & R_2 divide the V_{CC} vtg at the base
 \downarrow
 V_{DB}

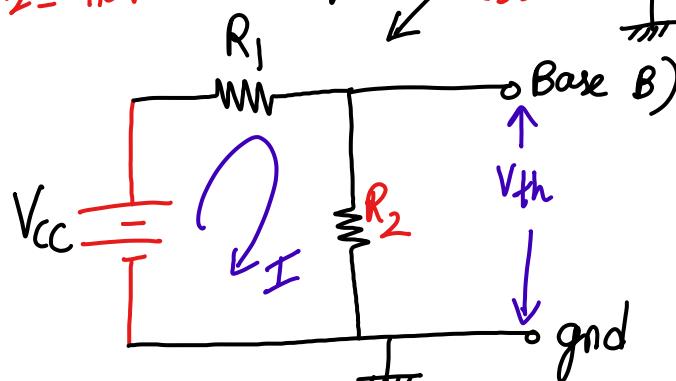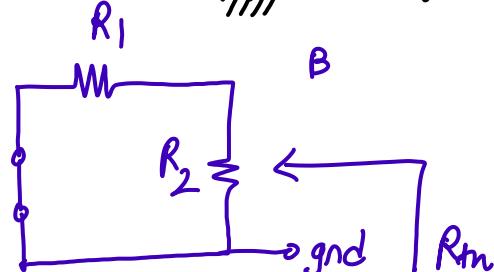 R_{th} :


Thévenin's thm at B & gnd

$$I = \frac{V_{CC}}{R_1 + R_2}$$


$$V_{th} = I R_2$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$
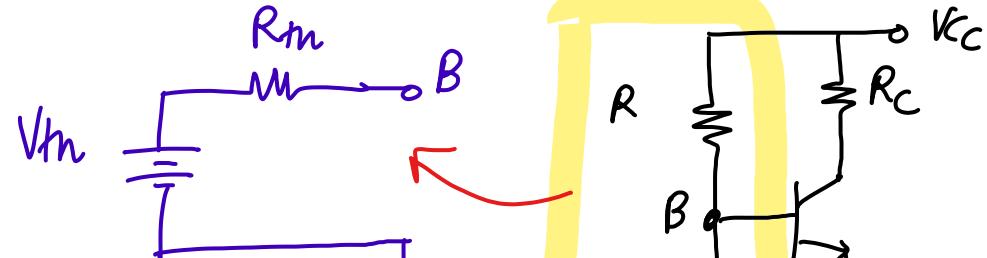
$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$



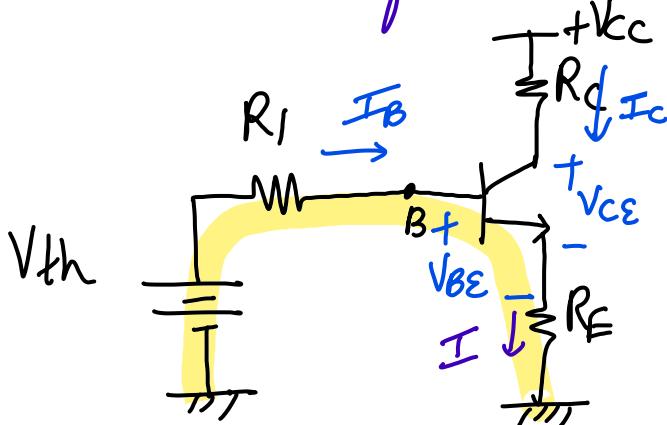Thévenin's equivalent circuit at Base of BJT



$$I_E = I_C + I_B = \beta I_B + I_B$$

$$I_E = (1 + \beta) I_B$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{cc}$$

$$R_{th} = R_1 \parallel R_2$$


KVL to I/P (B-E) loop,

$$V_{th} - I_B R_{th} - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$V_{th} - V_{BE} = I_B [R_{th} + (1 + \beta) R_E]$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E}$$

$$I_Q = \beta I_{BQ}$$

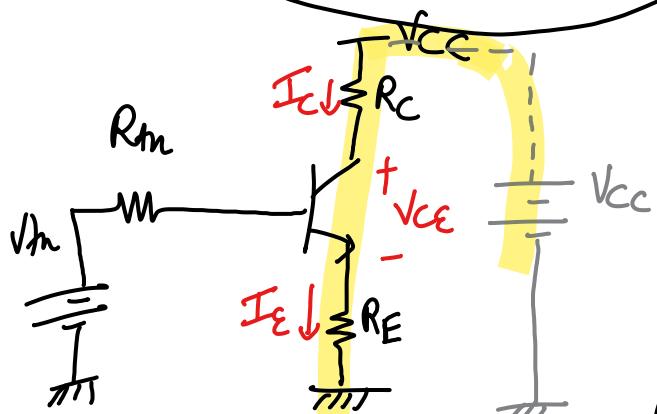

$$I \approx I_C \quad I_E = \frac{I_C}{\alpha}$$

$$I_C = \alpha I_E$$

KVL to O/P (CE) loop,

$$V_{cc} - I_C R_C - V_{CE} - I_C R_E = 0$$

$$V_{CEQ} = V_{cc} - I_C (R_C + R_E)$$

$$O_{pt} = (V_{CEQ}, I_{CQ})$$

Stability factor $S = \frac{\partial I_C}{\partial I_{CQ}} \quad ; \quad S = \frac{1 + \beta}{1 - \beta \left(\frac{\partial I_B}{\partial I_C} \right)}$

$$\frac{\partial I_B}{\partial I_C} = ? \quad \text{KVL to I/P, } V_{th} - I_B R_B - V_{BE} - (I_C + I_B) R_E = 0$$

Differentiate w.r.t I_C ,

$$0 - \frac{\partial T}{\partial I_C} R_{th} - 0 - R_E - \frac{\partial I_B}{\partial I_C} R_E = 0$$

$$-R_E = \frac{\partial I_B}{\partial I_C} (R_E + R_{th})$$

$$\frac{\partial I_B}{\partial I_C} = -\frac{R_E}{R_E + R_{th}}$$



$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_E + R_{th}} \right)}$$

V_{DB}

"Best biasing technique"

Numerical 8: Find V_{CEQ} , I_{CQ} and S for the ckt shown below. Also plot DC load line & locate Opt

Solution:

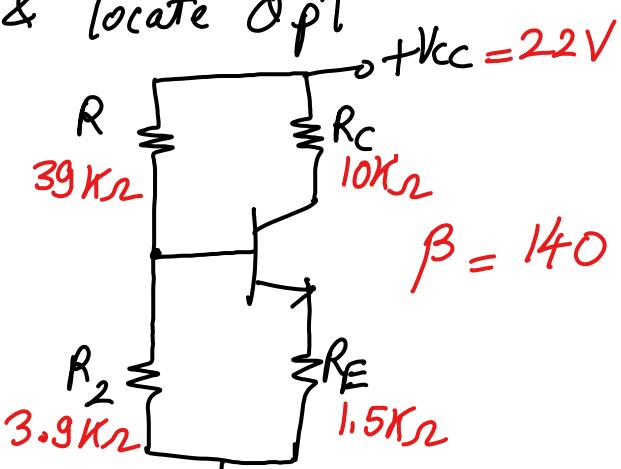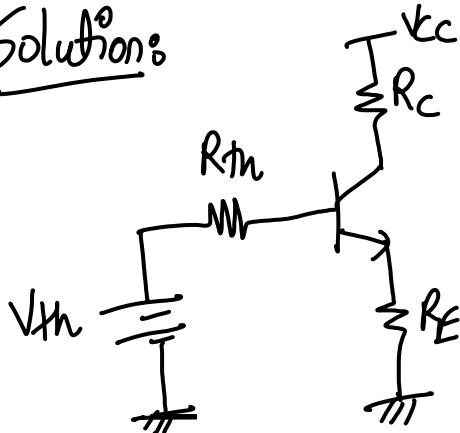

$$\textcircled{1} \quad V_{th} = \left(\frac{R_2}{R_1 + R_2} \right) V_{cc} = \left(\frac{3.9}{3.9 + 39} \right) 22 = 2V$$

$$\textcircled{2} \quad R_{th} = R_1 // R_2 = 39k\Omega // 3.9k\Omega = 3.545k\Omega$$

$$\textcircled{3} \quad I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{2 - 0.7}{3.545 \times 10^3 + 140 \times 1.5 \times 10^3} \quad \begin{matrix} V_{BE} = 0.7V \\ (\text{Assume}) \end{matrix}$$

$$I_{BQ} = \underline{6.04 \mu A}$$

$$\textcircled{4} \quad I_{CQ} = \beta I_{BQ} = 140 \times 6.04 \times 10^{-6} = 0.846mA$$

$$\textcircled{5} \quad V_{CEQ} = V_{cc} - I_C (R_C + R_E) = 22 - 0.846 \times 10^3 (10 + 1.5) \times 10^3$$

$$V_{CEQ} = \underline{12.27V}$$

$$\textcircled{6} \quad S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_{th} + R_E} \right)} = \frac{140}{1 + 140 \times \left(\frac{1.5}{3.545 + 1.5} \right)} = \underline{3.308}$$


$$S = \frac{\partial I_C}{\partial I_{CO}} \rightarrow \text{Lesser the value of } S \rightarrow \text{better is the stability of the circuit}$$

Plotting of DC load line:



$$V_{CEQ} = V_{CE} - I_{CQ}(R_C + R_E) \rightarrow \text{load line eq}^A$$

$$a) \text{ Put } I_{CQ} = 0 \rightarrow V_{CEQ} = V_{CC} \rightarrow (V_{CC}, 0)$$

$$b) \text{ Put } V_{CEQ} = 0 \rightarrow I_{CQ} = \frac{V_{CC}}{R_S + R_E} \rightarrow \left(0, \frac{V_{CC}}{R_S + R_E} \right)$$

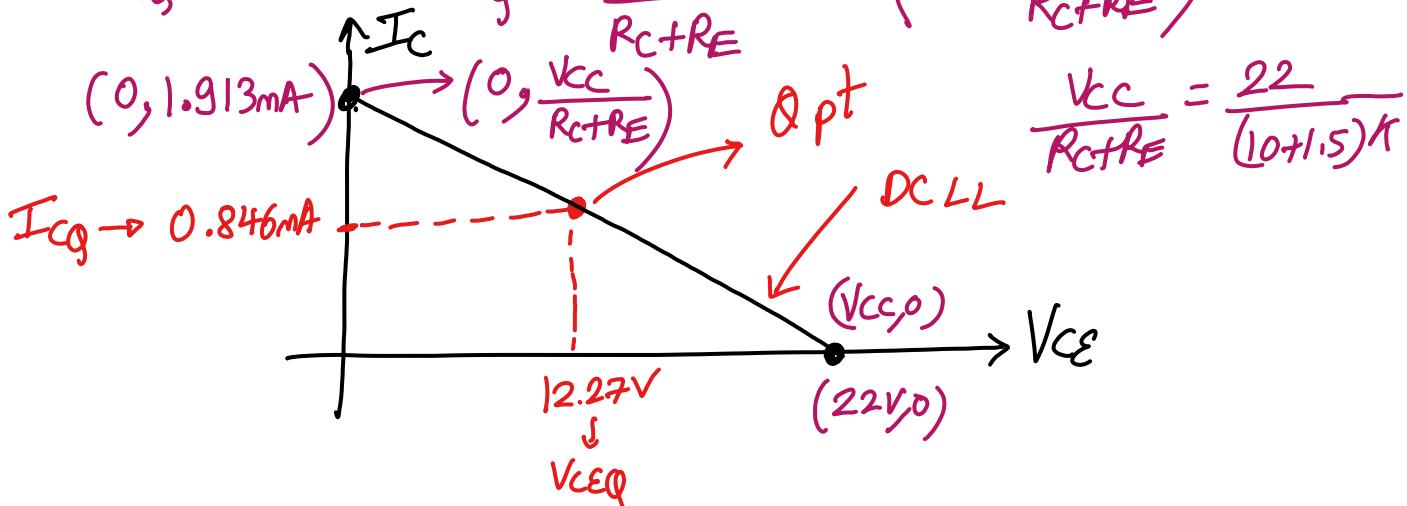

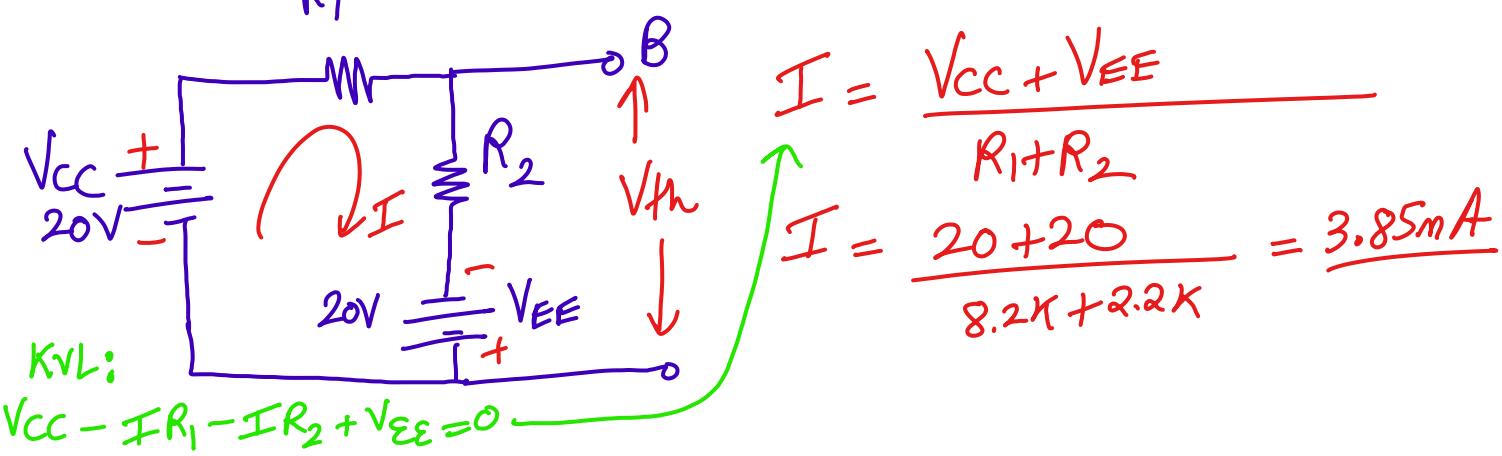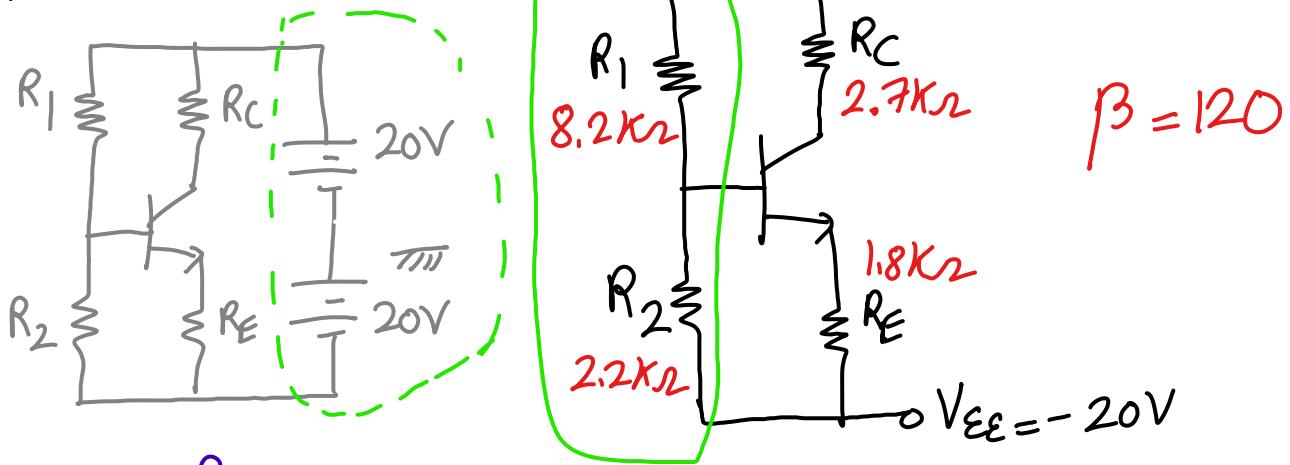Numerical 9: Find V_{CEQ} , V_C , V_B , and I_{CQ} for circuit shown below:



$$V_{th} = I R_2 - V_{EE} = 3.85 \times 10^{-3} \times 2.2 \times 10^3 - 20$$

$$V_{th} = -11.53V$$

$$R_m = R_1 \parallel R_2 = 8.2k \parallel 2.2k_2 = 1.73k_2$$


7, 85, 25, 24, 38, 72,
45, 33, 11, 22, 44, 67,
41, 6, 26, 8, 50, 64,
40, 42, 39

Attendance (AEC lec 8)
(4/8/23)

$$V_{BE(on)} = 0.7V$$

assume

$$I_E = (1+\beta) I_B$$

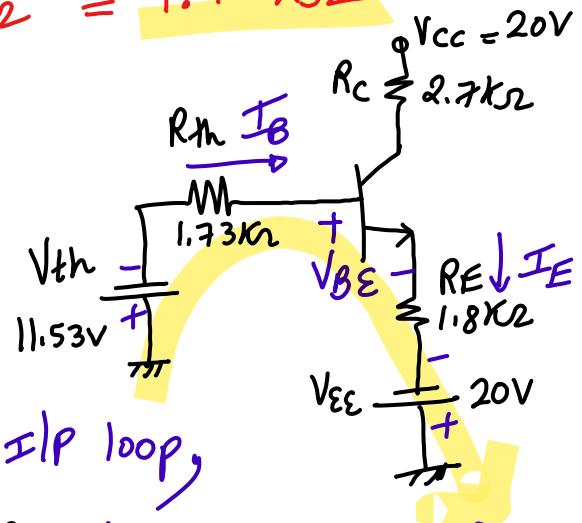

→ KVL to I/P loop,

$$-V_{th} - I_B R_m - V_{BE} - I_E R_E + V_{EE} = 0$$

$$\text{i.e. } -11.53 - I_B R_m - V_{BE} - (1+\beta) I_B R_E + \frac{20}{V_{EE}} = 0$$

$$I_B = \frac{V_{EE} - V_{th} - V_{BE}}{R_m + (1+\beta) R_E}$$

$$\text{i.e. } I_{BQ} = \frac{20 - 11.53 - 0.7}{1.73 \times 10^3 + 121 \times 1.8 \times 10^3}$$

$$\text{i.e. } I_{BQ} = 35.39 \mu A$$

$$\rightarrow I_{CQ} = \beta I_{BQ} = 120 \times \frac{35.39 \times 10^{-6}}{1.8 \times 10^3} = 4.25 \text{ mA}$$


KVL to o/p loop,

$$V_{cc} - I_c R_c - V_{CE} - I_E R_E + V_{EE} = 0$$

$$V_{CEQ} = V_{cc} + V_{EE} - I_c (R_c + R_E) \quad I_E \approx I_c$$

$$V_{CEQ} = 20 + 20 - 4.25 \times 10^3 (2.7 + 1.8) \times 10^3$$

$$V_{CEQ} = 20.875V$$

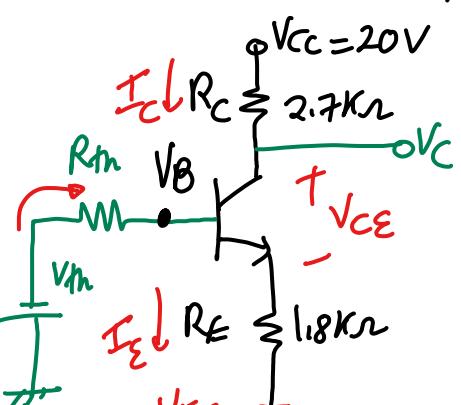

$$I_E \approx I_c$$

$$V_B = -V_{th} - I_B R_m$$

$$\rightarrow I_B = \frac{-V_{th} - V_B}{R_m}$$

$$I_B R_m = -V_{th} - V_B$$

$$V_B = -11.53 - 35.39 \times 10^{-6} \times 1.73 \times 10^3 \Rightarrow V_B = -11.59V$$

$$\rightarrow I_c = \frac{V_{cc} - V_c}{R_c} \rightarrow V_c = V_{cc} - I_c R_c$$

$$V_c = 20 - 4.25 \times 10^3 \times 2.7 \times 10^3$$

$$V_c = 8.53V$$

—X—

