
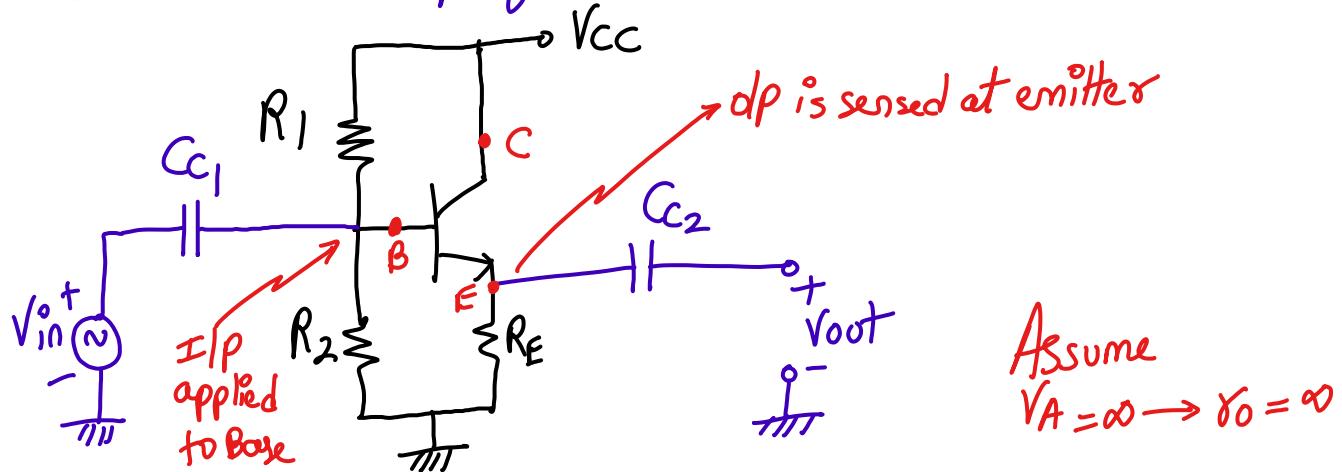


- Module 1.3 : Hybrid- π model, 1) CE ampl π (Av, Rin, Rout)
 2) CE ampl π w/o C_E (-1t)
 3) - π - Numerical: Av, Rin, Rout
 4) CB ampl π (Av, Rin, Rout)
 Numerical

Common collector amplifier:

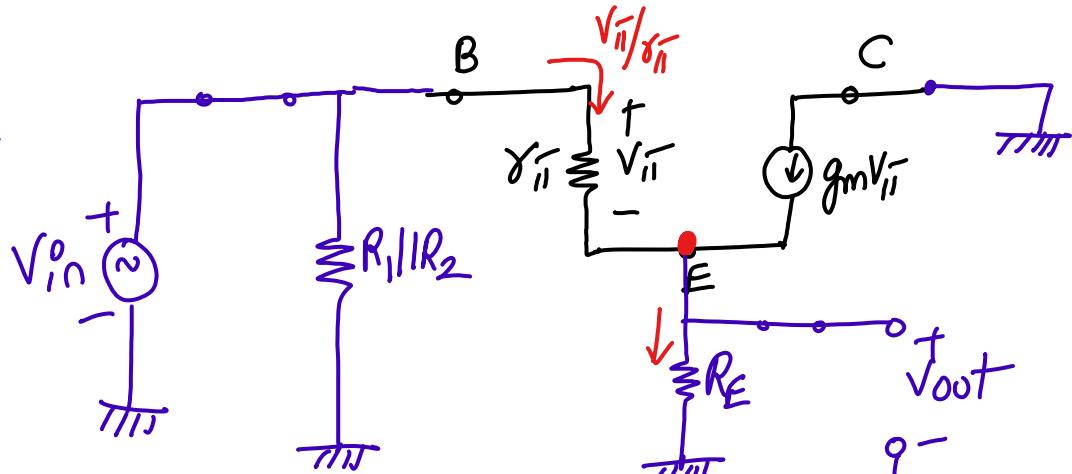


Av ✓
 R_{in} ✓
 R_{out} ✓



Small-signal equivalent ckt for CC ampl π

For Av, Rin and Rout derivations are given in AEC Lec 13 markings.pdf

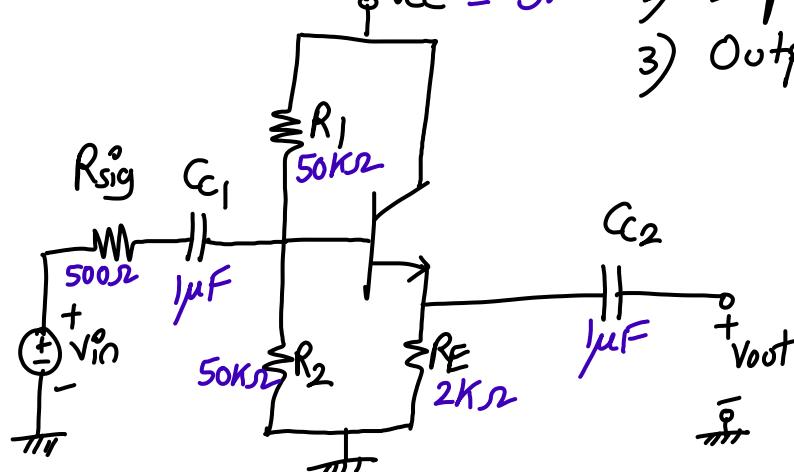Numerical 14: Determine 1) Small-sig voltage gain
 2) Input resistance
 3) Output resistance





$$\beta = 100$$

$$V_A = 80V$$

$$V_{BE(on)} = 0.7V$$

Solution: ① $I_{CQ} \rightarrow$ ② $\left(\frac{V_{th}}{R_{in}} \right) \left(\frac{V_A}{\beta R_{in}} \right) \left(\frac{R_E}{R_{out}} \right)$

② DC analysis:

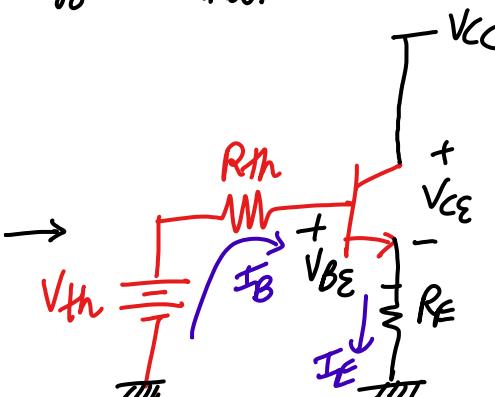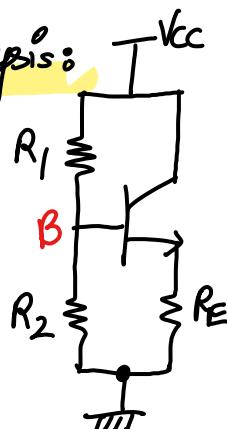

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{cc} = 2.5V$$

$$R_{th} = R_1 // R_2 = 25k\Omega$$

Apply KVL to B-E loop, $V_{th} - I_B R_{th} - V_{BE} - (1 + \beta) I_B R_E = 0$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{2.5V - 0.7V}{25k\Omega + 101 \cdot 2k\Omega} = 7.93\mu A$$


$$I_{CQ} = \beta I_{BQ} = 100 \times 7.93\mu A = 0.793mA$$

$$② g_m = \frac{I_{CQ}}{V_T} = \frac{0.793 \times 10^{-3}}{26 \times 10^{-3}} = 30.5 \frac{mA}{V} \quad V_T = 26mV$$

$$\gamma_{II} = \frac{\beta}{g_m} = \frac{100 \times 10^3}{30.5} = 3.279k\Omega$$

$$\gamma_0 = \frac{V_A}{I_{CQ}} = \frac{80}{0.793 \times 10^{-3}} = 100.88k\Omega$$

③ Small-sig equivalent ckt:

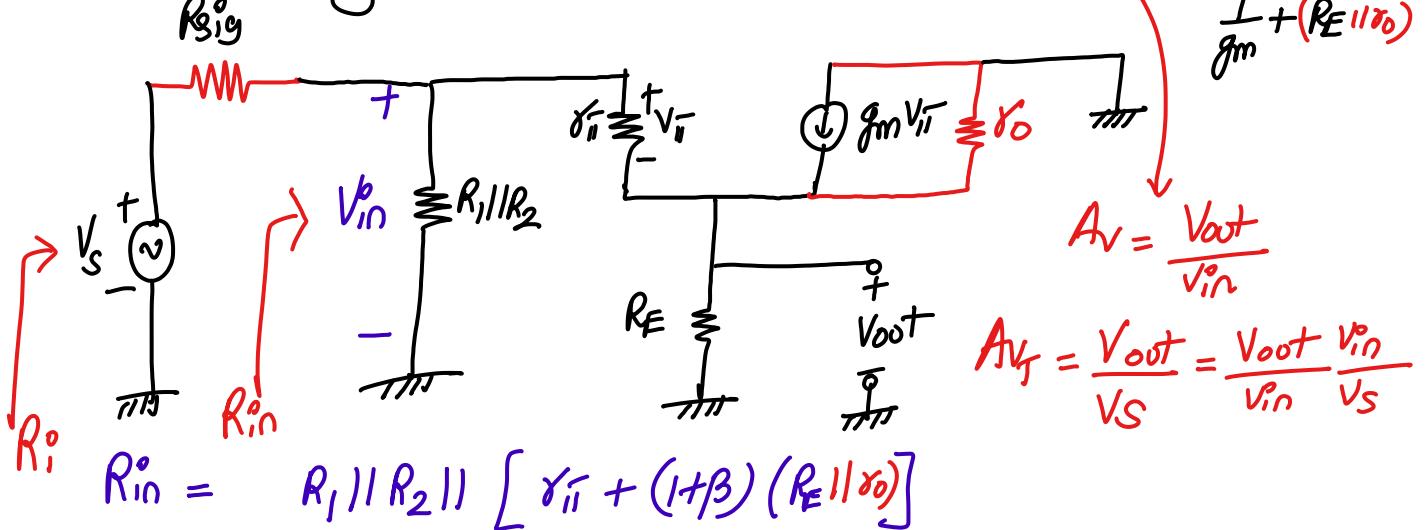

$$A_V = \frac{(R_E || r_o)}{\frac{1}{g_m} + (R_E || r_o)}$$

$$A_V = \frac{V_{out}}{V_{in}}$$

$$A_{V_T} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \frac{V_{in}}{V_s}$$

$$R_i^o = R_1 || R_2 || [r_{pi} + (1+\beta)(R_E || r_o)]$$

$$r_{pi} || R_E = 100.88\text{K} || 2\text{K} = 1.96\text{K}_2$$

$$r_{pi} + (1+\beta)(r_{pi} || R_E) = 201.24\text{K}_2$$

$$R_1 || R_2 || 201.24\text{K}_2 = 25\text{K}_2 || 201.24\text{K} = \underline{22.24\text{K}_2} (R_i^o)$$

$$R_i^o = R_{sig} + R_i^o = 500\text{S} + 22.24\text{K}_2 = \underline{22.74\text{K}_2}$$

$$R_{out}^+ = \frac{1}{g_m} || R_E || r_o$$

$$\frac{1}{g_m} = \frac{1}{30.5 \times 10^{-3}} = 32.78$$

$$R_{out}^+ = 32.78 || 2\text{K} || 100.88\text{K}_2$$

$$R_{out}^+ = 32.24\text{S} \quad \text{"Low"}$$

$$A_{V_T} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \frac{V_{in}}{V_s}$$


$$\rightarrow \frac{V_{out}}{V_{in}} = A_V = \frac{(R_E || r_o)}{\frac{1}{g_m} + (R_E || r_o)}$$

$$R_E || r_o = 2\text{K} || 100.88\text{K}$$

$$R_E || r_o = 1.96\text{K}_2$$

$$\rightarrow A_V = \frac{V_{out}}{V_{in}} = \frac{1.96\text{K}}{32.78 + 1.96\text{K}}$$

$$\underline{A_V = 0.9835}$$

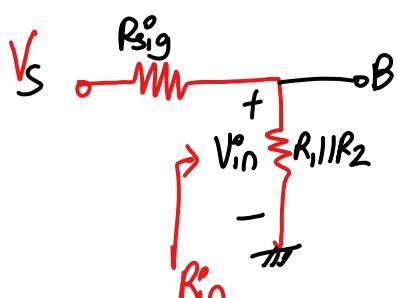

$$\frac{V_{in}}{V_s} = \frac{R_i^o}{R_i^o + R_{sig}}$$

$$\frac{V_{in}}{V_s} = \frac{22.24\text{K}}{22.24\text{K} + 500} = \underline{0.978}$$

$$A_{V_T} = \frac{V_{in}}{V_s} \times A_V = 0.978 \times 0.9835$$

$$Av_T = 0.962$$

—X—

CE, CB, CC amplifier comparison is given in AEC Lec 13_markings.pdf

24, 25, 30, 11, 72, 16,
67, 85, 97, 50, 54, 61,
41, 42, 69, 46, 58, 80,
78, 100

