

AEC lecture: Constant Current Sources


Topics Covered: Need of constant current sources, MOSFET current sources Basic two transistor MOSFET current mirror, three transistor MOSFET current mirror

Module or sub-module covered: 5.2

Constant Current Sources

○ Intro: To understand current sources, let's first understand current amplifier's & its requirements.

○ So, far we have discussed in majority on only voltage sources and voltage amplifiers.

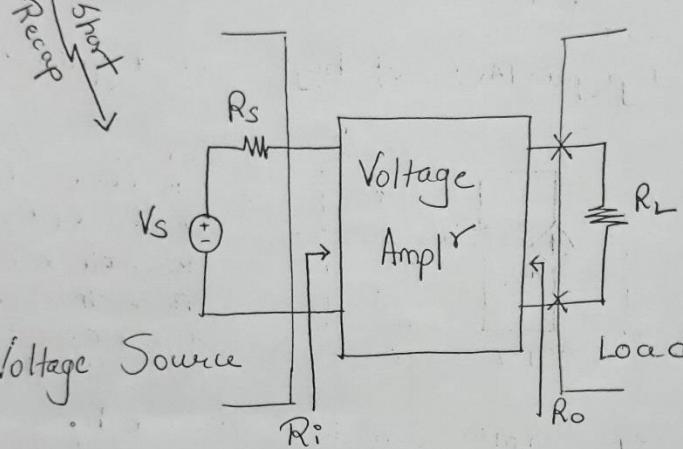○ 

where,
 $R_s \rightarrow$ internal source resistance

○ We know following w.r.t voltage ampl' that,

- 1) Its IIP impedance should be high (R_i)
- 2) Its OLP impedance should be low (R_o)

○ Requirements for voltage source, is

- 1) Its source resistance (internal) should be v. low
ie $R_s \ll R_i$ → so that entire source voltage (V_s) reach amplifier IIP and to prevent loading effect


○ Load requirement:-

- 1) OLP impedance (R_o) of amplifier should be low
ie $R_o \ll R_L$ → so that entire olp reaches Load (R_L)


Concept:

• Current

Amplifiers:-

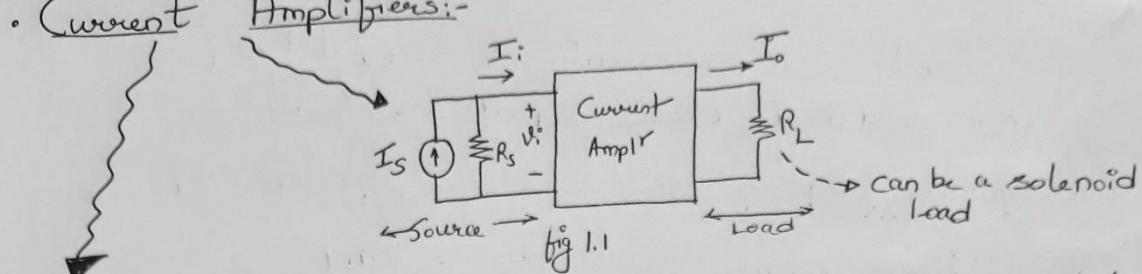

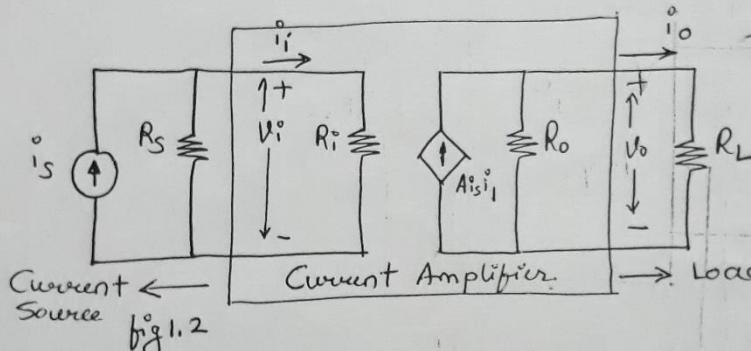- Its o/p current (I_o) is proportional to its IIP current (I_i)
- Its IIP is a "Current Source".
- Provides modest voltage gain (A_v) but high current gain (A_i)



where,
 R_L → Load resistance
 A_i → current gain.
 R_i → IIP resistance
 R_o → o/p resistance
 $A_i i_i$ → current-controlled current source

- O/P current (I_o) of the ampl'r can be obtained by using current-divider rule (CDR),

$$I_o = A_i i_i \left(\frac{R_o}{R_o + R_L} \right) \quad \text{--- (1)}$$

From (1), we see that $R_o \gg R_L \rightarrow$ so that max current (I_o) flows thr' the load

Also, o/p current i_o of the ampl'r is related to

s/g source current i_s by CDR,

$$i_i = \left(\frac{R_s}{R_s + R_i} \right) i_s \quad \text{--- (2)}$$

From (2), if $R_i \ll R_s$, then $i_i = i_s$, i.e entire source current reaches IIP of ampl'r.


From (1) & (2), the requirements of current Amplifier are

- 1) $R_i \ll R_s$
- 2) $R_o \gg R_L$

If these conditions are met, there will be no Loading effect.

In summary, an ideal current amplifier should have $R_o \rightarrow \infty$ & $R_i \rightarrow 0$, so that there is no reduction in the current gain.

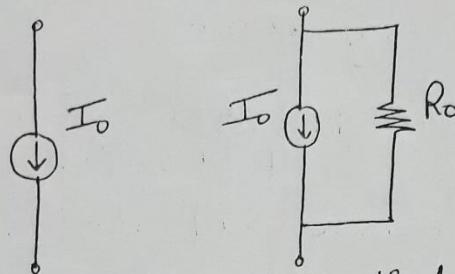From fig 1.2, it is evident that a current source should very high O/P resistance



where,
 R_o - internal current source resistance (or O/P resistance of current source).


fig 1.3 a) Ideal current source ($R_o \rightarrow \infty$)

b) Practical current source. ($R_o \rightarrow v.h$)

→ An ideal current source should have constant current and a v. large O/P resistance ($R_o \rightarrow \infty$).

Why use Current Source's ?

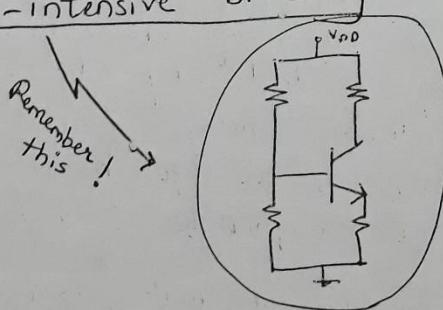1) Current-source biasing technique eliminates the need for resistor-intensive biasing used up to this point.



2) Current-source are used for biasing transistor's in Integrated circuits.

INDERJIT SINGH

Let's justify points (1) and (2),

- Biasing techniques for FET and BJT amplifiers employing voltage divider resistor networks can be used for discrete circuits, it is **NOT** suitable for integrated circuits.

Because of the following reasons:-

- 1) Resistors occupy large areas on an integrated circuit (IC) compared to transistors.
- ∴ A resistor-intensive ckt would necessitate a large chip area.
- 2) Transistors can easily be fabricated in ICs with matched or identical parameters (which may not be possible in discrete circuits).

Let's consider another justification for using current sources.

- Why we do DC biasing in BJTs (let's say):
- a) to turn the device on.
 - b) to place Q-point in region of characteristics where device operates most linearly so that any changes in the I_{IP} source causes a proportional change in the o/p signal.
 - c) ckt elements are selected so as to bias C-B & E-B Jⁿ of BJT in appropriate magnitude & polarity.
 - d) Since B-E Jⁿ behaves like a diode, transistor needs a B-E voltage V_{BE} of 0.7V to conduct.
INVERSE BIAS If we apply more than 0.7V, then transistor will be damaged due to excessive current.
 - f) Hence, resistors (R_C, R_B, R_E) are used to limit the transistor currents (I_B, I_C, I_E).

- Recollect that voltage gain (A_v) of a CE amplifier was $A_v = -g_m R_C$ \rightarrow small-signal mid-band voltage gain (with CE, w/o R_C)

In order to \uparrow the value of A_v , we need to \uparrow R_C .

But \uparrow R_C will lead to more power dissipation or loss

So replace R_C
by a current source

A current source
has a high o/p
resistance

Thereby, producing a
high A_v .

- Example:


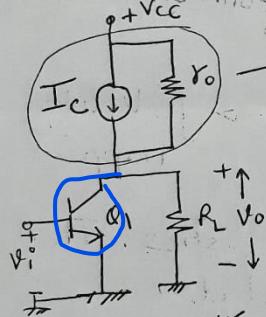


Fig. 1.3 a) CE amplifier

current source \rightarrow I_c flows out of current source into Q_1

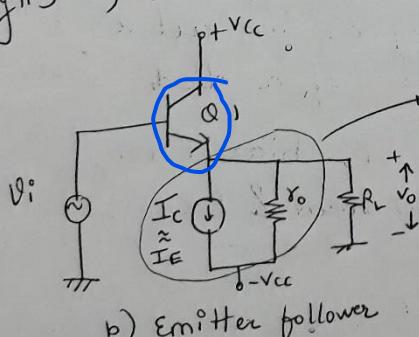Q1 is a MOSFET

This type of current source is referred to as "Sourcing Current source".



b) Emitter follower

current source \rightarrow Source current flows from Q_1 into the current source

This type of current source is referred to as "Sinking Current source".

fig. 1.3 Amplifier, with a biasing current source.

INDERJIT SINGH

Need of Constant current sources:

07


- For increasing CMRR in case of diffamp's, either emitter or source resistance (R_E or R_S) has to increase which has the following problems.
 - 1) It is very difficult to fabricate very large resistance values in Integrated Circuits (ICs) since $R = \frac{S(L)}{A}$, where L rises if R is required of high value.
 - 2) Any rise in R_E or R_S will affect or change Q point (I_{CQ} or I_{DQ}).
 - 3) In order to keep Q point constant for large value of R_E or R_S , very large negative power supplies ($-V_{EE}$ or $-V_{SS}$) are required.
 - 4) Such a large value of R_E or R_S leads to very high power dissipation \Rightarrow means loss of dc power.
- Hence for all practical diffamp's applications, the source or emitter resistance (R_E or R_S) are replaced by a constant current source, which only use value of R_E or R_S electrically, not physically at the same time providing constant bias current (I_{CQ} or I_{DQ}).
- This is possible becoz, o/p resistance (R_o) of current source is very high.
- This explains the need of CCS in diffamp.

INDERJIT SINGH

INDERJITSINGH

→ Diffamp using Constant current source

They will be MOSFETs

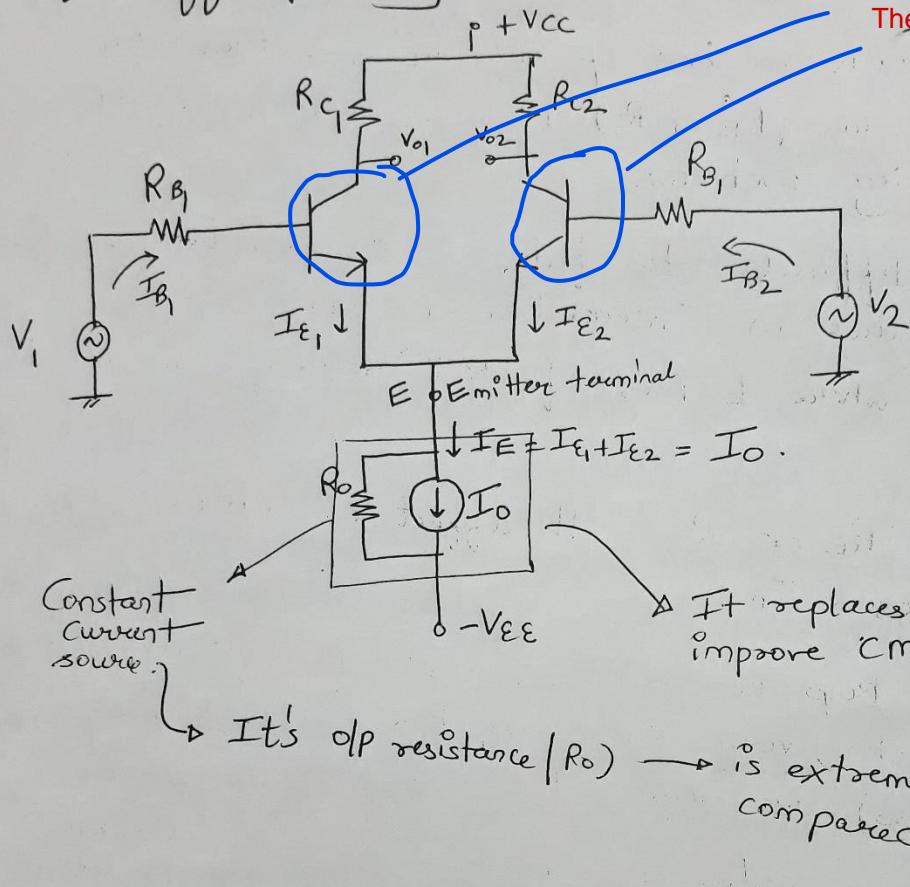

→ Now, this constant current source ckt's we are going to study and analyze in details.

i.e We will consider types of ckt's that can be designed to establish the bias current I_O .

Advantages of using Constant Current Sources :-

30

1. Transistor current sources are widely used in analog Integrated ckts both as biasing elements and as loads for amplifying stages.
2. Active current sources helps in increasing the voltage gain of an amplifier.
3. Constant current sources have a very high O/P resistance (R_o) and its O/P current is not sensitive to the transistor parameter β .
4. Current sources are less sensitive to variations in DC power supply and temperature.
5. Especially, for a small value of bias current, the current sources are more economical than resistor's in terms of die area required for resistors.

→ A current source can be designed by using either MOSFET's or BJTs.

We have analyzed various BJT current sources.


→ Let's analyze MOSFET current source's next.

- MOSFET current sources are analogous to BJT current sources

MOSFET Current Sources

31

- The choice of a BJT current source or a MOSFET current source generally depends on the type of integrated ckt involved (eg bipolar or MOS).
- BJT current sources have some advantages over MOSFET current sources, such as a wider compliance range and a higher o/p resistance.
- However, a higher o/p resistance can be obtained by cascode-like connections of MOSFETs.
- How MOSFET can be used as a Current Source?

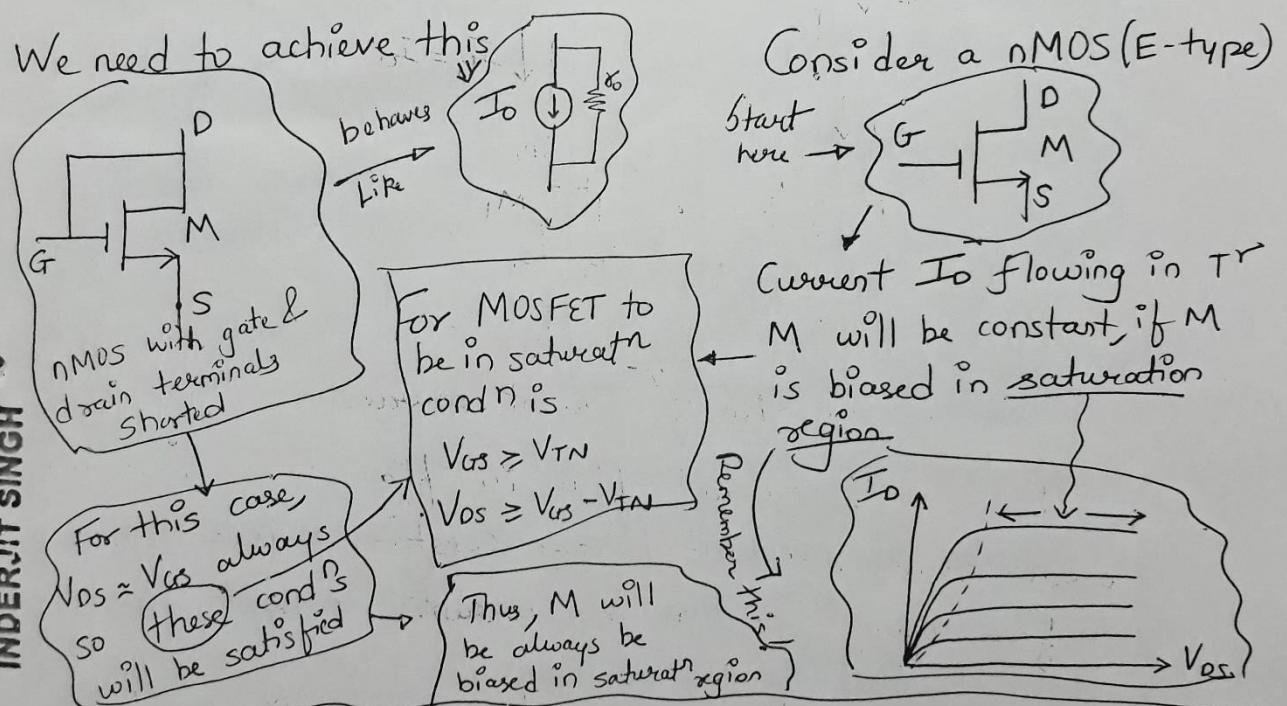

NB: Voltage compliance range :— It is the voltage range over which the ckt can maintain a constant current.

V_{TN} → Threshold voltage of NMOS-E type.

Types of MOSFET constant current sources which we will be studying are

- Basic two-transistor current source
- ~~Three-transistor current source.~~
- Cascoded current source
- Wilson current source.

A]

Basic two-transistor MOSFET Current Source.

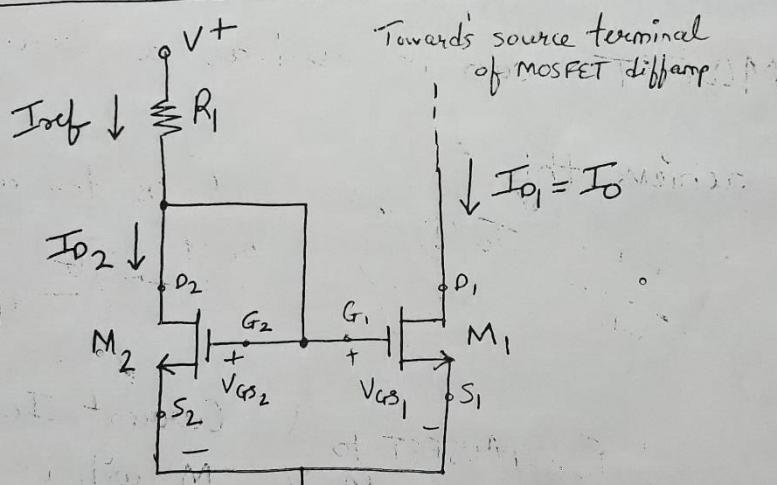


fig 7.1 Two-transistor NMOS current source.

- The direction of current flow in fig 7.1 is into the current source; this type of constant-current source is often referred to as a current sink.
- Let us assume that the two transistors M₁ and M₂ are identical (i.e. $V_{GS1} \approx V_{GS2}$, i.e. $I_{D1} = I_{D2}$)

INDERJIT SINGH

• Thus, the o/p current $I_o (= I_{D1})$ will be the mirror of I_{D2} .

• Also, since $V_{DS2} = V_{GS2}$, M_2 is always biased in the saturation region.

• Let V_{TN1} and V_{TN2} be the threshold voltages of M_1 & M_2 .

• For M_1 to be in saturation, V_{DS1} which is greater than or equal to $(V_{GS2} - V_{TN2})$, must be greater than $(V_{GS1} - V_{TN1})$.

• This condition reduces the voltage compliance range of the MOSFET current source and prevents it from operating from a low power supply.

Current Relationship:

• Drain current eqn of an E-type NMOS biased in saturation region is,

$$I_{Dsat} = k_n (V_{GS} - V_T)^2 (1 + \gamma V_{DS}) \quad \text{--- (a)}$$

where, $k_n = \mu_n C_{ox} \left(\frac{W}{L} \right) \frac{1}{2}$, γ - channel length modulation parameter

• The o/p current ' I_o ', which is equal to drain current of M_1 , is given by,

$$I_{D1} = I_o = k_{n1} (V_{GS1} - V_{TN1})^2 (1 + \gamma V_{DS1}) \quad \text{--- (1)}$$

• Drain current I_{D2} which is equal to the reference current I_{ref} is

$$I_{D2} = I_{ref} = k_{n2} (V_{GS2} - V_{TN2})^2 (1 + \gamma V_{DS2}) \quad \text{--- (2)}$$

- Since, all the components of the current source are processed on the same IC, all the physical parameters such as (V_{TN} , μ_n , l_{ox} & γ) are identical for both devices (M_1 and M_2)
- \therefore Ratio of I_o to I_{ref} is given by (using ① & ②),

$$\frac{I_o}{I_{ref}} = \frac{k_n_1 (V_{GS_1} - V_{TN_1})^2 (1 + 2V_{DS_1})}{k_n_2 (V_{GS_2} - V_{TN_2})^2 (1 + 2V_{DS_2})} \quad - \textcircled{3}$$

$$= \frac{\mu_n l_{ox} \left(\frac{w}{L}\right)_1 \left(V_{GS_1} - V_{TN_1}\right)^2 (1 + 2V_{DS_1})}{\mu_n l_{ox} \left(\frac{w}{L}\right)_2 \left(V_{GS_2} - V_{TN_2}\right)^2 (1 + 2V_{DS_2})}$$

$$\frac{I_o}{I_{ref}} = \frac{\left(\frac{w}{L}\right)_1}{\left(\frac{w}{L}\right)_2} \times \frac{(1 + 2V_{DS_1})}{(1 + 2V_{DS_2})} \quad - \textcircled{4}$$

In practice, $2V_{DS} \ll 1$, then eqn ④ can be approximated by,

$$\frac{I_o}{I_{ref}} = \frac{\left(\frac{w}{L}\right)_1}{\left(\frac{w}{L}\right)_2} \quad - \textcircled{5}$$

$$i.e. \frac{I_o}{I_{ref}} = \frac{\left(\frac{w}{L}\right)_1}{\left(\frac{w}{L}\right)_2} \cdot I_{ref}$$

By controlling the ratio (w/L) , we can change the o/p current.

By choosing identical transistors, with $W_1 = W_2$ and $L_1 = L_2$, a designer can ensure that the o/p current I_o is almost equal to the reference current I_{ref} .

From fig 7.1,

Since $V_{GS2} = V_{DD} - I_{ref} R_1$ and $V_{DS2} = V_{GS2}$ (From eqn ②)

$$\therefore I_{ref} = I_{D2} = K_n 2 (V_{DD} - I_{ref} R_1 - V_{TN2})^2 \quad \text{--- (6)}$$

I_{ref} can be solved for known values of V_{TN2} , $K_n 2$, V_{DD} and R_1 .

• O/P resistance:

The stability of the load current as a function of V_{DS} voltage is an important consideration in many applications.

- The small-sig o/p resistance of the current source can be estimated as follows, (fig 7.2)

$$R_o = Y_{O1}$$

$$; Y_{O1} = \frac{V_x}{I_x}$$

since $g_m 2 V_{GS2} \approx 0$, V_{GS1}
so $g_m 1 V_{GS1}$ becomes redundant

where, Y_{O1} is o/p resistance looking into transistor M₁

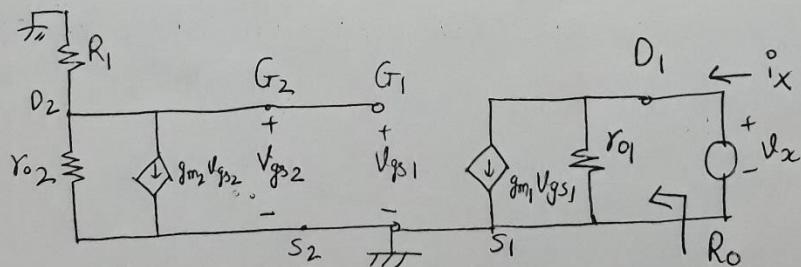


fig 7.2 : Small-sig equivalent ckt. of fig 7.1

- The stability of the load current ($I_o = I_{D1}$) can be described in terms of O/P resistance,

From fig 7.1, $V_{DS2} = V_{GS2} = \text{constant}$ for a given reference current

Normally, $\lambda V_{DS2} = \lambda V_{GS2} \ll 1$, & if $(W/L)_1 = (W/L)_2$] (a)

Then the change in bias current w.r.t to a change in V_{DS_1} is

$$\frac{1}{R_o} = \frac{\partial I_o}{\partial V_{DS_1}} = \frac{1}{Y_{O_1}} = \frac{\partial I_{D1}}{\partial V_{DS_1}} \quad \text{--- (b)}$$

from (a) & eqⁿ ① and ④

$$\frac{\partial I_{D1}}{\partial V_{DS_1}} \approx \frac{K_{n1} (V_{GS_1} - V_{TN1})^2 (1 + \lambda V_{DS_1})}{\lambda}$$

$$\approx I_{D1} \lambda$$

$$\text{i.e. } \frac{1}{Y_{O_1}} \approx I_{D1} \lambda$$

$$\therefore \boxed{Y_{O_1} \approx \frac{1}{\lambda I_{D1}}}$$

where, Y_{O_1} is the o/p resistor of the transistor M_1 .

$$\therefore \boxed{R_o = Y_{O_1} = \frac{1}{\lambda I_{D1}}} \quad \text{which is relatively small.}$$

This small o/p resistance is a disadvantage of having only one MOSFET M_1 at the o/p side of a current source.

INDUSTRIAL ELECTRONICS

— X —

3) Modified three-transistor MOSFET Current source: 37

- Reference current in BJT current sources is generally established by bias voltage and a resistor. Since MOSFETs can be configured to act like a resistor, the reference current in MOSFET current sources is usually established by using additional transistors.
- The reference resistance R_i in fig 7.1 can be replaced by another MOSFET M_3 as shown in fig 8.1.

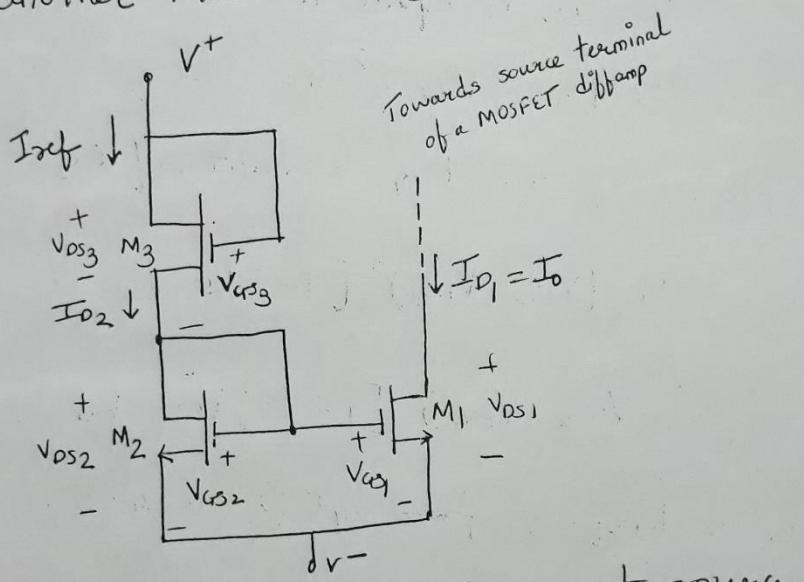


Fig 7.1 → Three-transistor MOSFET current source.

- Transistors M_2 and M_3 are used as voltage dividers to control the gate-source voltage of M_1 .
- If M_1 and M_2 are identical, the o/p current (I_o) exactly mirrors the drain current through M_2 and M_3

$$I_o \approx I_{D1} \quad (\text{From fig 7.1})$$

INDERJIT SINGH

Current Relationship:

Since $V_{GS1} = V_{GS2}$, from fig (7.1)

The drain current I_{D1} ($= I_0$) is equal to the drain current I_{D2} and is given by

$$I_{D1} = I_{D2} = I_{ref} = k_{n1} (V_{GS1} - V_{TN1})^2 (1 + \gamma V_{GS1}) \quad \text{--- (1)}$$

Since $V_{DS2} = V_{GS2} \rightarrow I_{D2}$ is equal to reference current I_R ,

$$I_{D2} = I_{ref} = k_{n2} (V_{GS2} - V_{TN2})^2 (1 + \gamma V_{GS2}) \quad \text{--- (2)}$$

Since $V_{GS3} = V^+ - V_{GS2}$, the drain current of M_3 is

$$I_{D3} = I_{ref} = k_{n3} (V_{GS3} - V_{TN3})^2 (1 + \gamma V_{GS3}) \quad \text{--- (3)}$$

$$I_{D3} = k_{n3} (V^+ - V_{GS2} - V_{TN3})^2 [1 + \gamma (V^+ - V_{GS2})] \quad \text{--- (4)}$$

Since $I_{D2} = I_{D3} = I_{ref}$, from eqn (2) & (4), we get

$$\frac{k_{n2} (V_{GS2} - V_{TN2})^2 (1 + \gamma V_{GS2})}{k_{n3} (V^+ - V_{GS2} - V_{TN3})^2 [1 + \gamma (V^+ - V_{GS2})]} = 1 \quad \text{--- (5)}$$

Thus, by controlling the constants k_{n2} & k_{n3} , we can obtain the desired value of $V_{GS2} = V_{GS1}$, which will give the desired o/p current (I_0) (from eqn (1)).

INDERJIT SINGH

Finally the load current, for $\lambda=0$, is given by 39

$$I_O = \frac{k_n' W}{2} \left(\frac{V_{GS1} - V_{TN1}}{L} \right)^2 \quad \text{--- (6)}$$

where $k_n' = \mu_0 C_x$

- Since the designer has control over the (W/L) ratios of transistors, there is considerable flexibility in the design of MOSFET current sources.

- O/P resistance (R_O):

→ The O/P resistance of three-transistor MOSFET constant current source can be determined by looking into O/P transistor M_1 .

→ It is similar to two-transistor's O/P resistance

$$\therefore R_O = r_{O1} = \frac{1}{2ID_1}$$

which is relatively small.

→ INDERJIT SINGH This small O/P resistance is a disadvantage of having only one MOSFET M_1 at the O/P side of a current source.

The O/P resistance of a MOSFET basic current source & modified MOSFET current source can be increased by connecting MOSFETs in a cascode-like connection.

INDERJIT SINGH

