

Avg: Voltage with -ve f_{lb}

$$V_{out} = A_v(V_{in} - KV_{out})$$

$$V_{out} = A_v V_{in} - A_v K V_{out}$$


$$V_{out}(1 + KA_v) = A_v V_{in}$$

$$A_{vf} = \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + KA_v}$$

open-loop gain

→ (closed)-loop gain

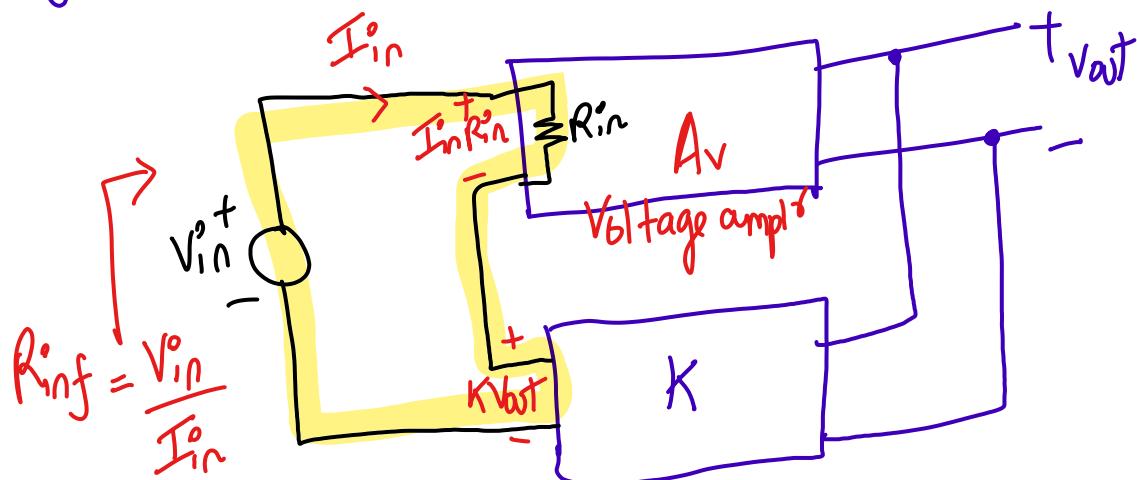② R_{inf} ((closed loop I_{lp} resistance))



$$\rightarrow V_{out} = A_v I_{in} R_{inf}$$


$$\rightarrow \text{KVL at } I_{lp} \text{ side, } V_{in} - I_{in} R_{inf} - KV_{out} = 0$$

$$V_{in} = I_{in} R_{inf} + K A_v I_{in} R_{inf}$$

$$R_{inf} = \frac{V_{in}}{I_{in}} = R_{in} (1 + KA_v)$$

$R_{in} - I_{lp}$ resistance
of open loop
amplifier

3) Root_f (Closed-loop o/p resistance)

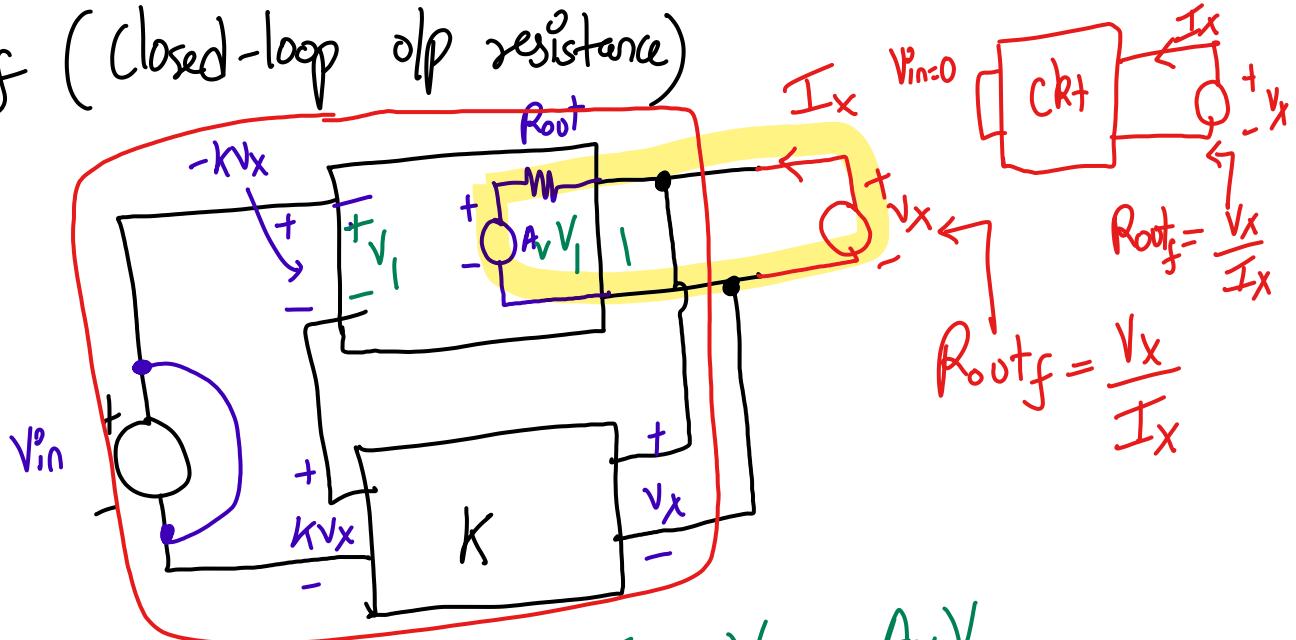

$$\rightarrow A_v V_1 = -A_v K V_x \rightarrow I_x = \frac{V_x - A_v V_1}{R_{out}}$$

$$\rightarrow I_x = \frac{V_x + A_v K V_x}{R_{out}}$$

$$R_{out} I_x = V_x (1 + K A_v)$$

$$Root_f = \frac{V_x}{I_x} = \frac{R_{out}}{(1 + K A_v)}$$

Current-shunt ~~ve fb amplifier~~:

