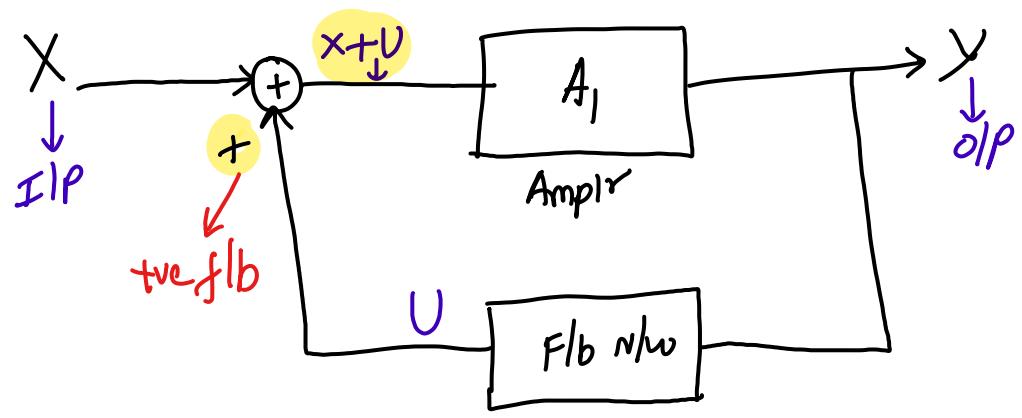


Concept of Positive feedback:



X & U are
in phase

$$\rightarrow \text{Feedback signal: } U = KY \quad \frac{Y}{X} = ?$$

$$\rightarrow Y = A_1(X+U)$$

$$\rightarrow Y = A_1(X+KY)$$

$$\rightarrow Y(1-KA_1) = A_1X$$

A_1 - open loop gain

$$\frac{Y}{X} > A_1$$


Closed
loop gain

+ve f/b

KA_1 : loop gain

$$\rightarrow \text{If } K \uparrow \text{ses } \rightarrow A_1 \text{ being constant } \rightarrow \frac{Y}{X} \text{ will } \uparrow \text{se } KA_1 \rightarrow 1 \rightarrow \frac{Y}{X} \rightarrow \infty$$

v.hig. \rightarrow instability

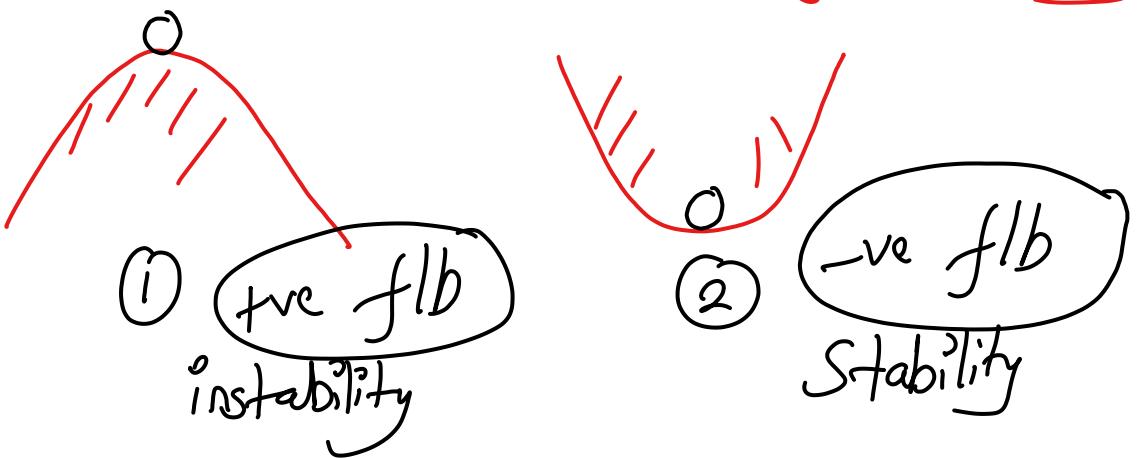

Oscillator

V_S




Amplifier

sustained oscillation

→ An oscillator is an amplifier with +ve f/b

An oscillator provides a periodic sinusoidal waveforms of adjustable amplitude of any desired frequency



Oscillator.

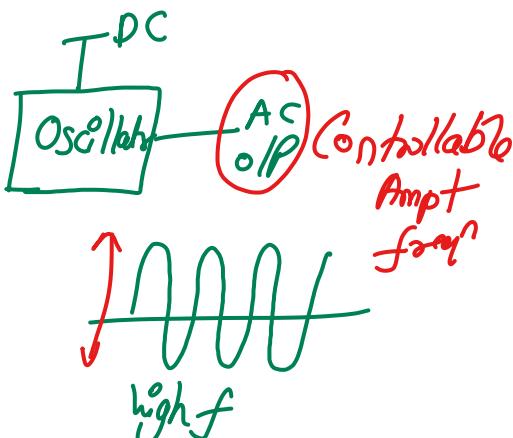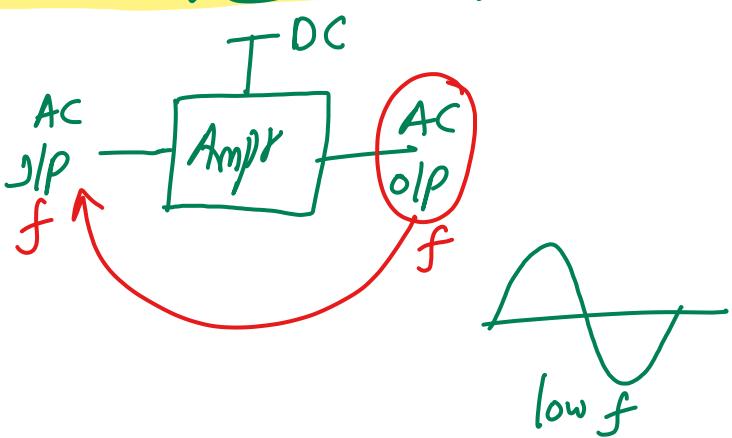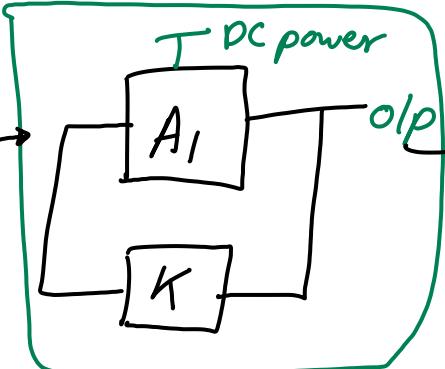

Principle of oscillations:

Oscillator: +ve f/b does not guarantee oscillations.

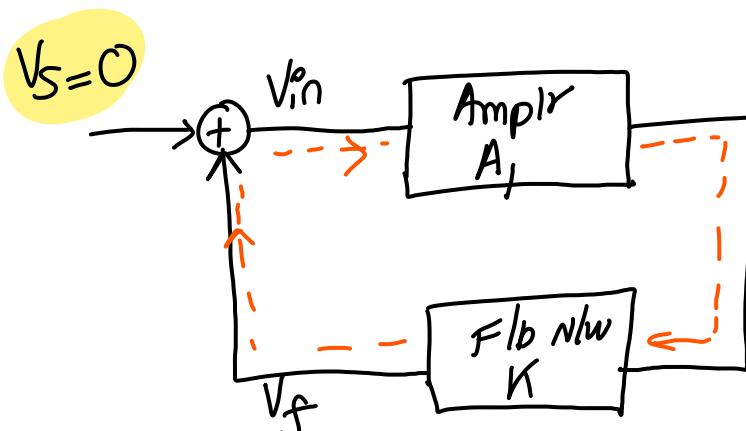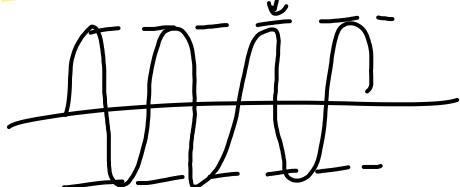An oscillator, to produce sustained oscillation → it should obey "Barkhausen's criterion"




$$\textcircled{1} \quad A_1 K \geq 1$$

$$\textcircled{2} \quad \frac{A_1 K}{\sqrt{A_1 K}} = 0 \text{ or } 360^\circ \text{ or } 2\pi \text{ radians}$$


Phase shift

Effect of loop gain $|A_1 K|$ on nature of oscillations?


$$\textcircled{1} \quad |A, K| < 1$$

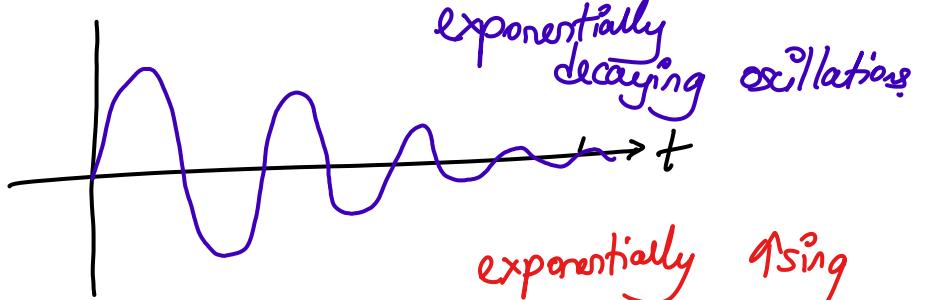


$$\textcircled{2} \quad |A, K| > 1$$

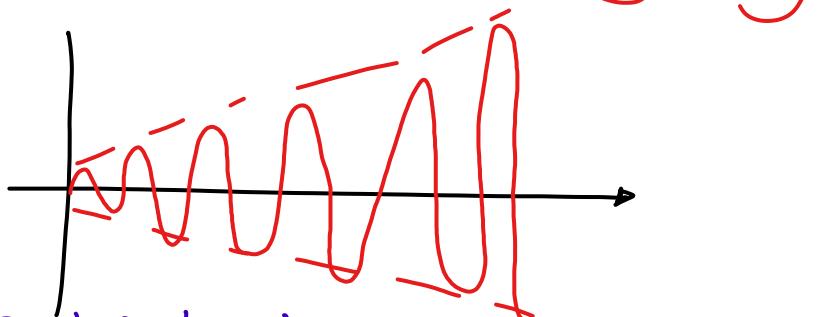

$$\textcircled{3} \quad |A, K| = 1$$

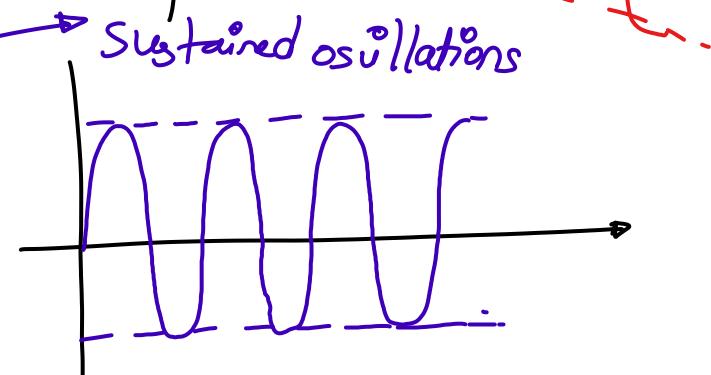



$$\textcircled{4} \quad |A, K| \geq 1$$

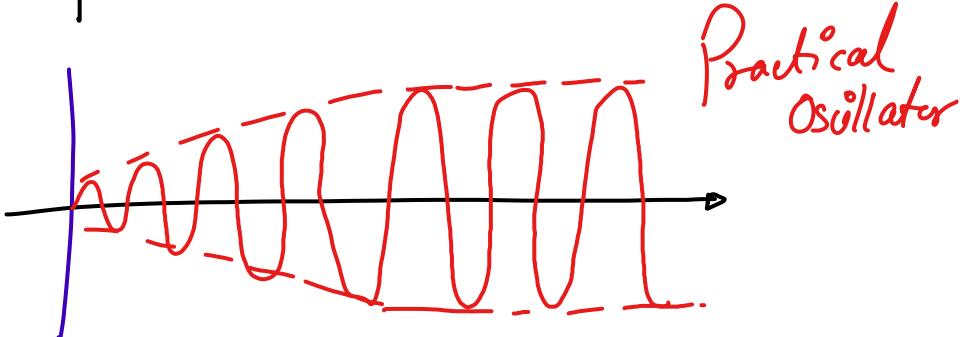

$|A, K| \geq 1$? Why
+10% → offset the non-linearities existing in the ckt
(BJT, MOSFET)

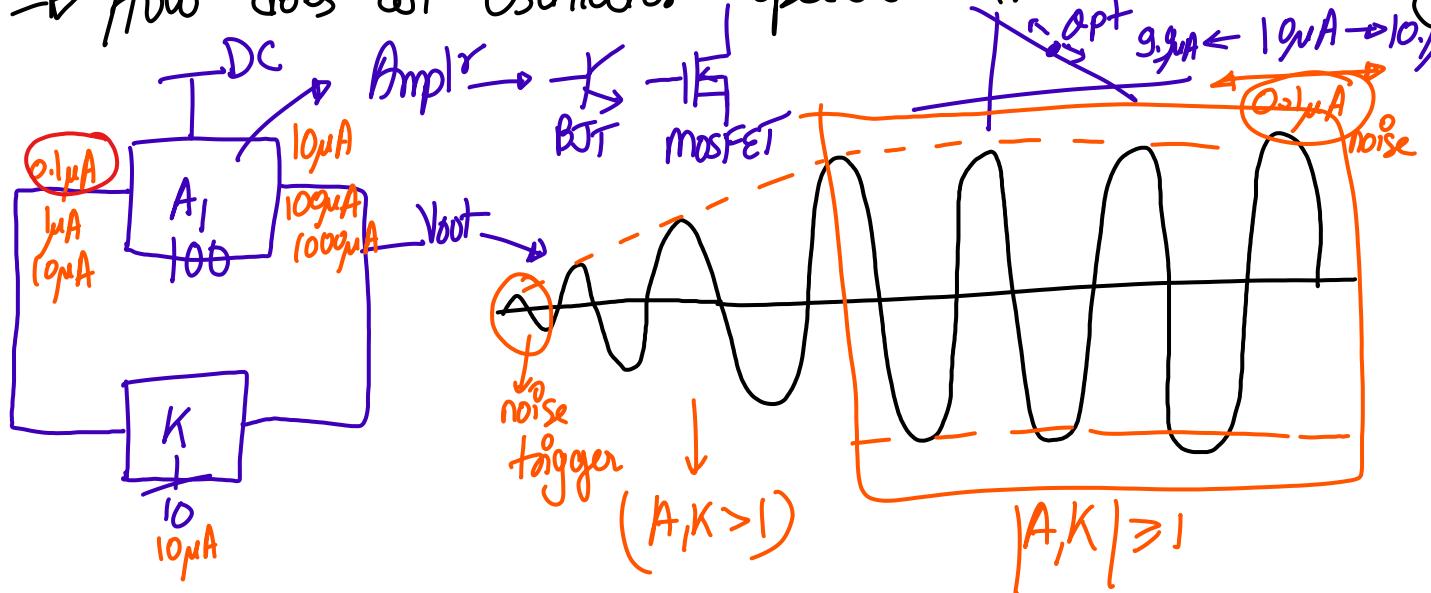→ How does an Oscillator operate without an AC input sig?



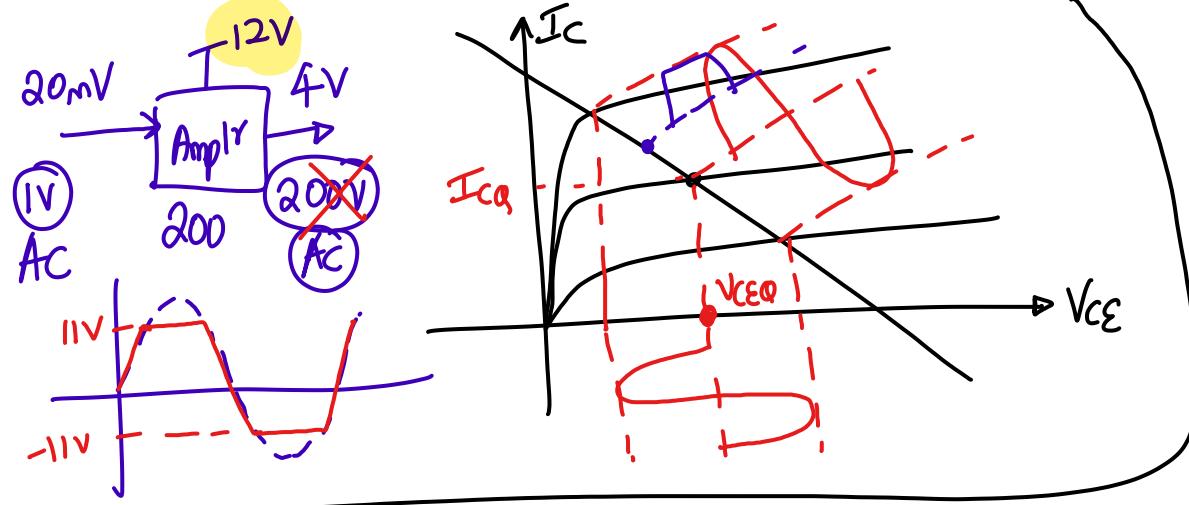

Classification of oscillators:-

Sinusoidal oscillators

- ① low-frequency oscillator (audio-freqⁿ)
- ② high-frequency oscillator (RF oscillator)

eg ① RC phase shift oscillator
② Wien-bridge oscillator

f_{lb} f_{ub}
 R, C elements
($20\text{Hz} - 20\text{kHz}$)



eg ① Hartley oscillator
② Colpitt's oscillator
(Clapp's)

- Not in syllabus*
- ### Non-sinusoidal
- Multivibrators (Schmitt trigger)
 - UJT relaxation oscillator
 - Crystal oscillator

Quartz crystal

10M
ckt diagⁿ = 3M
principle of oscillation \rightarrow 2M
Working: 3M
freq exp: 1M
Adv, Disadv: 1M

RC phase oscillator (BJT)

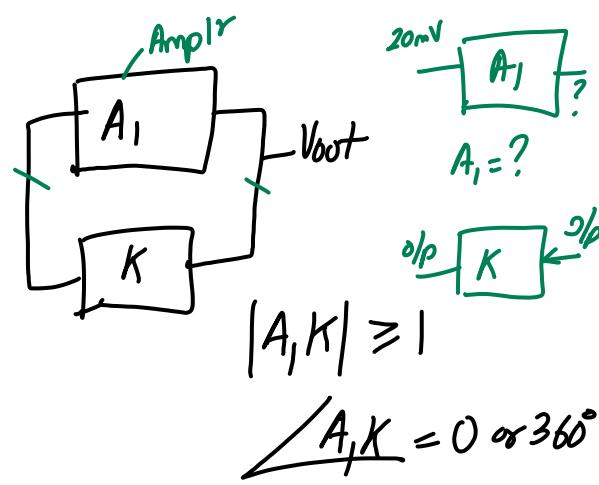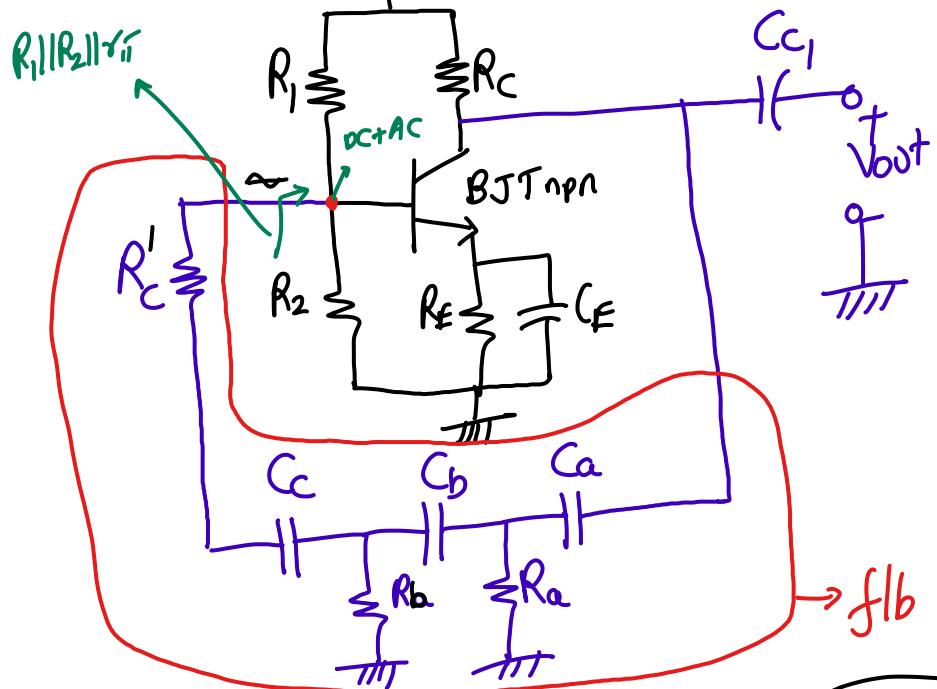

$$RC \rightarrow 60^\circ$$

$$3 \times RC \rightarrow 60^\circ \times 3 = 180^\circ \rightarrow f_{lb} \text{ n/w}$$

$$CE \text{ Amplifier} \rightarrow 180^\circ$$


Phase shift

$360^\circ \text{ or } 0^\circ$

$$f_0 = \frac{1}{2\pi R C \sqrt{6+4K}}$$




$$R = \frac{R_C}{R}$$

$$R'_c = R - R_{in}$$

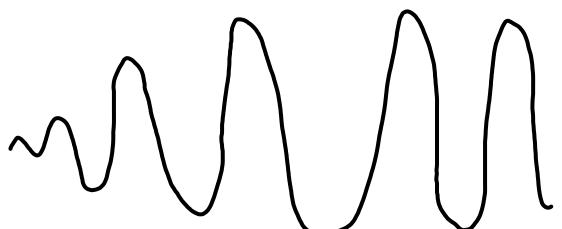

$$R = R_a = R_b$$

$$C = C_a = C_b = C_c$$

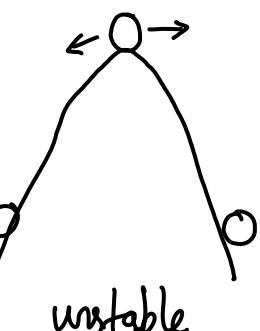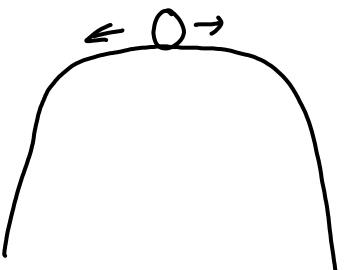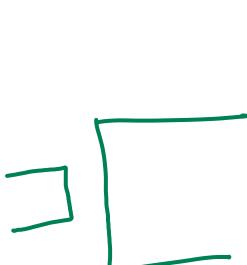

$$A_1 = 45.514$$

$$K = 0.067$$

$$|A_1 K| > 1$$

$$|A_1 K| = 3.04$$

Wien-bridge oscillator:

