
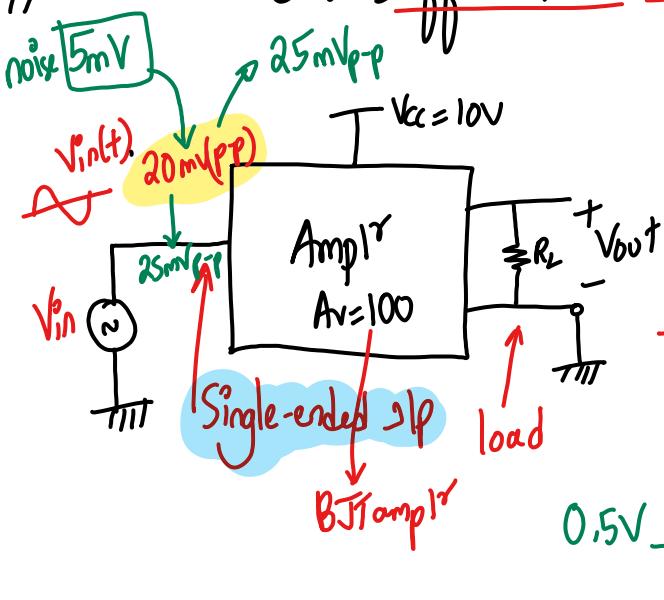



Module 5: Differential amplifier

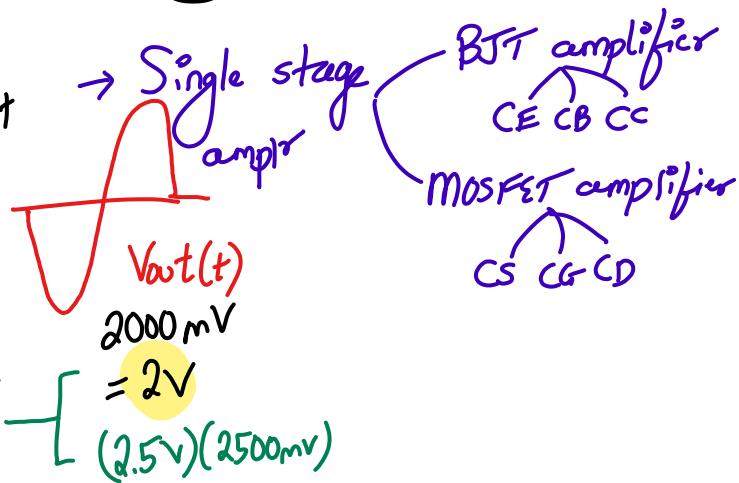


Why diffamp?



Source of noise (AC-DC):

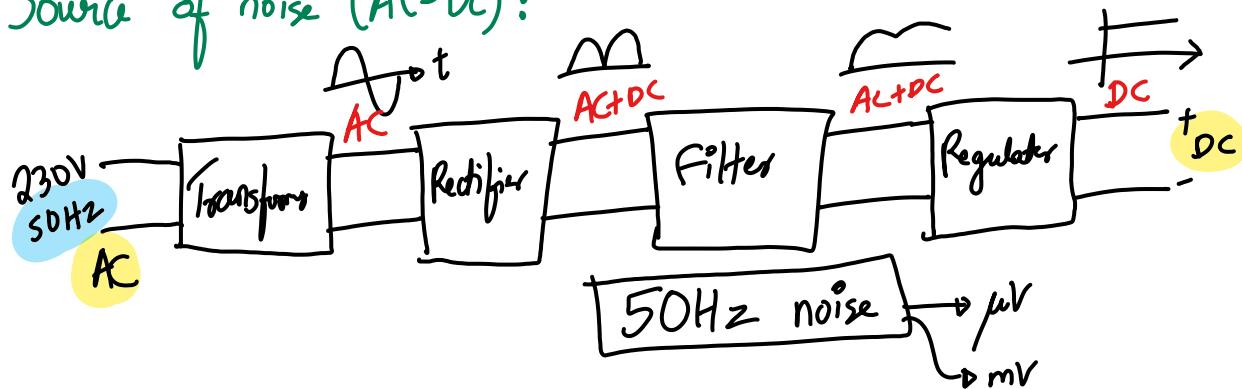

Concept of Differential sig:

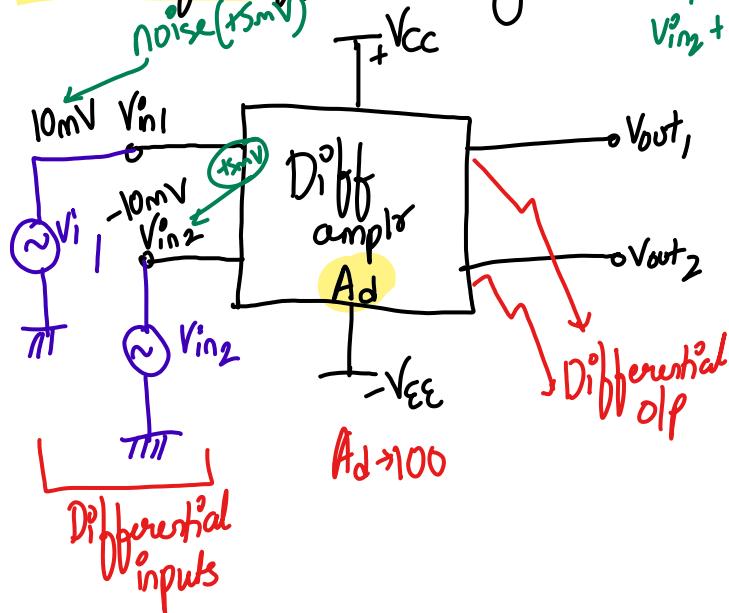

$$V_{out} = V_{out_1} - V_{out_2}$$

$$V_{out} = A_d(V_{in_1} - V_{in_2})$$

$$V_{out} = Ad \left(V_{in_1}^o + \cancel{V_{in_2}} - \cancel{(V_{in_2}^o + V_{in_3})} \right)$$

$$V_{out} = Ad(V_{in1}^o - V_{in2}^o)$$

$$V_{out} = 100(10_{mV}(-10mV))$$

$$V_{out} = \underline{2V}$$

(AC) $\overline{\rightarrow}$ noise free o/p


1) Differential op voltage (V_d or V_{id}):

If inputs (V_{in1} & V_{in2}) applied to the differential amplifier are such that there exist either amplitude or phase difference between them \rightarrow such inputs are called as "differential op"

$$V_d = V_{id} = V_{ind} = V_{in1} - V_{in2}$$

eg $V_{in1} = 40\text{mV}$, $V_{in2} = 20\text{mV}$ $\rightarrow V_{id} = V_d = 20\text{mV}$
(Amplitude difference)

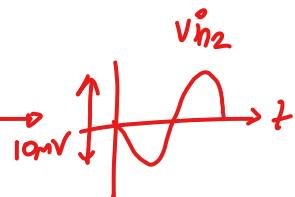eg $V_{in1} = 10\text{mV} @ 0^\circ$, $V_{in2} = 10\text{mV} @ 180^\circ$ phase
(phase difference)
 $V_{id} = 10\text{mV} - (-10\text{mV})$
 $V_d = 20\text{mV}$



2. Differential mode gain (A_d or A_{vd})

The gain with which differential amplifier amplifies the differential inputs signal (V_{id} or V_d) is known as

"Differential mode gain" $\frac{\text{differential op voltage } (V_{out}) \text{ w.r.t } (V_{in1} - V_{in2})}{\text{differential op voltage } (V_{out}) \text{ w.r.t } (V_{in1} + V_{in2})}$

$$A_d = \frac{V_{out1} - V_{out2}}{(V_{in1} - V_{in2})} = \frac{V_{outd}}{V_{ind}} = \frac{V_{od}}{V_{id}}$$

100 μV $\rightarrow V_{id}$ 50 μV

Ideally: $A_d : \infty$

Practically: $A_d \rightarrow$ very high

Diff amp ∞
ECG - low mV
EEG - low mV or μV

3. Common mode input voltage : (V_{icm} or V_{cm})

If inputs (V_{in1} , V_{in2}) applied to diffamp are of same magnitude & phase \rightarrow then such sig's are known as 'Common-mode input voltage'

$$V_{cm} = \frac{V_{in1} + V_{in2}}{2}$$

$$V_{in1} = 10\mu V, V_{in2} = 10\mu V$$
$$V_{cm} = \frac{10\mu V + 10\mu V}{2} = 10\mu V$$

eg $V_{in1} = 1V$, $V_{in2} = 1V$ $\rightarrow V_{cm} = \frac{1+1}{2} = 1V$ $V_{cm} \neq 0$
(same magnitude)

4. Common mode gain (A_{cm} or A_{vcm})

The gain with which the diffamp amplifies the common-mode sig is called "Common-mode gain"

$$A_{cm} = \frac{V_{out}}{V_{cm}} = \frac{V_{outcm}}{V_{cm}}$$

V_{out} due to common-mode component of op V_{cm} noise

Ideally, $A_{cm} \rightarrow 0$

Practically, $A_{cm} \rightarrow$ very low (< 1)

Reject?

5. CMRR (Common mode rejection ratio):

- It is the ability of diffamp to amplify differential mode signal & reject common-mode signal

- It is the ratio of differential mode gain (A_d) to the common-mode gain (A_{cm})


- $CMRR = \frac{A_d}{A_{cm}}$
- $CMRR_{dB} = 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right)$

eg 80dB

Ideally $\rightarrow CMRR = \frac{A_d \rightarrow \infty}{A_{cm} \rightarrow 0} \rightarrow CMRR \rightarrow \infty$


Practically $\rightarrow CMRR \rightarrow$ very high

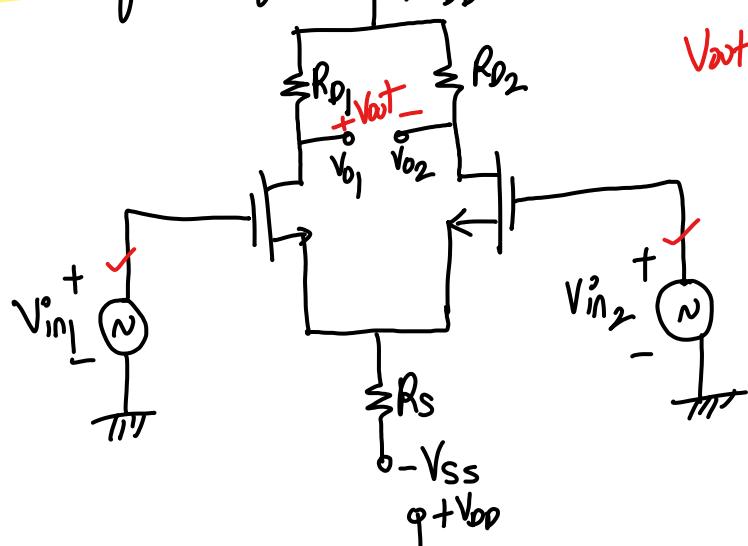Types of Differential amplifier: DIBO, DIUO, SIBO, SIUO



$$V_{out} = V_{o1} - V_{o2}$$

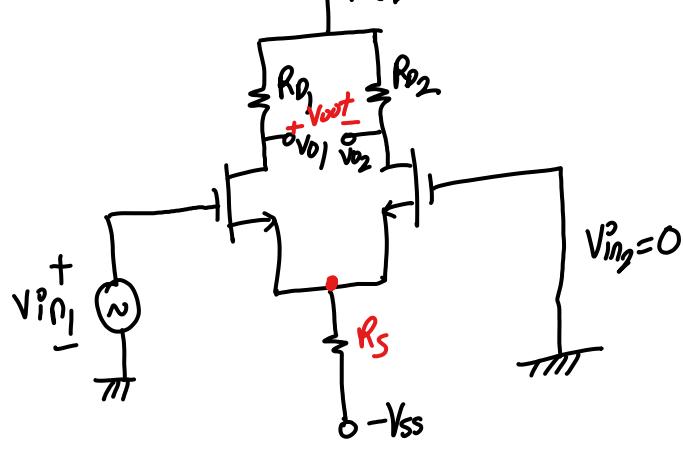
Dual i/p balanced o/p
Differential ampl'r
(DIBO)




SIBO
(Single i/p balanced
o/p diff ampl'r)

$$V_{out} = V_{o1} - V_{o2}$$

$$V_{in2} = V_{in1}$$

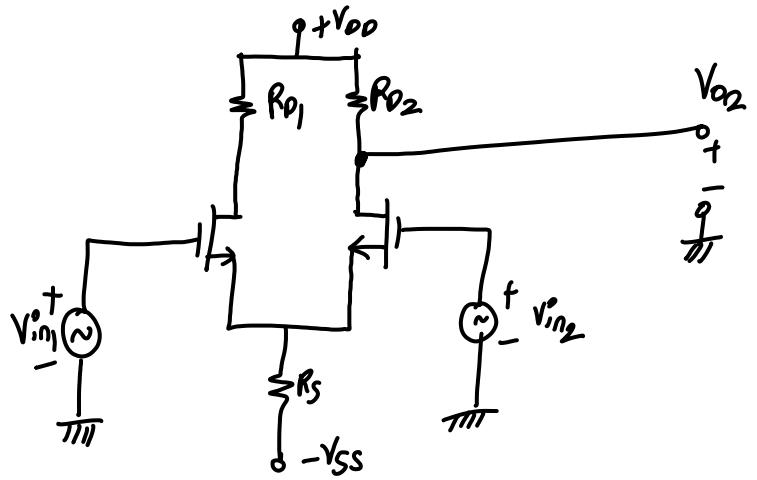

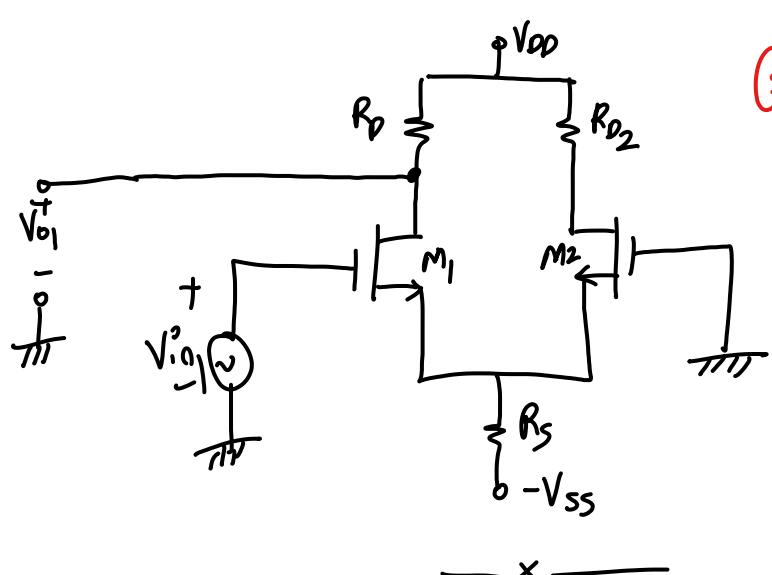DIVO
(Dual-gate unbalanced opamp)
 $V_{out} = V_{o1} \text{ or } V_{o2}$
 op measured
w.r.t. ground



SILO
(Single-gate unbalanced opamp)
 $V_{out} = V_{o1} \text{ or } V_{o2}$

$V_{in} = V_{in1} \text{ or } V_{in2}$

