

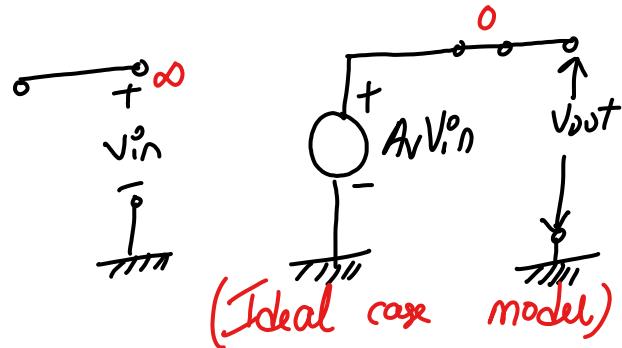


Models of 4 amplifier topologies:-


① Voltage amplifier

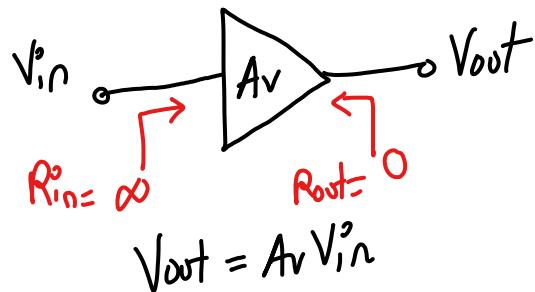



(Practical model
of Voltage ampl)

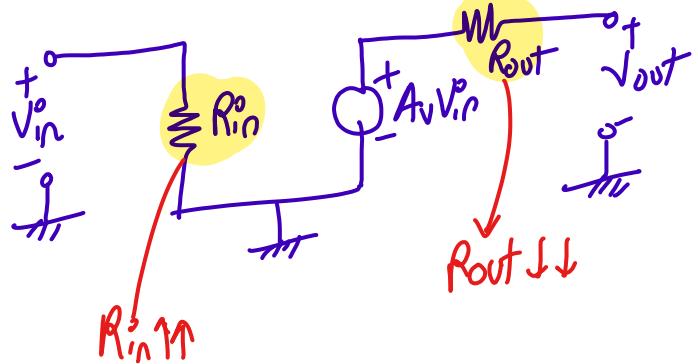


② Transimpedance amplifier

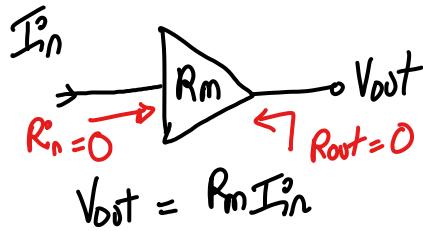


Practical model
of TI ampl

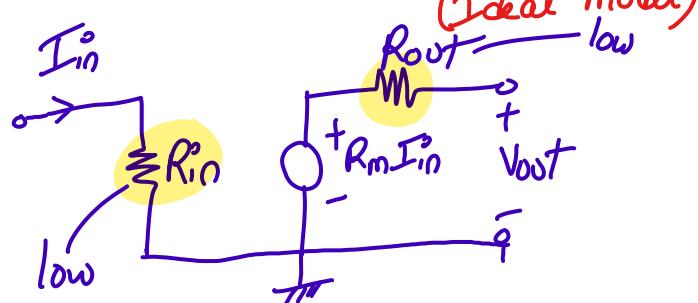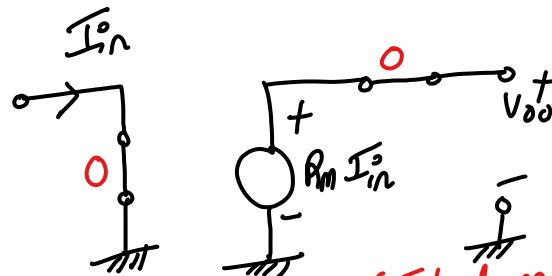

③ Transconductance amplifier

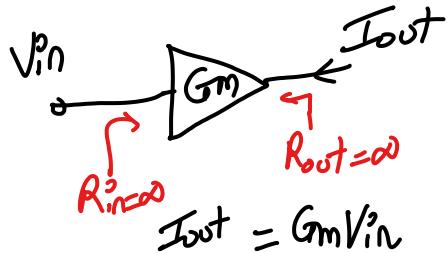


④ Current amplifier

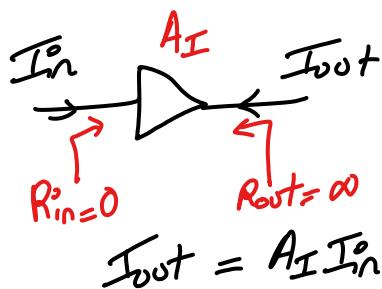


Ideal model




Ideal model

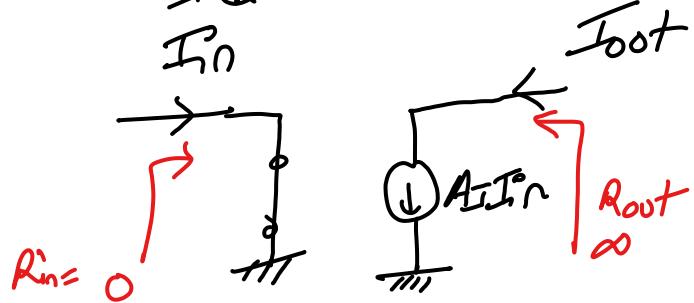


Practical model

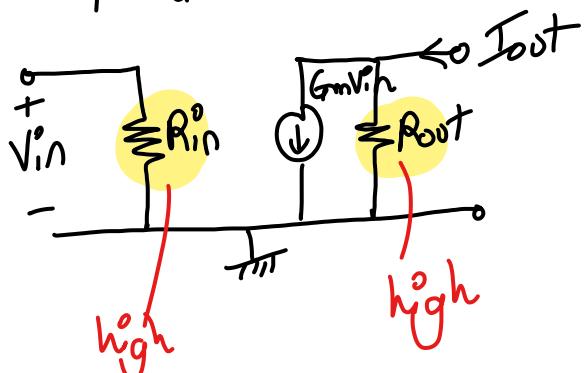

Practical model

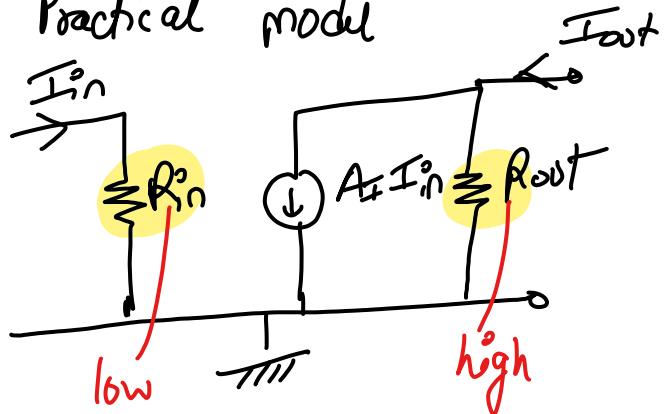

Sense & Return mechanism:

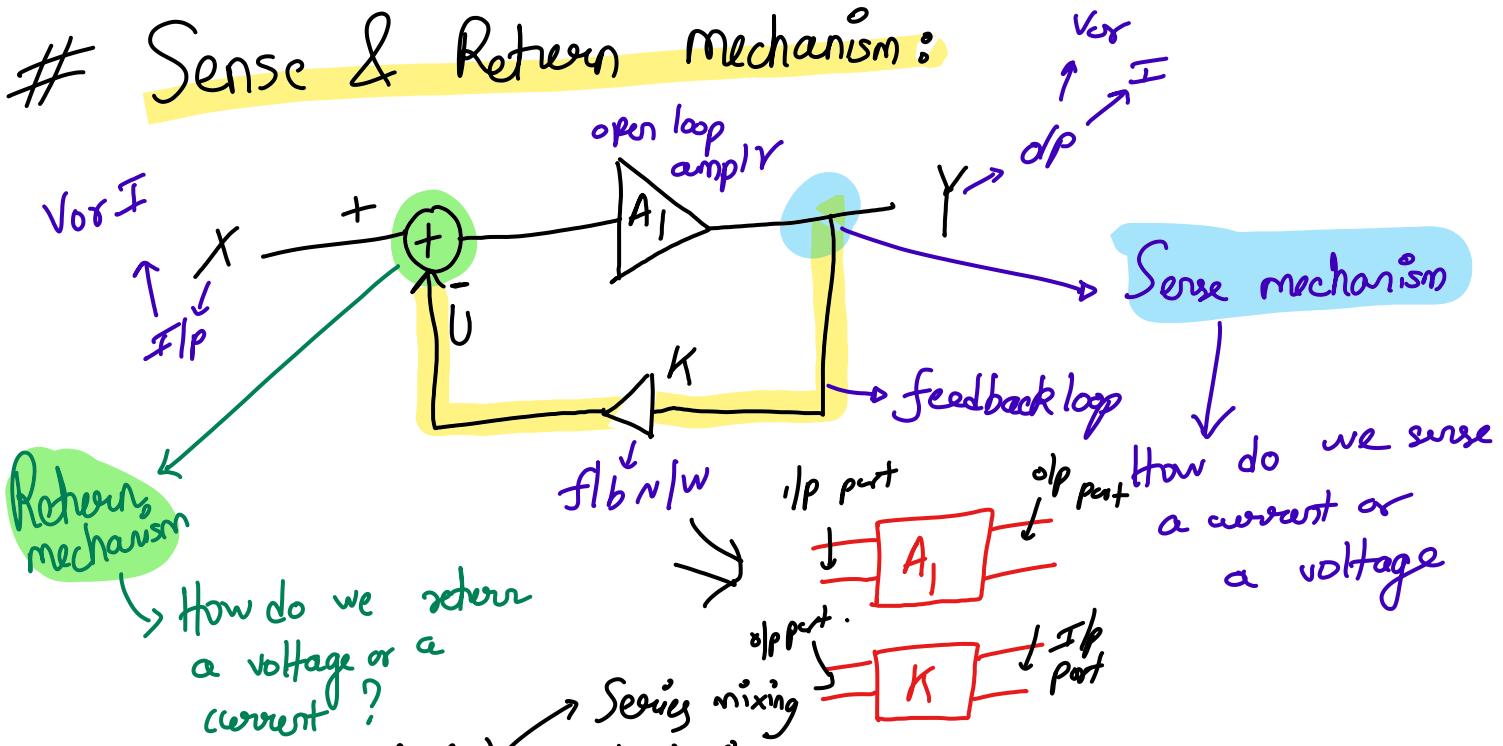



Return mechanism:


→ How to subtract two voltages or two currents

$$2V + 6V \quad \frac{V_1}{T} - \frac{2V}{T}$$


$$\frac{V_2}{T} - \frac{6V}{T}$$

V_1 & V_2 are in series.

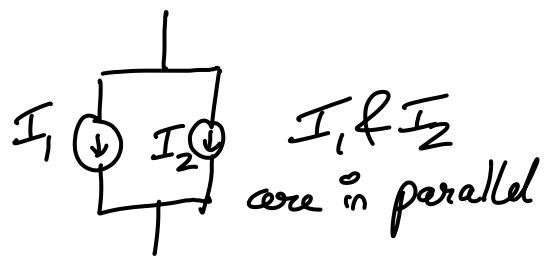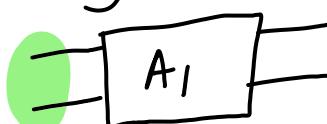

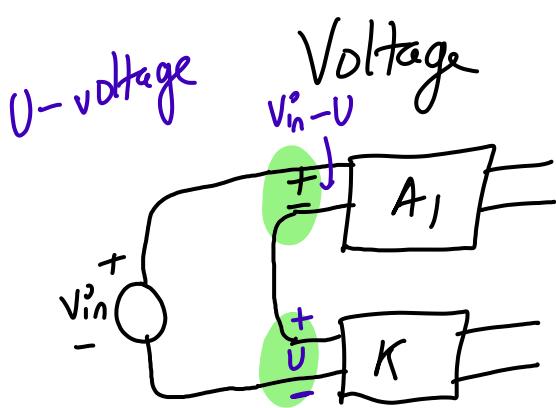


Returning a voltage at I_{out}

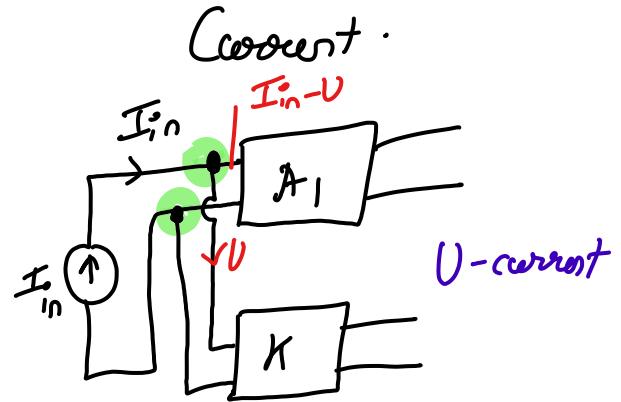


Returning a current at I_{out}

Sense mechanism: /Sampling


Voltage sense
Current sense

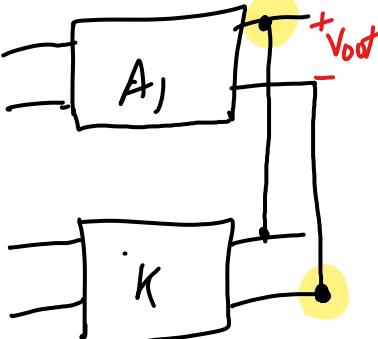

Sensing a voltage

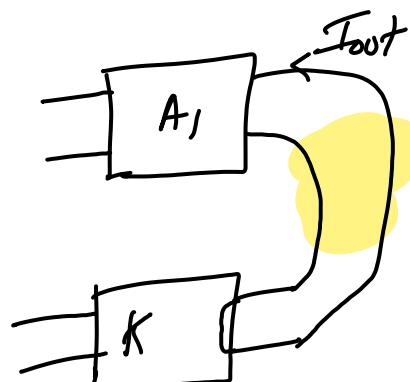

Sensing a current

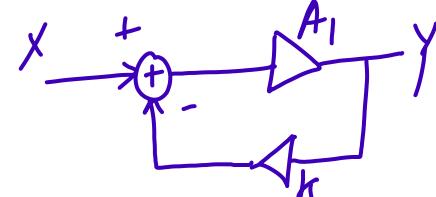

I_{out}	o/p	feedback signal
X	Y	U

Feedback Topology

Voltage - Voltage fb
sensing returning
Shunt - Series fb
Voltage - series fb

Voltage - current fb
Shunt - shunt fb
Voltage - shunt fb

Current - voltage fb
sensing return
Series - Series fb
Current - Series fb

Current - Current fb
Series - shunt fb
Current - shunt fb

A -ve negative topologies:

' A_f '

AIM → to find Closed-loop gain

& closed-loop o/p impedance ($R_{in,f}$)

& closed-loop o/p impedance ($R_{out,f}$)

Analysis of Voltage-series -ve f/b topology:


V_{in} -inbut o/p
Voltage-series
 \rightarrow J/fb (voltage)

$$V_{out} = A_v (V_{in} - k V_{out})$$

$$V_{out} + A_v k V_{out} = A_v V_{in}$$

$$V_{out} (1 + A_v k) = A_v V_{in}$$
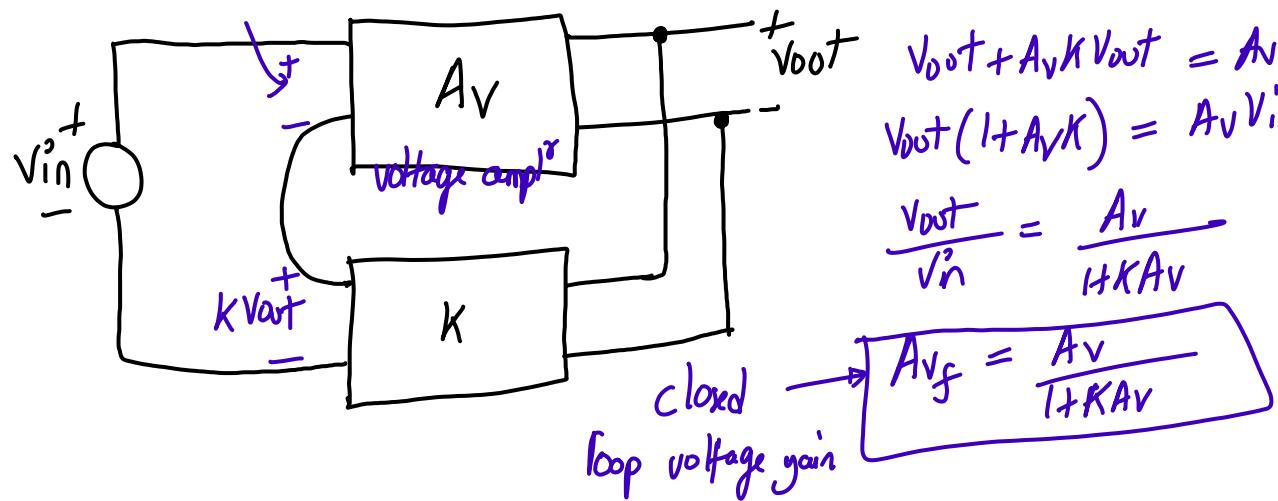
$$\frac{V_{out}}{V_{in}} = \frac{A_v}{1 + K A_v}$$



$$A_{vf} = \frac{A_v}{1 + K A_v}$$

