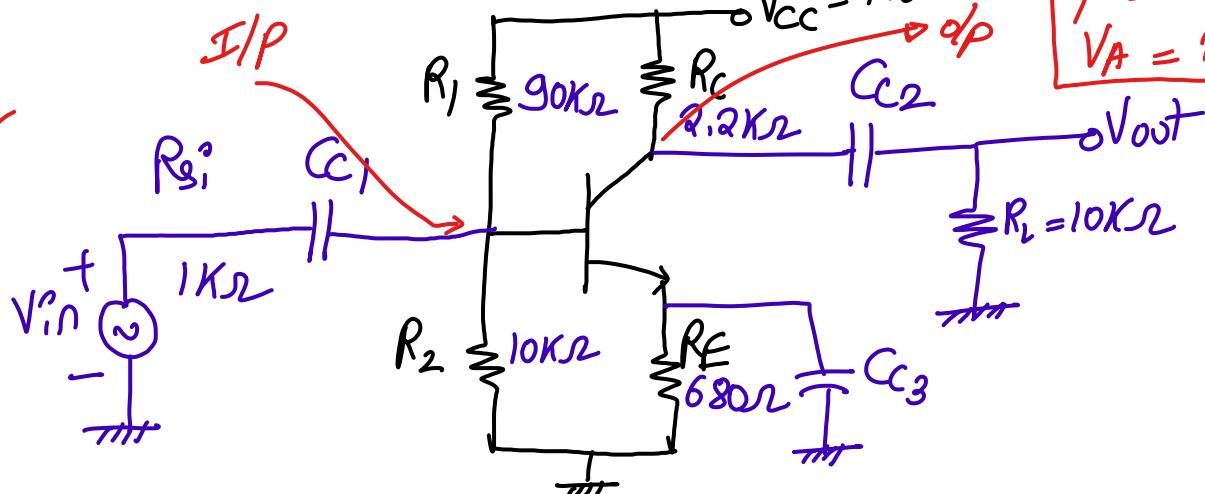


Numerical 11: Find voltage gain, R_{in} & R_{out}

CE
amp)




$$\beta = 210$$

$$V_A = 100V$$

Solution:

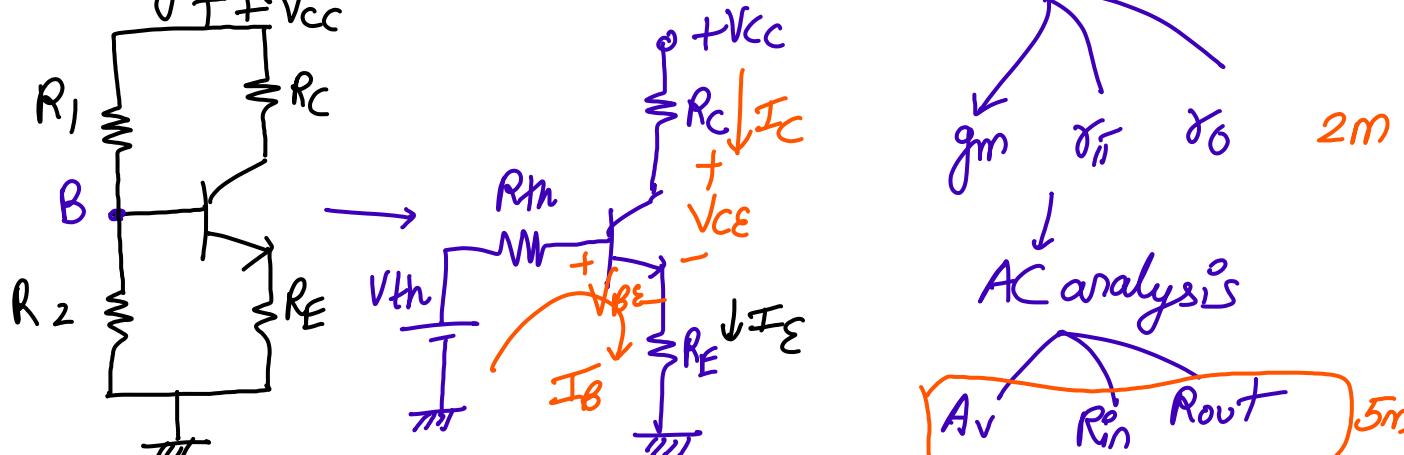① DC Analysis (o.c all caps) → AIM → I_{CQ} 3



AC analysis
 A_v R_{in} R_{out} 5m
 $f_E = (1 + \beta) f_B$

- KVL to IIP loop (B-E),

$$V_{th} - I_B R_{th} - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E}$$

$$V_{BF} = 0.7V$$

(assume)

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = \left(\frac{10}{90 + 10} \right) \times 16 = 1.6V$$

$$R_{th} = R_1 \parallel R_2 = 90k \parallel 10k = 9k\Omega$$

$$I_{BQ} = 5.9 \mu A$$

$$I_{BQ} = \frac{1.6 - 0.7}{9k + 2 \parallel 680}$$

$$I_{CQ} = |I_{BQ}| = 210 \times 5.9 \mu A = \underline{\underline{1.239 mA}}$$

b) Small-signal parameters:-


$$\underline{\underline{V_T = 26 mV}}$$

$$g_m = \frac{I_{CQ}}{\sqrt{T}} = \frac{1.239 \times 10^{-3}}{26 \times 10^{-3}} = \underline{\underline{47.67 \frac{mA}{V}}}$$

$$r_{II} = \frac{\beta}{g_m} = \frac{210}{47.67 \times 10^{-3}} = \underline{\underline{4.4 k\Omega}}$$

$$\gamma_0 = \frac{V_A}{I_{CQ}} = \frac{100}{1.239 \times 10^{-3}} = \underline{\underline{80.68 k\Omega}}$$

c) AC analysis:-

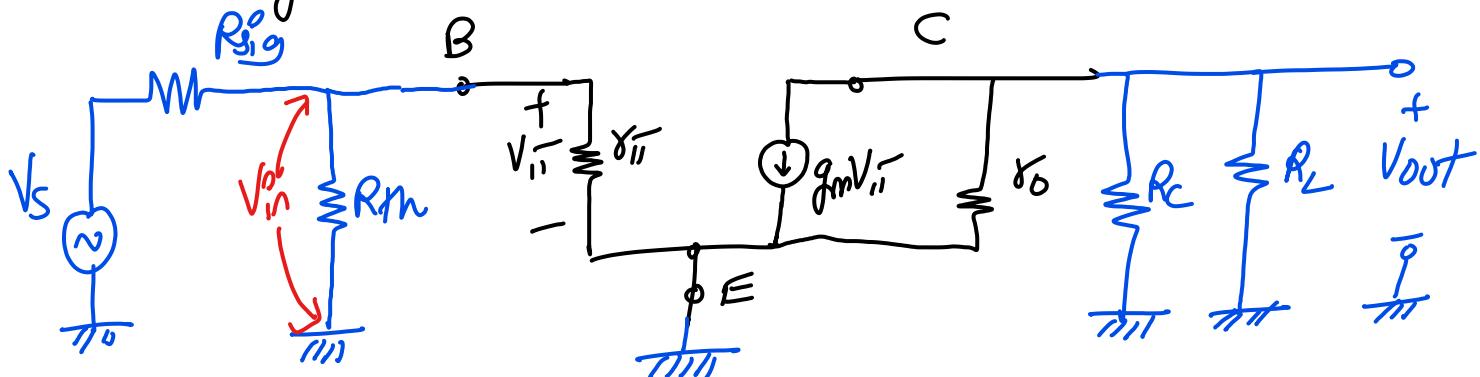

a) Voltage gain (A_V): $A_V = \frac{V_{out}^o}{V_S} = \frac{V_{out}^o}{V_{in}^o} \frac{V_{in}^o}{V_S}$

$$\frac{V_{out}^o}{V_{in}^o} = -g_m (\gamma_0 || R_C || R_L)$$

$$\frac{V_{in}^o}{V_S} = \left(\frac{R_{th} || \gamma_0}{R_{th} || \gamma_0 + R_{sig}} \right)$$

$$R_{th} = R_1 || R_2$$

b) Input resistance ' R_{in}^o ': $R_{in}^o = (R_1 || R_2 || \underline{\underline{\gamma_0}}) + R_{sig}$

$$R_{in}^o = 2.95 k\Omega + 1 k\Omega = \underline{\underline{3.95 k\Omega}}$$

c) Output resistance ' R_{out} ': $R_{out} = (\gamma_0 || R_C || R_L)$

$$80.68 k\Omega \quad 0.2 k\Omega \quad 10 k\Omega$$

$$R_{out} = 1.76 \text{ k}\Omega$$

$$4) \frac{V_{out}}{V_{in}} = - g_m \left(\frac{\delta_0 || R_C || R_L}{1.76 \text{ k}\Omega} \right) = - 47.67 \times 10^{-3} \times 1.76 \times 10^3$$

$$\frac{V_{out}}{V_{in}} = -83.8$$

$$\frac{V_{in}}{V_s} = \frac{R_m || r_{in}}{R_{in} || r_{in} + R_{sig}} = \frac{2.95 \text{ k}\Omega}{2.95 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.746$$


$$A_V = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s} = -83.89 \times 0.746$$

$$A_V = -62.65$$

I/p & o/p are out of phase

2] Degenerated CE amplifier:

(CE amplifier with RE unbypassed)

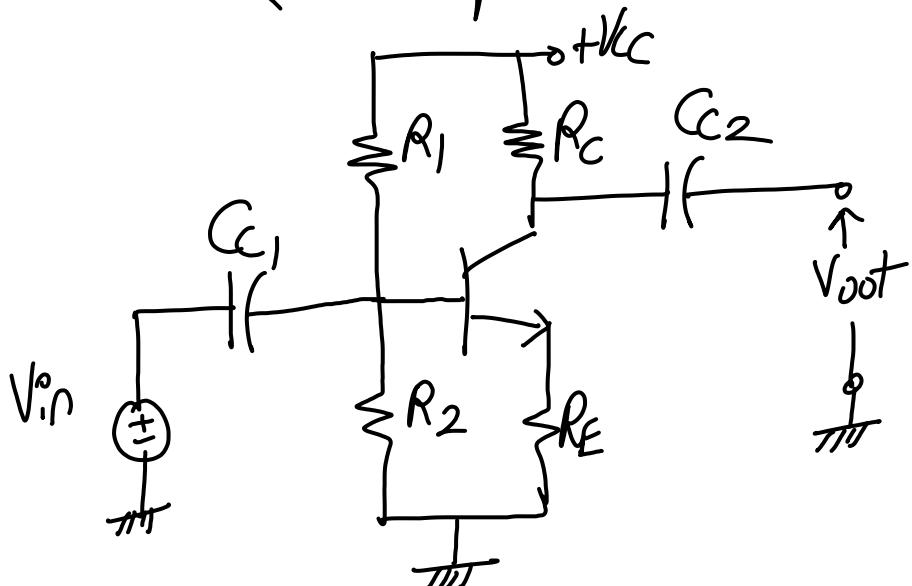

$$\delta_0 = \infty$$

$$A_V = -g_m (R_C)$$

No R_L , No δ_0

$$A_V = \frac{V_{out}}{V_{in}} \approx - \frac{R_C}{\frac{1}{g_m} + R_E}$$

(A_V have reduced but more stable)

$$R_{in} = R_1 || R_2 || \left[r_{pi} + (1+\beta) R_E \right] \quad (R_{in} \uparrow \text{sed})$$

$R_{out} = R_C$ (R_{out} remains same)

—x—

24, 25, 44, 58, 8, 3, 55, 45,
75, 72, 85, 78, 100, 80, 64, 54

Attendance: AEC lec 11 @ 10/8/23

