

Numerical 4: For the following circuit, find  $I_B$ ,  $I_C$  &  $V_{CE}$ ,  $S$

Solution:

a) KVL to  $\text{B-E}$  loop:

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (1+\beta) I_B R_E = 0$$

$$V_{CC} - V_{BE} = I_B (R_B + (1+\beta) R_E)$$

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E} \quad \mu A$$

$$\therefore I_{BQ} = \left( \frac{20 - 0.7}{430 \times 10^3 + 51 \times 1 \times 10^3} \right) = \underline{40.12 \mu A}$$

$$\therefore I_{CQ} = \beta I_{BQ} = 50 \times 40.12 \mu A = \underline{2.01 mA}$$

$V_{CEO}$ : KVL to  $\text{B-C}$  loop,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$I_E = I_B + I_C \quad \mu A / mA$$

$$V_{CEOQ} = V_{CC} - I_C R_C - I_E R_E \quad (I_B + I_C)$$

$$I_E \approx I_C$$

$$V_{CEOQ} = 20 - (2.01 \times 10^{-3} \times 2 \times 10^3) - (40.12 \times 10^{-6} + 2.01 \times 10^{-3}) \times 1 \times 10^3$$


$$V_{CEOQ} = \underline{13.92} V$$

Plot of DC load line:

$$V_{CE} = V_{CC} - I_C (R_C + R_E) \rightarrow \text{load line eqn}$$

$$\textcircled{1} \text{ Put } I_C = 0, V_{CE} = V_{CC} \rightarrow (V_{CC}, 0)$$
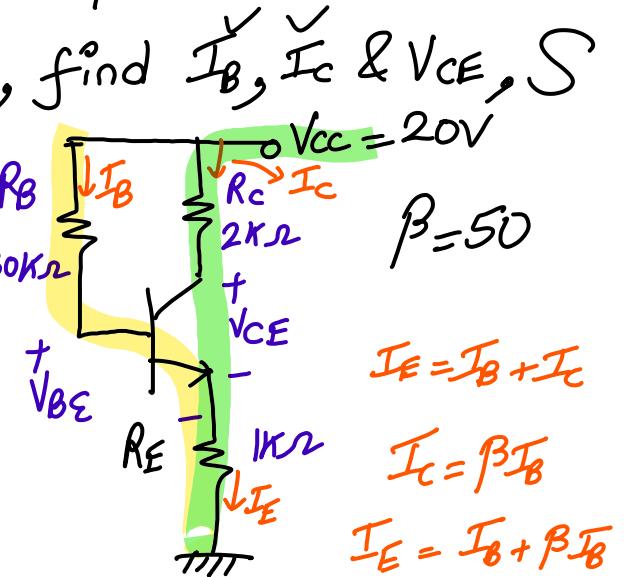
$$\textcircled{2} \text{ Put } V_{CE} = 0, I_C = \frac{V_{CC}}{R_C + R_E} \rightarrow (0, \frac{V_{CC}}{R_C + R_E})$$



$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$


$$I_E = I_B + \beta I_B$$

$$I_E = (1+\beta) I_B$$

$$V_{BE} = 0.7V \quad (\text{assume})$$

$$40.12 \mu A$$

$$I_E = I_B + I_C \quad \mu A / mA$$

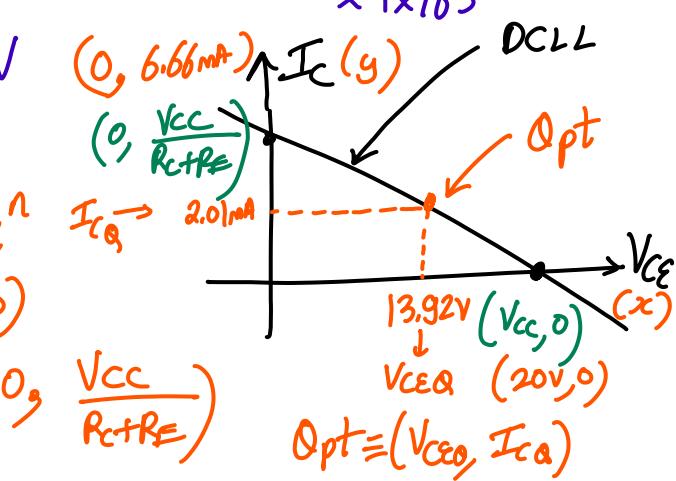

$$I_C = -\frac{V_{CE}^{(x)}}{R_C + R_E} + \frac{V_{CC}^{(c)}}{R_C + R_E}$$

$m = \frac{-1}{R_C + R_E} \quad (y = mx + c)$

$c = \frac{V_{CC}}{R_C + R_E}$

Stability factor: ( $S$ )  $\rightarrow S = \frac{1 + \beta}{1 - \beta \left( \frac{\partial I_B}{\partial I_C} \right)}$

KVL to  $I_B$ ,  $V_{CC} - I_B R_B - V_{BE} - (I_B + I_C) R_E = 0 \quad \text{--- (1)}$

Dif<sup>n</sup> eq<sup>n</sup> (1) w.r.t  $I_C$ ,


$$0 - R_B \frac{\partial I_B}{\partial I_C} - 0 - R_E - R_E \frac{\partial I_B}{\partial I_C} = 0$$

$$\frac{\partial I_B}{\partial I_C} (R_B + R_E) = -R_E$$

$$\frac{\partial I_B}{\partial I_C} = -\frac{R_E}{R_B + R_E}$$

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_B + R_E} \right)} = \frac{1 + 50}{1 + 50 \left( \frac{1K}{430K + 1K} \right)} = \frac{45.69}{45.69}$$

**Numerical 5:** Find  $R_C$  &  $R_E$

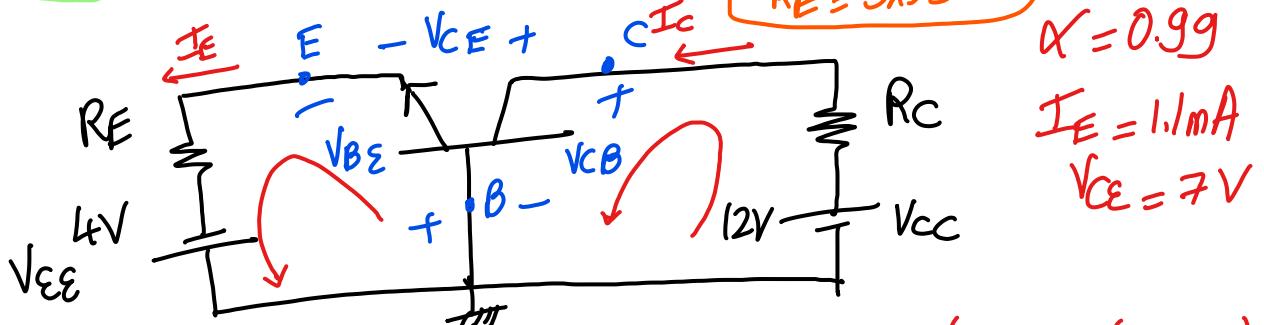

**Solution:**

① KVL to  $I_B$  loop,  $V_{EE} - I_E R_E - V_{BE} = 0$

$$R_E = \frac{V_{EE} - V_{BE}}{I_E} = \frac{4 - 0.7}{1.1 \times 10^{-3}} = 3\text{k}\Omega$$

$$V_{BE} = 0.7 \text{ (assume)}$$

$$I_C = \alpha I_E = 0.99 \times 1.1\text{mA} = 1.089\text{mA}$$

$$\textcircled{2} \quad V_{CB} = V_{CE} - V_{BE} = 7 - 0.7 = \underline{6.3V} \quad (V_{BC} = -6.3V \rightarrow B-C J^n \text{ is R.B})$$

\textcircled{3} KVL to the o/p (B-C) loop,

$$V_{CC} - I_C R_C - V_{CB} = 0$$

$$\text{i.e } I_C R_C = V_{CC} - V_{CB}$$

$$\text{i.e } R_C = \frac{V_{CC} - V_{CB}}{I_C}$$

$$\text{i.e } R_C = \frac{12 - 6.3}{1.089 \times 10^{-3}}$$

$$\text{i.e } \boxed{R_C = 5.23 \text{ k}\Omega}$$

## II Collector to base bias:


→ Find Opt  $= (V_{CEO}, I_{CO})$

\textcircled{1} KVL to o/p loop,  $\rightarrow I_{BO}$

$$V_{CC} - (I_C + I_B) R_C - I_B R_B - V_{BE} = 0$$

$\downarrow \beta I_B$
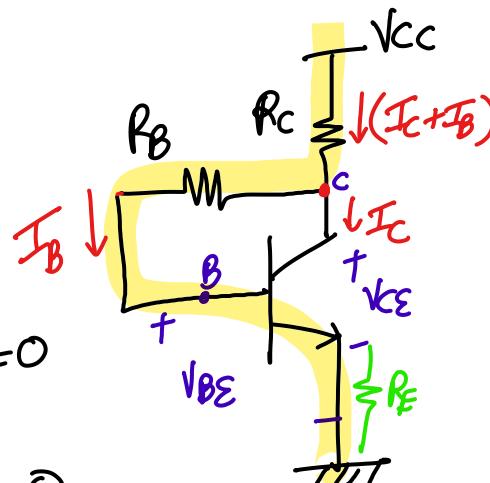
$$\text{i.e } V_{CC} - (1 + \beta) I_B R_C - I_B R_B - V_{BE} = 0$$



$R_B$  bet^n C & B


$$\boxed{I_{BO} = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)(R_C + R_E)}}$$

$$; I_{CO} = \beta I_{BO}$$

\textcircled{2} KVL to o/p loop,

$$V_{CC} - (I_C + I_B) R_C - V_{CE} = 0$$
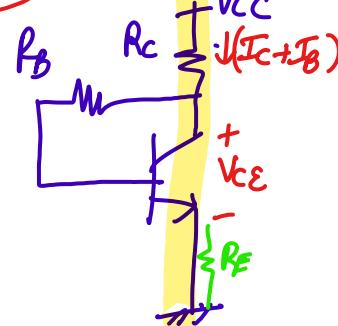
$$\boxed{V_{CE} = V_{CC} - (I_C + I_B)(R_C + R_E)}$$



$$③ S = \frac{1+\beta}{1-\beta \left( \frac{\partial I_B}{\partial I_C} \right)} - ①$$

$$\text{KVL to } \Delta \text{P}, V_{CC} - (I_C + I_B) R_C - I_B R_B - V_{BE} = 0 - ②$$

Diffr eqn ② w.r.t  $I_C$ ,

$$0 - R_C - \frac{\partial I_B}{\partial I_C} R_C - \frac{\partial I_B}{\partial I_C} R_B - 0 = 0$$

$$- \frac{\partial I_B}{\partial I_C} (R_C + R_B) = R_C$$

$$\boxed{\frac{\partial I_B}{\partial I_C} = - \frac{R_C}{R_C + R_B}}$$

$$S = \frac{1+\beta}{1+\beta \left( \frac{R_C + R_E}{R_C + R_B + R_E} \right)}$$


Numerical 6: Find  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$  and  $S$  for ckt below,

KVL to  $\Delta P$  loop,

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_C}$$

10V  
 0.7  
 500x10<sup>3</sup>  
 101

3x10<sup>3</sup>

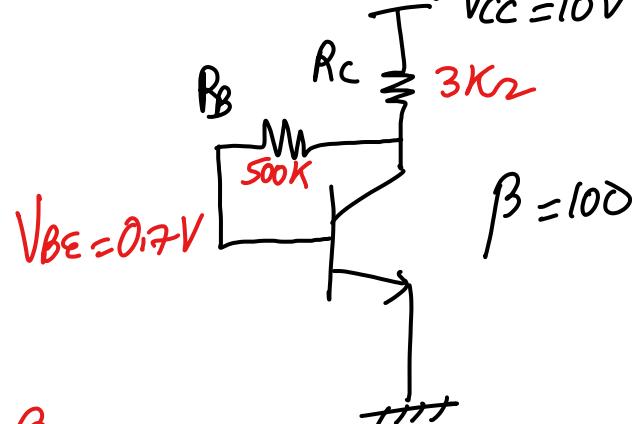

$$I_{BQ} = \frac{11.58}{500} \mu A ; I_{CQ} = \frac{1.158}{3} mA$$

KVL to  $\Delta P$  loop,


$$V_{CEQ} = V_{CC} - (I_C + I_B) R_C$$

10V  
 1.158mA  
 1.158x10<sup>-3</sup>  
 3k2

$$; V_{CEQ} = \frac{6.49V}{}$$

$$S = \frac{1+\beta}{1+\beta \left( \frac{R_C}{R_C + R_B} \right)} = \frac{101}{1+100 \left( \frac{3}{500+3} \right)} = \frac{63.267}{}$$

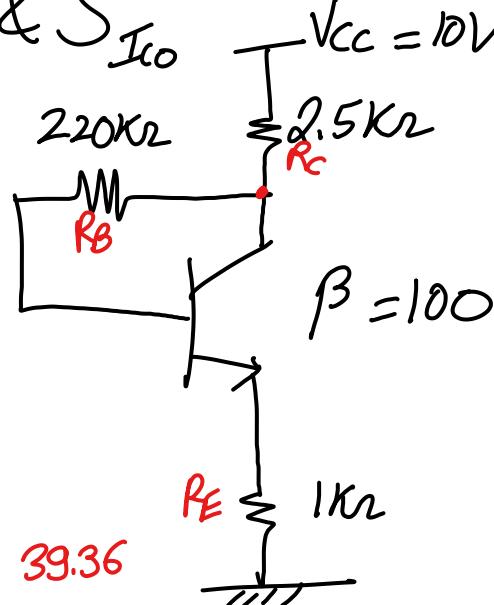Numerical 7: Find  $I_{CQ}$ ,  $V_{CEQ}$ , &  $S_{I_{CQ}}$   
(HW)



$$I_{CQ} = 1.62 \text{ mA}, V_{CEQ} = 4.269 \text{ V}, S = 39.36$$

Solution:

$$\textcircled{1} \quad I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)(R_C + R_E)} = \underline{16.216 \mu A}$$

10V  
 0.7  
 220k 101 2.5k 1kΩ

$$\textcircled{2} \quad I_{CQ} = \beta I_B = 100 \times 16.216 \mu A = \underline{1.621 \text{ mA}}$$

$$\textcircled{3} \quad V_{CEQ} = V_{CC} - (I_B + I_C)(R_C + R_E) = \underline{4.269 \text{ V}}$$

10V 16.216 μA 1.621 mA 2.5k 1kΩ

$$\textcircled{4} \quad S = \frac{1+\beta}{1+\beta \left( \frac{R_C + R_E}{R_C + R_E + R_B} \right)}$$

$$\text{ie } S = \frac{101}{1+100 \left( \frac{2.5+1}{2.5+1+220} \right)}$$

$$S = \underline{39.36}$$

88, 93, 69, 40, 42, 39,  
 97, 100, 67, 41, 7, 45, 25,  
 16, 80, 85, 78, 50, 58, 44, 70, 46, 64

Attendance (AEC b/c 7, 2/8/23)













