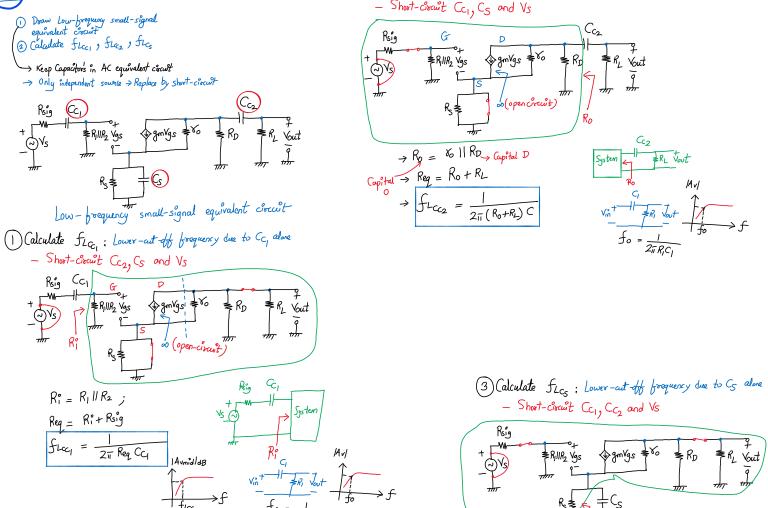


AEC 24

Step 5: Calculate Low-cut-off frequency of the circuit (f_L):



Step 6: Calculating f_L

Learning:

- External capacitors C_{C1} , C_{C2} and C_S will affect only low-frequency response
- A_V is gain constant


Select the highest frequency among f_{LC1} , f_{LC2} and f_{LC3} as the lower (f_L) cut-off frequency of the amplifier

* Transient $V_{out}(t)$ vs t at one freq (10kHz)

In transient analysis, the frequency at AC signal should fall in mid-band range

* Frequency response: Response of amplifier at different frequencies

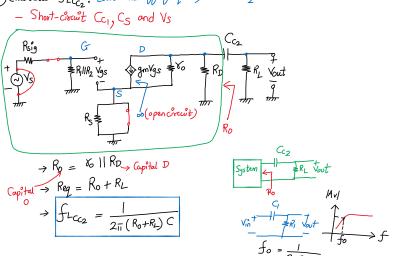② Calculate f_{LC2} : Lower-cut-off frequency due to C_{C2} alone



③ Calculate f_{LC3} : Lower-cut-off frequency due to C_S alone


- Short-circuit C_{C1} , C_{C2} and V_S

$R_{T1} = R_1 \parallel R_2$; $R_{T2} = R_1 + R_2$

$$f_{LC3} = \frac{1}{2\pi R_{T2} C_S}$$

* Procedure to calculate R_{eq} :

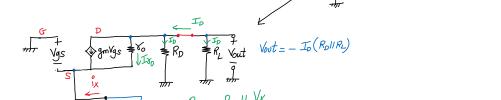- Apply a test source V_x and force current i_x into it
- Find $R_{eq} = \frac{V_x}{i_x}$



$$\rightarrow \text{From above circuit, we can write}$$

$$V_x = -V_{GS}$$

$$\rightarrow i_x = \frac{V_{out} - V_x}{R_{eq}} = \frac{V_{out} + V_{GS}}{R_{eq}} \dots (2.1)$$

$$\rightarrow \text{KCL at node } S_2$$

$$i_x + g_m V_{GS} + i_{D2} = 0$$

$$\therefore i_x + \left(g_m + \frac{1}{R_{D1} \parallel R_{D2}} \right) V_{GS} = 0 \dots (2.2)$$

$$\rightarrow V_{out} = -i_x (R_{D1} \parallel R_{D2})$$

$$\rightarrow \text{Substitute } V_{out} \text{ in equation (2.2),}$$

$$\rightarrow i_x + \left(g_m + \frac{1}{R_{D1} \parallel R_{D2}} \right) V_{GS} = -\frac{i_x}{R_{D1} \parallel R_{D2}}$$

$$\rightarrow \text{From circuit, } i_x = -i_D$$

$$\rightarrow i_x + \left(g_m + \frac{1}{R_{D1} \parallel R_{D2}} \right) V_{GS} + \frac{i_x}{R_{D1} \parallel R_{D2}} = 0$$

$$\rightarrow V_{GS} = -V_x$$

$$\rightarrow i_x \left(1 + \frac{R_{D1} \parallel R_{D2}}{R_{eq}} \right) = V_x \left(g_m + \frac{1}{R_{eq}} \right)$$

$$\therefore \frac{V_x}{i_x} = \frac{\left(1 + \frac{R_{D1} \parallel R_{D2}}{R_{eq}} \right)}{g_m + \frac{1}{R_{eq}}}$$

$$\therefore \frac{V_x}{i_x} = \left(\frac{R_{D1} \parallel R_{D2}}{1 + g_m R_{eq}} \right)$$

$$R_{eq} = R_1 \parallel \left(\frac{V_x + (R_{D1} \parallel R_{D2})}{1 + g_m R_{eq}} \right)$$

$$R_{eq} = R_1 \parallel \frac{1}{g_m}$$